
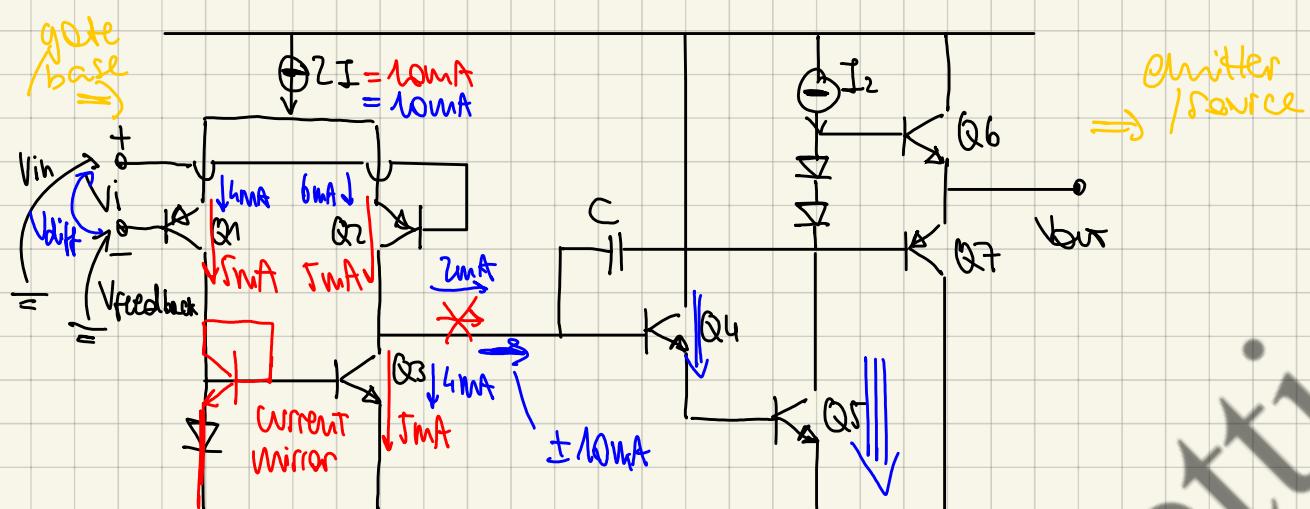

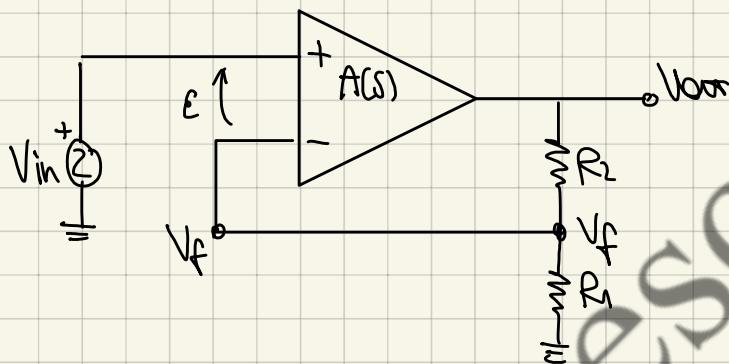
## VOLTAGE MODE OPAMP (VVA - VOLTAGE OPERATING AMPLIFIER)



REQUIREMENTS :

- Voltage-driven inputs → high impedance inputs
- Voltage output → low impedance output



$$V_o = \epsilon \cdot A_o = \propto \cdot \infty$$

$\epsilon \rightarrow \infty$

$\Rightarrow V_f \rightarrow V_{in}$  (virtual ground)

$$\Rightarrow V_{out} \frac{R_1}{R_1+R_2} = V_f = V_{in} \Rightarrow$$


$$G_{VVA} = 1 + \frac{R_2}{R_1}$$

TRADE-OFF GAIN-BW

GBWP remains constant

Performances

## CURRENT FEEDBACK AMPLIFIER (CFA)

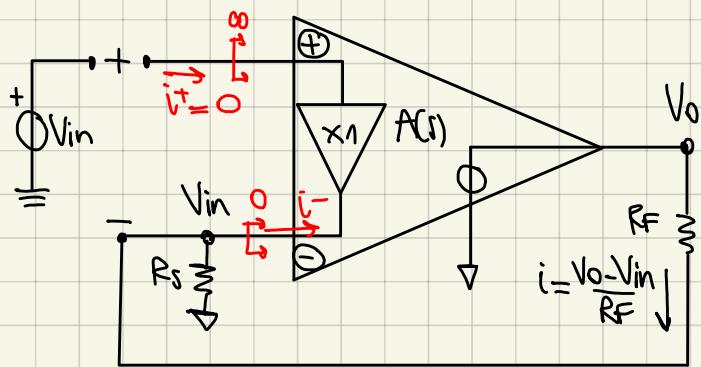


REQUIREMENTS :

- One high-impedance input (hence voltage driven input)
- One low-impedance input (hence input-current, i.e. acting as an output)
- Voltage output (proportional to the input current)


CFA GAIN

$$G_{CFA} = 1 + \frac{R_f}{R_s}$$

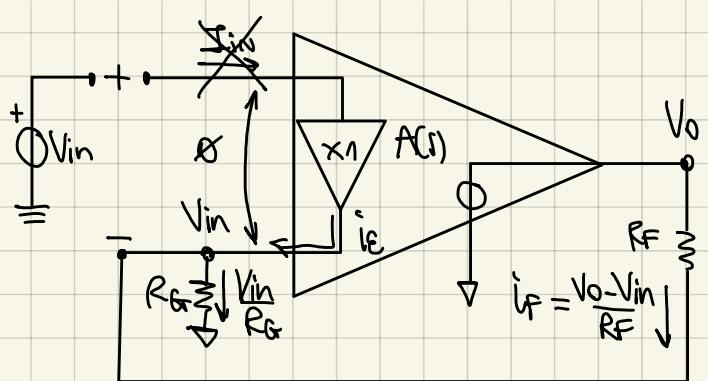

$V_0 = i_e \cdot R_G = 0 \cdot \infty$  Thanks to FG  
 ideally:  $i_e \rightarrow 0$  input buffer can provide current, but it's not needed thanks to feedback  
 $i_F \rightarrow \frac{V_{in}}{R_f}$
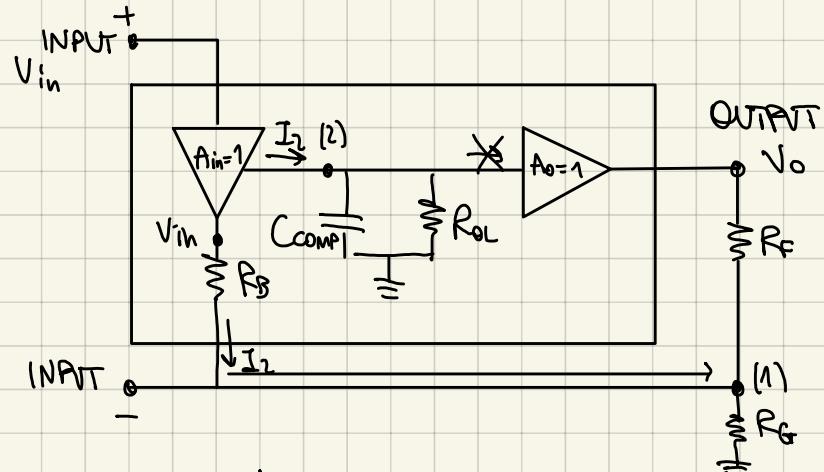
$$\frac{V_{in}}{R_G} = \frac{V_0 - V_{in}}{R_F} \Rightarrow \frac{V_0}{V_{in}} = \frac{1}{R_G} + \frac{1}{R_F} = \frac{R_F + R_G}{R_G R_F}$$



$$(1) I_2 = \frac{V_{in} - V_1}{R_B} = \frac{V_{in} - V_{out}}{R_F} + \frac{V_1}{R_G} \\ = V_1 \left( \frac{1}{R_G} + \frac{1}{R_F} \right) - \frac{V_{out}}{R_F}$$

$$(2) V_1 = I_2 \left( \frac{1}{sC \cdot R_{out}} \right) = I_2 \frac{R_{out}}{1 + sC_{comp} R_{out}} = V_0$$

Doing computations we end up w/:

CLIPED LOOP GAIN

$$\frac{V_{out}}{V_{in}} = \frac{1 + R_F/R_G}{\left( 1 + \frac{R_F + (1 + R_F/R_G) R_B}{R_{out} \cdot A_{out}} \right) \left[ 1 + s \frac{\left[ R_F + (1 + R_F/R_G) R_B \right]}{A_{out} + \frac{R_F (1 + R_F/R_G) R_B}{R_{out}}} \cdot C_{comp} \right]}$$

$$f_{out} \approx \frac{A_{out}}{2\pi \left[ R_F + (1 + \frac{R_F}{R_G}) R_B \right] C_{comp}}$$

• for low gain:  $\left( R_B \ll \frac{R_F R_G}{R_F + R_G} = R_F // R_G \right) \rightarrow f_{out} \approx \frac{1}{2\pi R_F C_{comp}}$

→ BW depends only on  $R_F$ , not on  $R_B$ , hence not on gain!

• for high gain ( $> 50$ )  $\rightarrow f_{BW} = \frac{A_{out}}{2\pi R_B \cdot C_{comp}}$

→ As for VOA, again BW stays constant → trade-off gain vs BW

By changing  $R_f$  we can change the gain of the stage w/o changing its frequency response, i.e. its SW

If we want to reach very high gain, since  $G = 1 + R_f/R_g$ ,  $R_f$  should be high, while  $R_g$  should be small.


If  $R_g = 10 \Omega \rightarrow$  set  $R_f \approx 10 R_g$  at VEST, but under this condition the gain cannot increase too much.

### ES07 - CFA (2)

26/10/2021

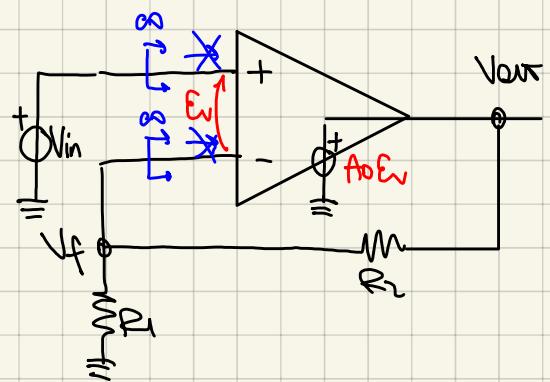
### V<sub>OA</sub>

Up to now we have worked w/ V<sub>OAs</sub>, which is an amplifier w/ high input impedances (ideally  $\infty$ )



$$\begin{aligned} \text{Since } A_o \rightarrow \infty &\rightarrow G_{\text{voa}} = A_o \beta \rightarrow \infty \\ \Rightarrow E_v &\rightarrow 0 \\ \Rightarrow V_f &\equiv V_{\text{in}} \\ V_{\text{out}} \frac{R_1}{R_1 + R_2} &= V_{\text{in}} \\ \Rightarrow G &= \frac{V_{\text{out}}}{V_{\text{in}}} = 1 + \frac{R_2}{R_1} \end{aligned}$$

What about the freq. response?

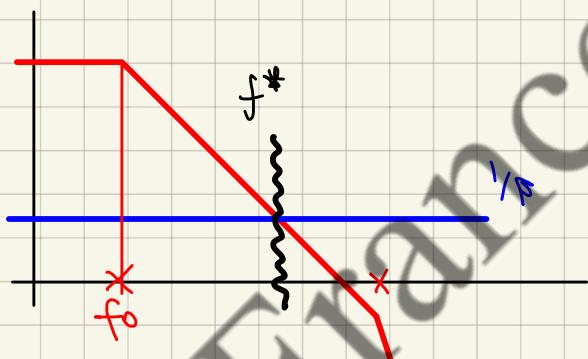

$$\beta = \frac{R_g}{R_g + R_f} \Rightarrow \frac{1}{\beta} = 1 + \frac{R_f}{R_g}$$

If we change  $G \Rightarrow$  we also change  $1/\beta$   
 $\rightarrow$  we also change  $f^*$

- if  $f \uparrow \Rightarrow \frac{1}{\beta} \uparrow \Rightarrow f^* \downarrow \quad \left. \begin{array}{l} \text{TRADE-OFF} \\ \text{GAIN-BW} \end{array} \right\}$
- if  $f \downarrow \Rightarrow \frac{1}{\beta} \downarrow \Rightarrow f^* \uparrow \quad \left. \begin{array}{l} \text{TRADE-OFF} \\ \text{GAIN-BW} \end{array} \right\}$


for example:

- if  $G = 10 \rightarrow f^* = 10 \text{ MHz}$
- if  $G = 100 \rightarrow f^* = 1 \text{ MHz}$

$G = \alpha f^*$
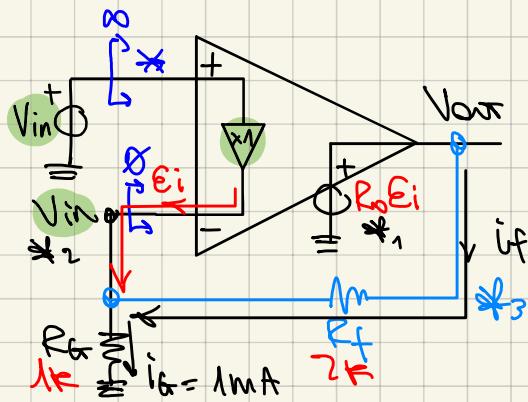
## CFA - CURRENT FEEDBACK AMPLIFIER

\*<sub>1</sub>:  $[A_0] = \infty$  since The error is a current signal so we can call it  $i_{\text{err}}$



+ input:  $R_{\text{in}}^+ = \infty \Rightarrow$  VOLTAGE READER

- input:  $R_{\text{in}}^- = \infty \Rightarrow$

\*<sub>2</sub>: here we have  $V_{\text{in}}$  thanks to the buffer, not due to the feedback, cause the feedback is not acting yet

$$\text{if } V_{\text{in}} = 1V \text{ and } R_f = 1k \Rightarrow E_i = \frac{V_{\text{in}}}{R_g} = 1\text{mA} = i_G$$

$$\Rightarrow \text{if } R_o = 1M\Omega \Rightarrow V_{\text{out}} = 1M\Omega \cdot 1\text{mA} = 1\text{mV}$$

Now we can introduce the FB

A current flowing through  $R_f$  tries and it tends to go towards the  $\ominus$  pin where the input resistance is nil

if  $R_o \rightarrow \infty \Rightarrow E_i \rightarrow 0$  thanks to the FB

$$\Rightarrow V_{\text{out}} = R_o \cdot E_i = [\infty] \cdot [0] = 1 + \frac{R_f}{R_g} = 3V$$

$V_{\text{out}}$  does not saturate, but it settles to 3V in such a way that:

if  $= \frac{3V - 1V}{2k} = \frac{2V}{2k} = 1\text{mA} = i_G \rightarrow$  The current that the FB can provide is the sum current that  $R_o$  requires

$E_i = 0$  even if the  $\ominus$  input can provide current since  $R_{\text{in}}^- = 0$


• In The VOA,  $E_i$  could be different to zero, but it isn't, but thanks to the FB  $E_i \rightarrow 0$


• In The CFA,  $E_i$  could be different to zero, but it isn't, but thanks to the FB  $E_i \rightarrow 0$

$$i_f = i_G \Rightarrow \frac{V_{\text{out}} - V_{\text{in}}}{R_f} = \frac{V_{\text{in}}}{R_g} \Rightarrow G = \frac{V_{\text{out}}}{V_{\text{in}}} = 1 + \frac{R_f}{R_g}$$

NOTICE (IMP!!): The big ADVANTAGE of The CFA is that you can adjust the gain as you wish but the pole remains at a constant frequency  
 → To do so, we must change just  $R_f$
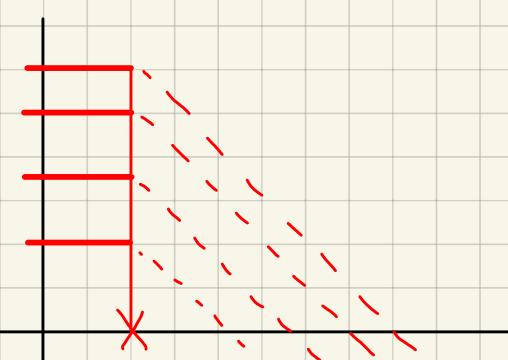
$$\text{In fact } f_p = \frac{1}{2\pi C R_f}$$



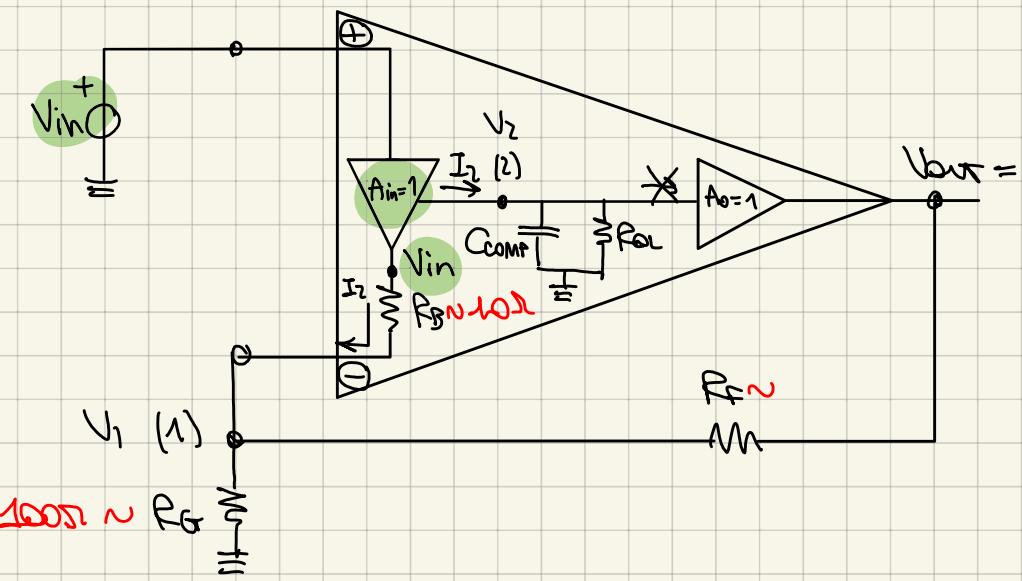

$$(1) \quad I_2 = \frac{V_{in} - V_1}{R_B} = \frac{V_1 - V_{out}}{R_f} + \frac{V_1}{R_g}$$

$$= V_1 \left( \frac{1}{R_g} + \frac{1}{R_f} \right) - \frac{V_{out}}{R_f}$$

$$(2) \quad V_2 = I_2 \left( \frac{1/C \cdot R_{fb}}{1/C + R_{fb}} \right) = I_2 \frac{R_{fb}}{1 + s C_{comp} R_{fb}} = V_0$$

Doing computations we end up w/:

UNFD  
LOOP GAIN

$$\frac{V_{out}}{V_{in}} = \frac{1 + R_f/R_g}{\left( 1 + \frac{R_f + (1 + R_f/R_g) R_B}{R_{fb} \cdot A_{out}} \right) \left[ 1 + s \frac{R_f + (1 + R_f/R_g) R_B}{A_{out} + \frac{R_f (1 + R_f/R_g) R_B}{R_{fb}}} \cdot (C_{comp}) \right]}$$

### CFA BANDWIDTH

$$f_{BW} \approx \frac{A_{out}}{2\pi \left[ R_f + \left( 1 + \frac{R_f}{R_g} \right) R_B \right] C_{comp}}$$

- for low gain:  $\left( R_B \ll \frac{R_f R_g}{R_f + R_g} = R_f // R_g \right) \rightarrow f_{BW} \approx \frac{1}{2\pi R_f C_{comp}}$

→ BW depends only on  $R_f$ , not on  $R_g$ , hence not on gain!

- for high gain ( $> 50$ )  $\rightarrow f_{BW} = \frac{A_{out}}{2\pi R_B \cdot C_{comp}}$


→ As for VOA, again BW stays constant → trade-off gain vs BW

let's study the FG in a smarter way:

- Open loop:  $\text{pole}_{\text{OL}} \approx \frac{1}{C_{\text{comp}} R_{\text{OL}}}$   $\text{G}_{\text{OL}} \approx -R_{\text{in}} \cdot A_{\text{FGWP}} \frac{1}{R_{\text{OL}} + R_{\text{F}}} \approx -\frac{R_{\text{in}}}{R_{\text{F}}}$
- Closed loop:  $\text{pole}_{\text{CL}} = \text{pole}_{\text{OL}} (1 - \text{G}_{\text{OL}}) \approx \frac{-1}{C_{\text{comp}} R_{\text{OL}}} \cdot \frac{R_{\text{in}}}{R_{\text{F}}} = \frac{-1}{C_{\text{comp}} \cdot R_{\text{F}}}$

We set  $C_{\text{comp}} = 1 \mu\text{F}$   $R_{\text{in}} = 1 \text{M}\Omega$   $R_{\text{F}} = 1 \text{k}\Omega$   $R_{\text{OL}} = 10 \Omega$
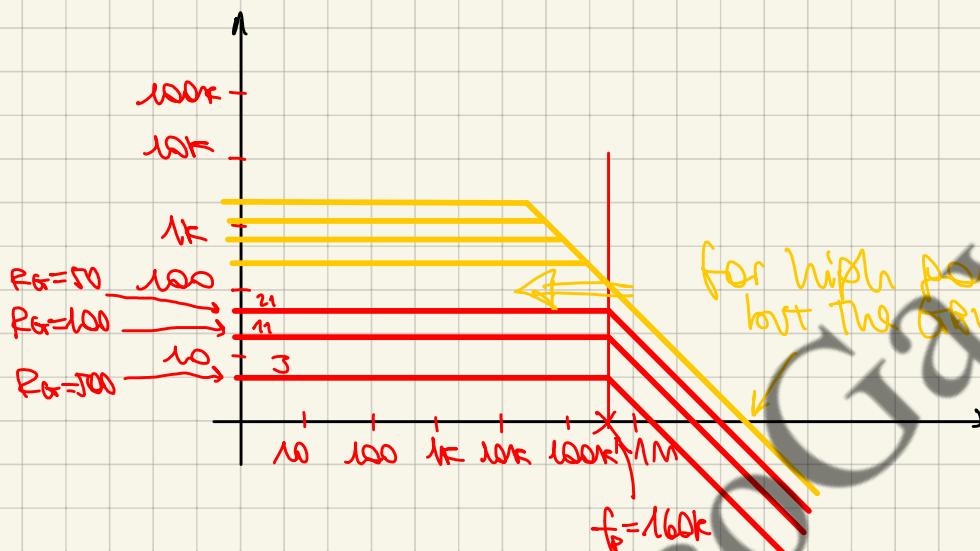
$$f_p = \frac{1}{2\pi C_{\text{comp}} R_{\text{F}}} \approx 160 \text{ kHz}$$




if  $R_G = 1\Omega \Rightarrow f_p$  doesn't stay @ 160kHz anymore

Why? Because if  $R_G$  becomes comparable to  $R_{\text{F}}$ , the gain increases too much and  $f_p$  is no more constant, but the GFWP becomes constant

## REAL ARCHITECTURE OF THE CFA

STEP 1: we need to design a BUFFER


### SOLUTION ① BUFFER = Emitter Follower

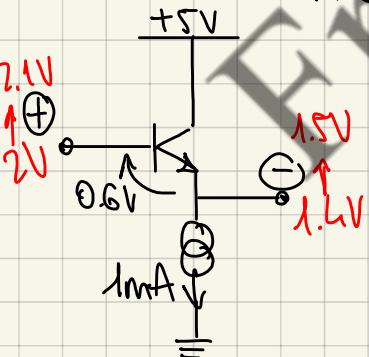

$\Rightarrow$  in this way we loose 0.6V  $\Rightarrow$  There's 0.6V of offset (600mV)

ISSUE! 😢

### SOLUTION ②

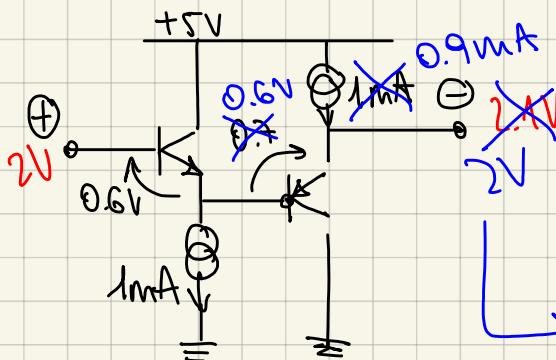

$\Rightarrow$  There's 8mV & 100mV offset 😢


\* we can close it by changing the current

$\hookrightarrow$  NOW IT'S PERFECT!! ( $0S=0$ )

There's still an issue → in this way we cannot provide more than 0.9 mA to the output

→ if the output draws more than 0.9 mA ⇒ the pnp transistor interdicts (pops off!) 😢


SOLUTION ③

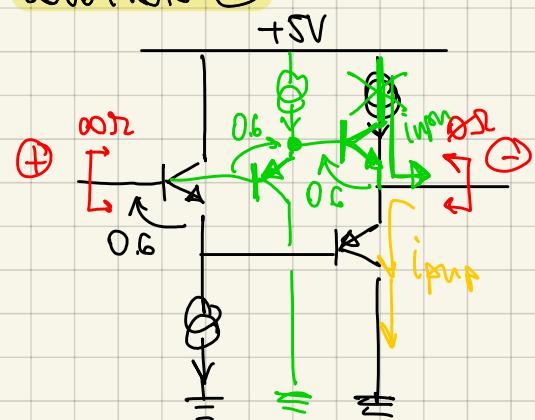

⇒ This is a symmetric voltage buffer


STEP 2: we need to make a copy of  $i_{pnp}$  to feed into  $R_{on}$

SOLUTION ④: we use a current mirror


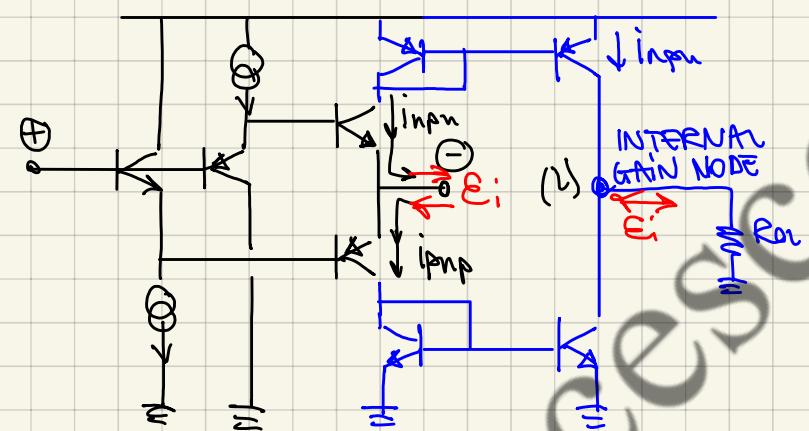


STEP 3: we want to provide the voltage across  $R_{on}$  to the output w/o drawing current from node (1)

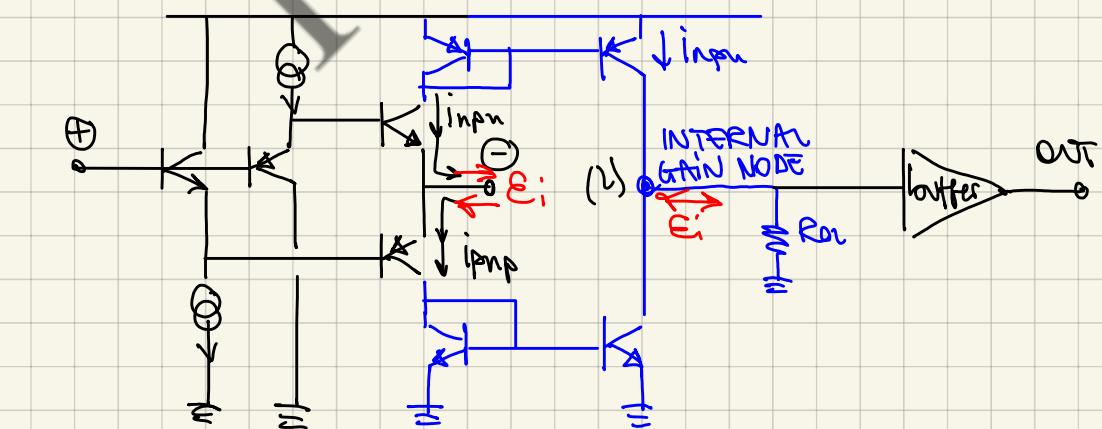How? Again, using a buffer! (which will be the same of the input one)




In conclusion we have:

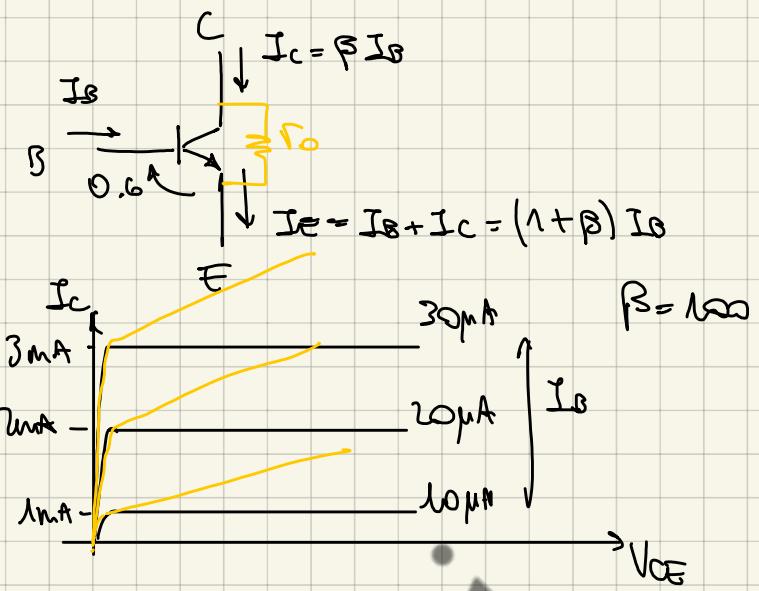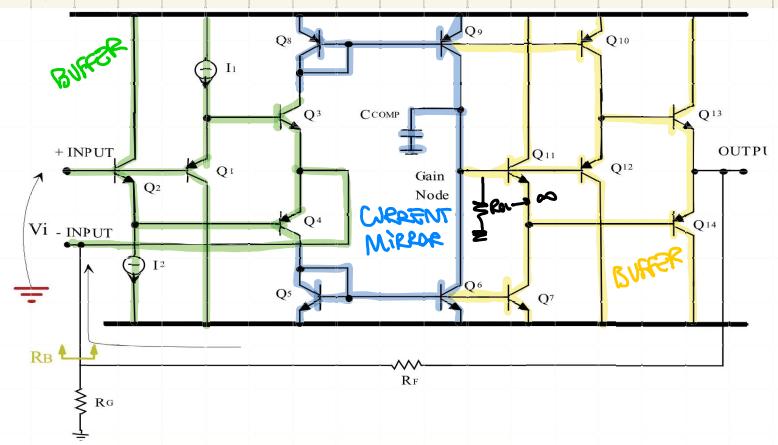

The CFA is much better than the VOA even in terms of SLEW RATE:

VOA SR

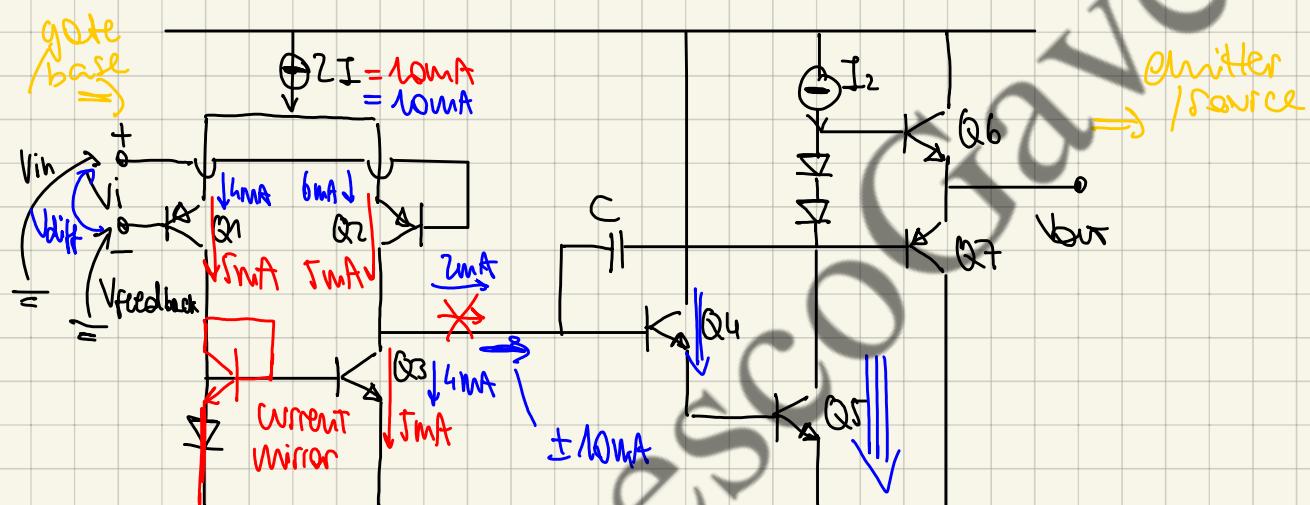


$$SR = \frac{\Delta V_{out}}{\Delta t} = \frac{I}{C_{max}} \quad \text{and since both } I \text{ and } C \text{ are fixed by the manufacturer}$$

we cannot change the SR of a VOA

$$\hookrightarrow \sim 10 \div 100 \text{ V/}\mu\text{s}$$

CFA: TRANSIENT RESPONSE → SLEW RATE

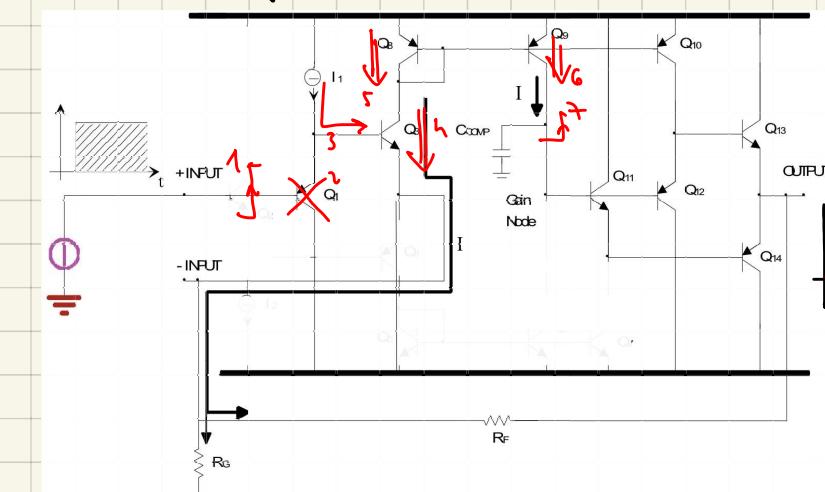Now, let's imagine to apply a step at the input of the CFA:





$$SR = \frac{dV}{dt} = \frac{I_{max}}{C_{comp}} \approx \frac{V_{step}/R_F}{C_{comp}} =$$

$$= \frac{1mA}{1pF} = \frac{50kV}{\mu s}$$

$\Rightarrow$  In a CFA, in principle, the SR can be much faster than in a VOA

COMPARISON:

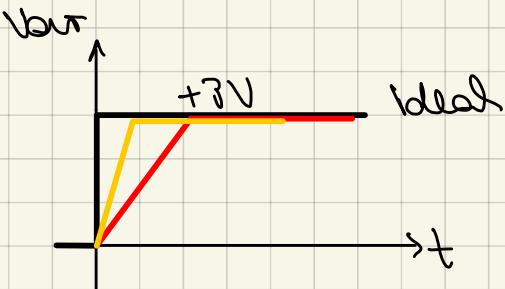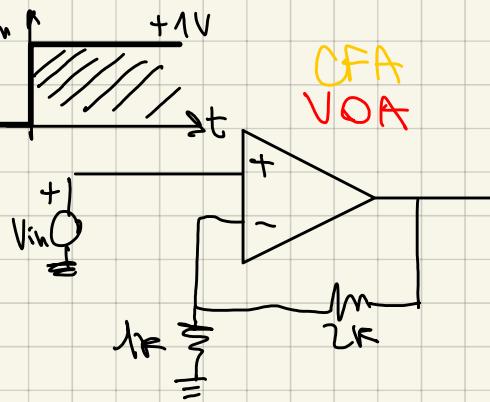


$$SR_{CFA} \sim 1k \div 100 \text{ kV}/\mu\text{s}$$

$$SR_{VOA} \sim 10 \div 100 \text{ V}/\mu\text{s}$$

At a freq. stand point:

- CFA  $\rightarrow$  The pole remains constant (for a low gain)
- VOA  $\rightarrow$  The GFWP stays constant

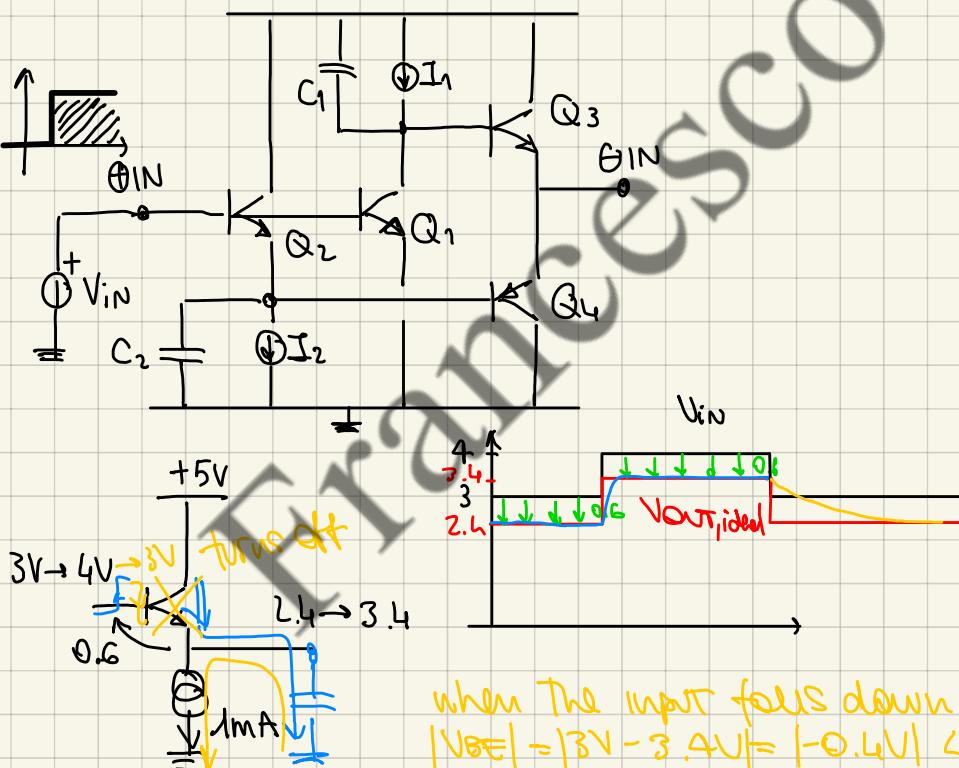Unfortunately there are parasitics that slow down also the CFA:




when the input falls down from 4V to 3V  
 $|V_{BE}| = |3V - 3.4V| = |-0.4V| < 0.6V \Rightarrow$  The transistor turns off

$\Rightarrow$  The capacitor can be discharged only through the current generator

let's add another transistor:

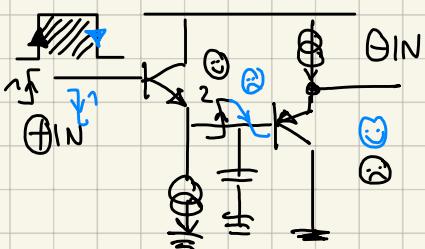a pnp transistor which is a slow transistor, so it's happy during the slow falling down




Due to parasitics the CFA is not as ideal as we supposed to be  
 ↓  
 The parasitics slow down both the pull-up and the pull-down



**How can we solve it?**

We have to introduce some improvements:

① Introduce transdiodes:


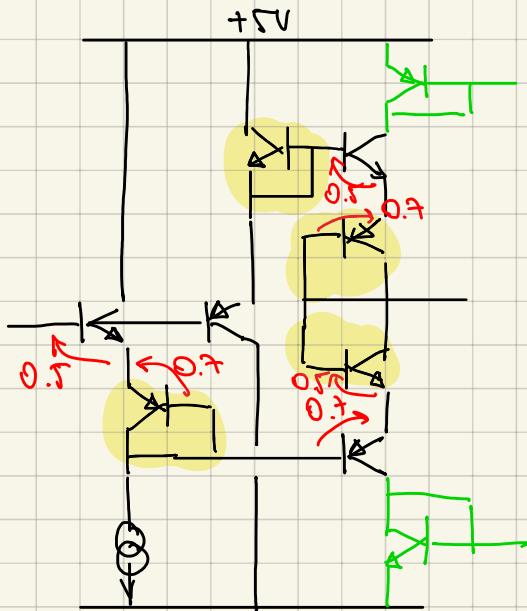


② Use multi-emitter transistors

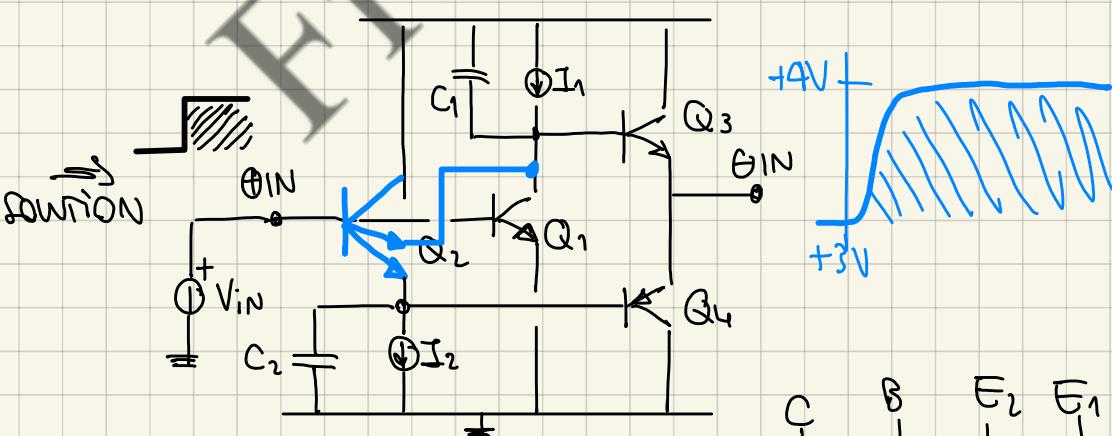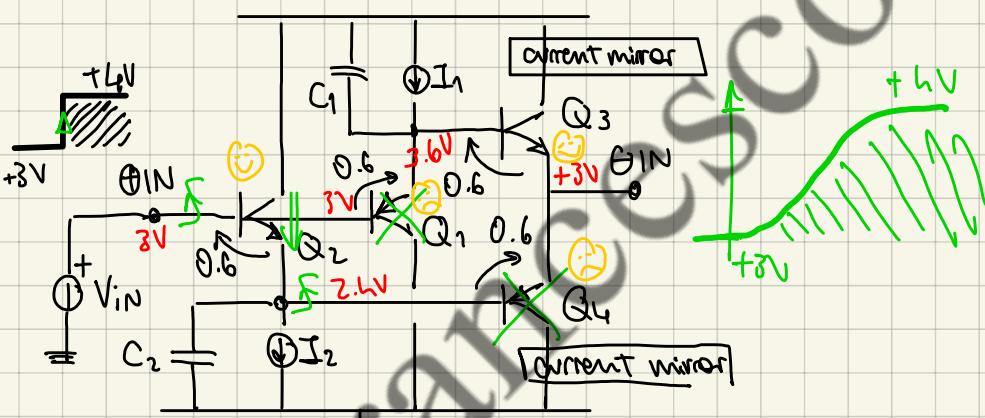

The output will speed up


What is a multi-emitter transfer??

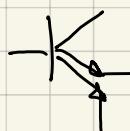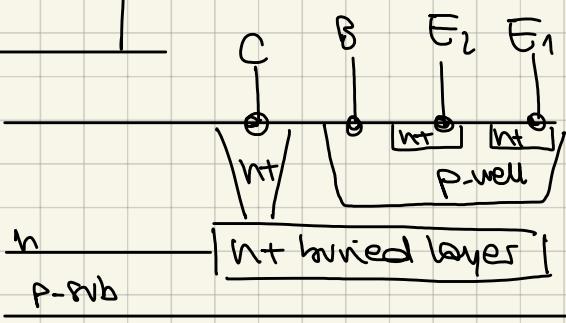


## ES08 - OTA and ISO AMPLIFIERS

26/10/2021


VOA

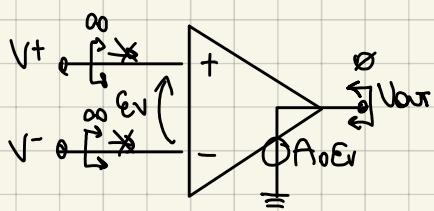



CFA

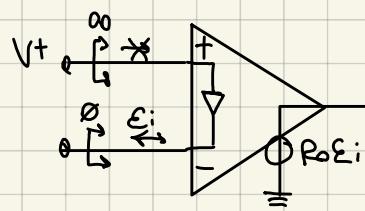

OTA

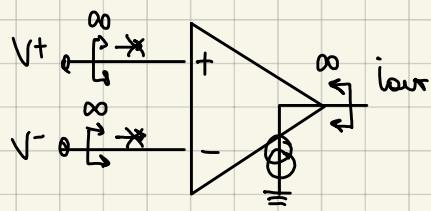

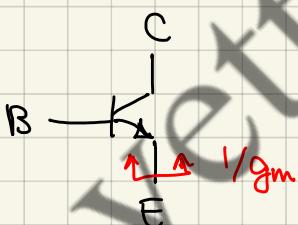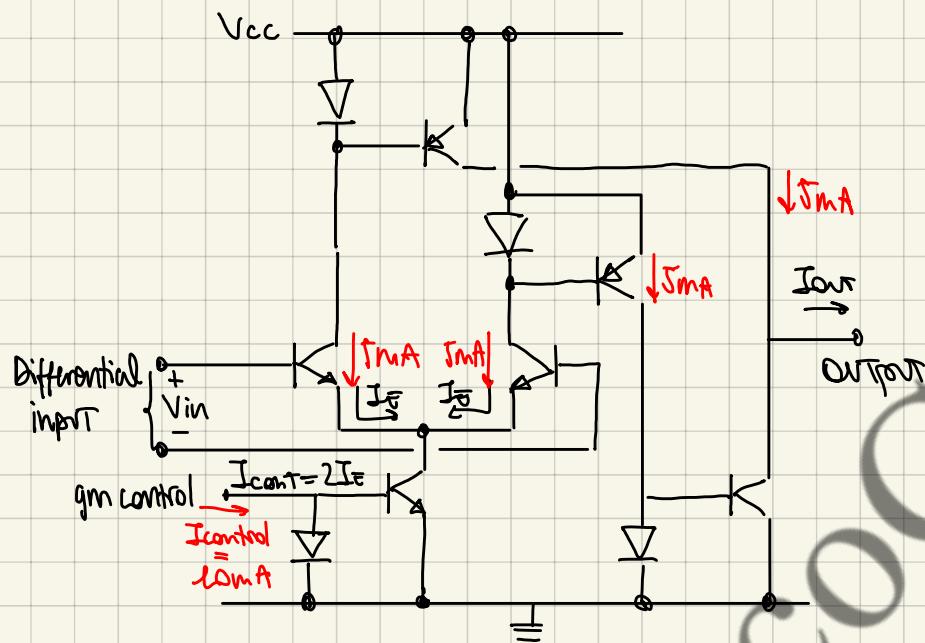**OTA : OPERATIONAL TRANSCONDUCTANCE AMPLIFIER**




$$\text{TRANSCONDUCTANCE } \frac{dI_C}{dV_{BE}} = g_m = \frac{I_C}{kT/q}$$

$$I_C = I_s (e^{\frac{V_{BE}}{kT/q}} - 1)$$



Where  $I_E$  is the current we force in the input stage

OTA:

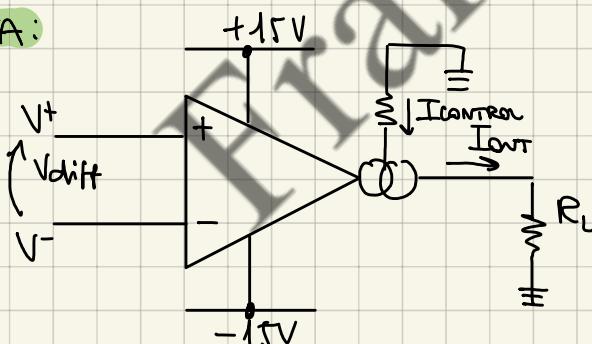

$$I_{\text{out}} = G_m \cdot V_{\text{diff}} = \frac{I_{\text{control}}}{kT/q} \cdot V_{\text{diff}} = \frac{I_{\text{control}}}{kT/q} V_{\text{diff}}$$

$$G_m = \frac{I_{\text{out}}}{V_{\text{diff}}} = \frac{I_{\text{control}}}{kT/q}$$

$$25\text{mV} \downarrow$$

$$kT/(qRT) = 25\text{mV}$$

**ADVANTAGES :** • all low-impedance nodes inside the OTA


↳ This means that any parasitism will introduce very low spurious time constants  $T = RC$  is low since  $R$  is low

• wide BW (low  $T \rightarrow$  high freq poles)


$$\omega_{\text{cutoff}} = 1/2\pi C R$$
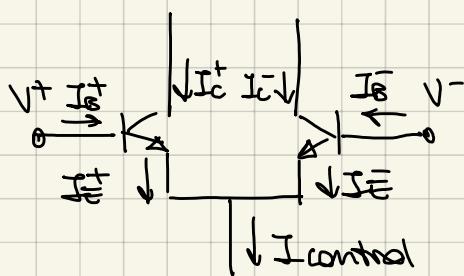
## DISADVANTAGES

- no infinite gain
- no virtual ground
- it is used open loop (but Gm is too poor)


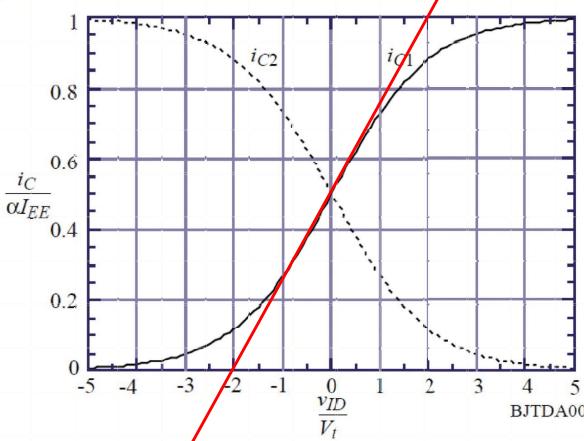
$$I_{out} = I_C^+ - I_C^- = I_{control} \cdot \text{tanh} \left( \frac{V_{diff}}{2kT/q} \right)$$





If  $V_{diff} = 0 \Rightarrow I_C^+ = I_C^-$

Up to  $|V_{diff}| \leq 2V \Rightarrow$  linear slope
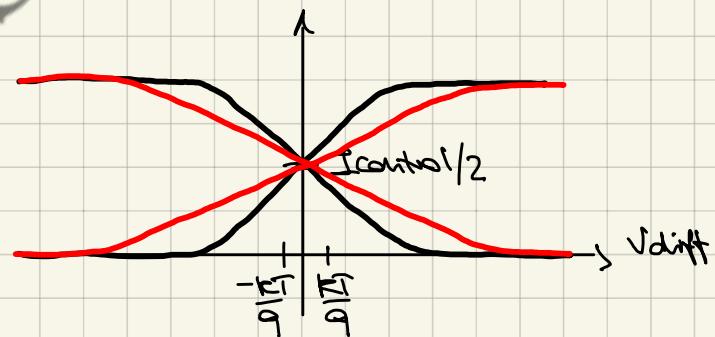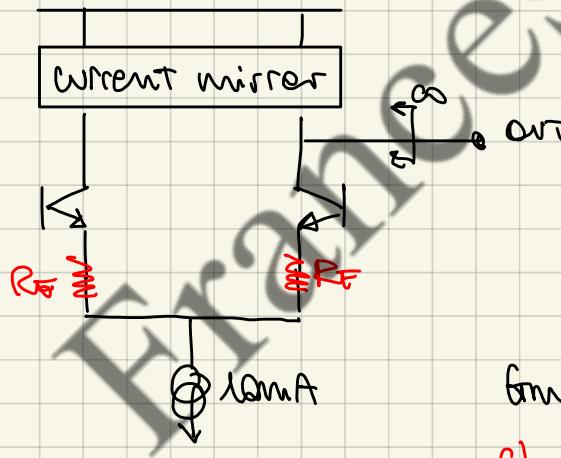
## LINEARIZATION

How can we increase the linearity of this stage?




$$f_m = I_{control}/V_{th} = g_m$$

$$g_m' = \frac{1}{1/g_m + R_F}$$

Another way to improve linearity is adding diodes into the configuration
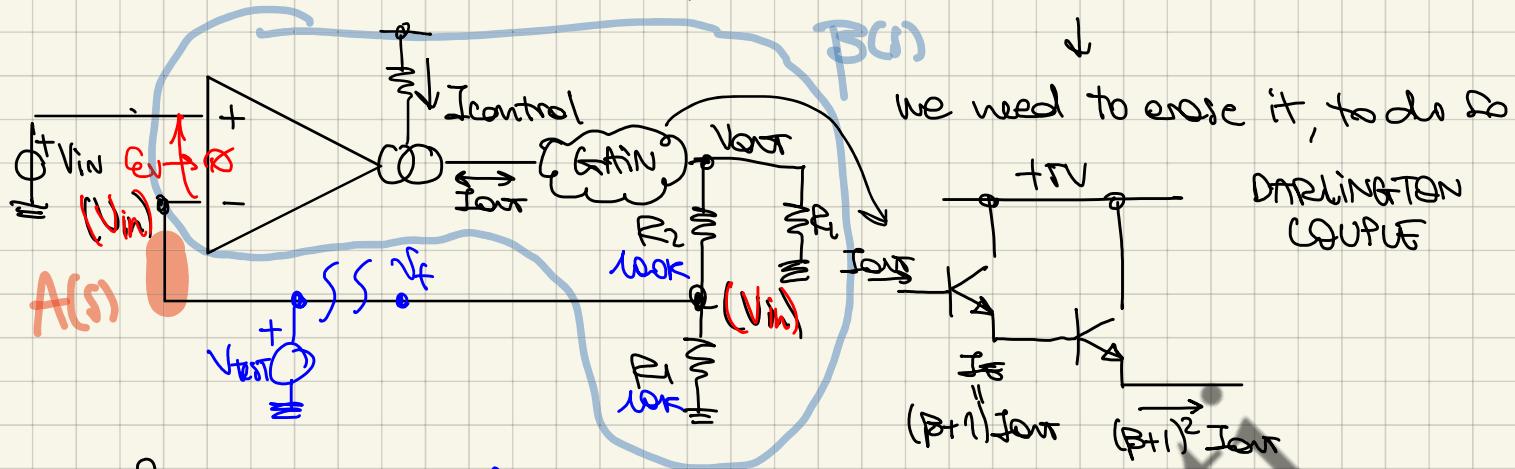
## EXAMPLE OF OTA APPLICATION: VOLTAGE-CONTROLLED LOW-PASS FILTER

I want to use the OTA in a FG config. but we can't b/c Gm<sub>op</sub> is too poor



$$G_{mop} = ?$$

$$I_{out} = V_{out} \cdot G_m$$

$$V_{out} = V_{out} \cdot G_m \cdot (\beta + 1)^2 \cdot \left[ \frac{R_f}{R_1 + R_f} \right]$$

$$V_f = V_{out} \cdot \frac{R_1}{R_1 + R_f} = V_{out} \cdot G_m \cdot (\beta + 1)^2 \cdot \left[ \frac{R_f}{R_1 + R_f} \right] \cdot \frac{R_1}{R_1 + R_f}$$

$$G_{mop} = G_m \cdot (\beta + 1)^2 \cdot \left[ \frac{R_f}{R_1 + R_f} \right] \cdot \frac{R_1}{R_1 + R_f} = \\ = \frac{I_{control}}{K T / q} \cdot (10000) \cdot 1 \text{ k} \cdot \frac{10k}{1 \text{ M}} \xrightarrow{1/11} \ggg 1$$

$$\left. \begin{array}{l} G_{mop} = G_{mop}(I_{control}) \end{array} \right\}$$


$$\text{if } G_{mop} \text{ is very high} \Rightarrow E_V \rightarrow \infty \Rightarrow V_{out} \cdot \frac{R_1}{R_1 + R_f} = V_{IN}$$

$$\Rightarrow G = \frac{V_{out}}{V_{IN}} = 1 + \frac{R_2}{R_1}$$

$$\beta(s) = G_{mop}(I_{control})$$


$$G_{ideal} = 1 + R_2/R_1$$

let's study the Bode diagram:

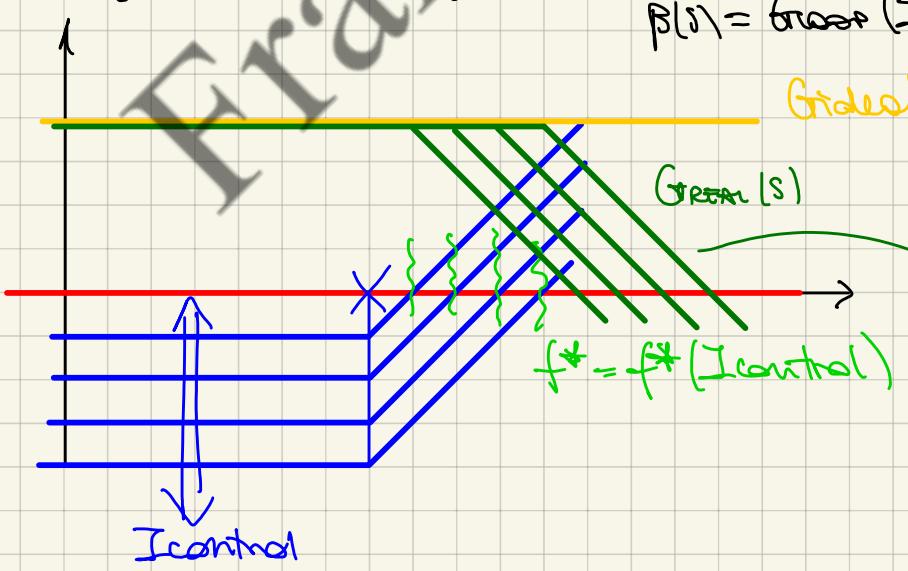

The gain is fixed but it's pole changes as function of Icontrol

pole<sub>roll-off</sub>(Icontrol)

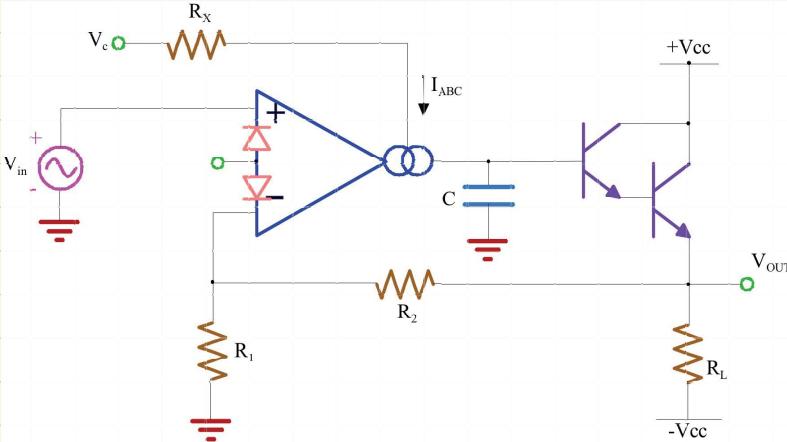

$$f_{out,RFM} = f_{out,R} (I_{control}) = f_{out,R} (V_C)$$

$$\text{since } I_{control} = I_{ABC} = V_C / R_X$$

That's why this configuration is called VOLTAGE-CONTROLLED LPF

## ES08 - OTA and ISO AMPLIFIERS (2)

27/10/2021

### ISO-ISOLATION AMPLIFIER

#### REQUIREMENTS:

- isolated input and output stages
- double power supply
- galvanic isolation

In this way, if an issue happens @ the output part it doesn't have any impact on the input and vice versa


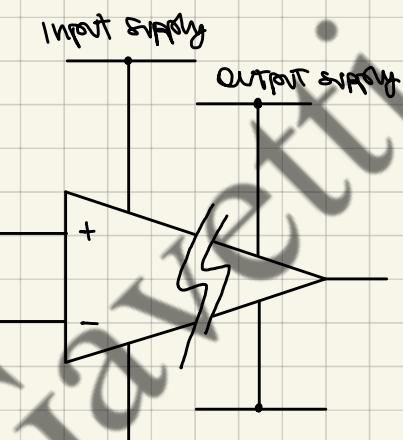


figure of merit  $\rightarrow$  ISOLATION MODE REJECTION RATIO

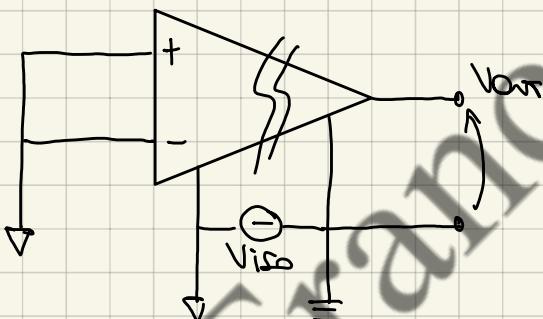


$$\hookrightarrow \text{IMRR} = 20 \log \left( \frac{V_{iso}}{V_{out}/G} \right)$$


it gives an idea on how much the isolation is able to cancel any possible voltage difference between the two power supplies

### EXAMPLE: ISOLATED POWERLINE MOTOR

#### TRIphase:

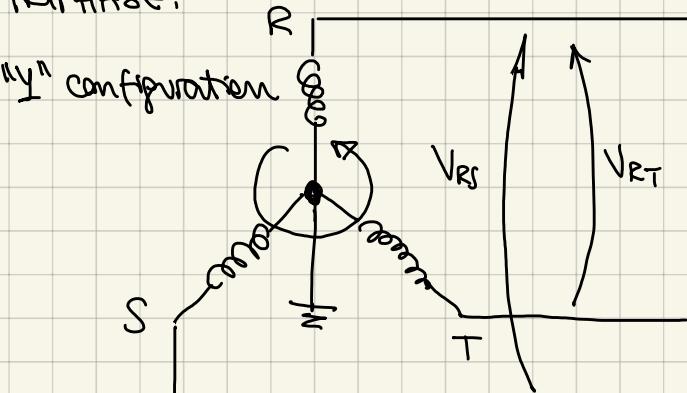

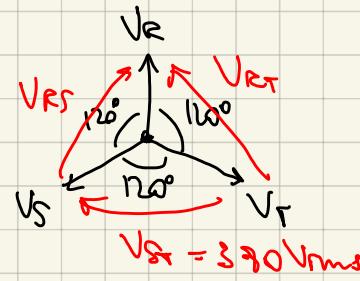
$$50\text{Hz} \\ 390\sqrt{2} \approx 500\text{V}$$




$$VS = 390\text{Vrms}$$

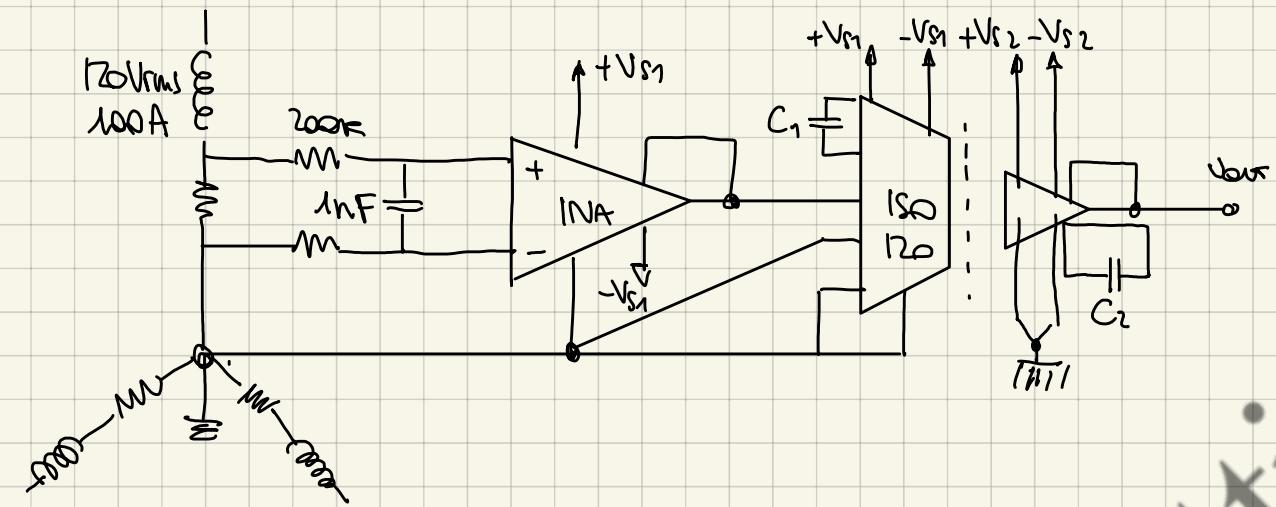If we want to measure what's the current absorption we should measure what's the current flow through each winding.


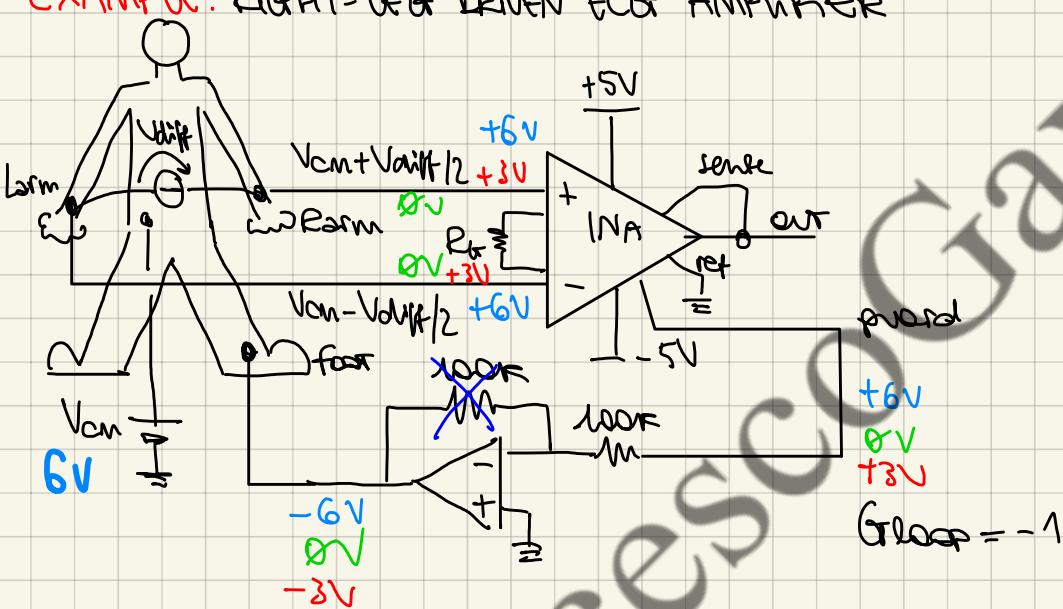
### EXAMPLE: RIGHT-LEG DRIVEN ECG AMPLIFIER




In this circuit we've introduced negative FB to reject the common mode signal but  $G_{loop}$  is too poor

we have to increase it

we can open the FB of the 2nd OpAmp \*  $\Rightarrow G_{loop} = -A_0 = -10^5$

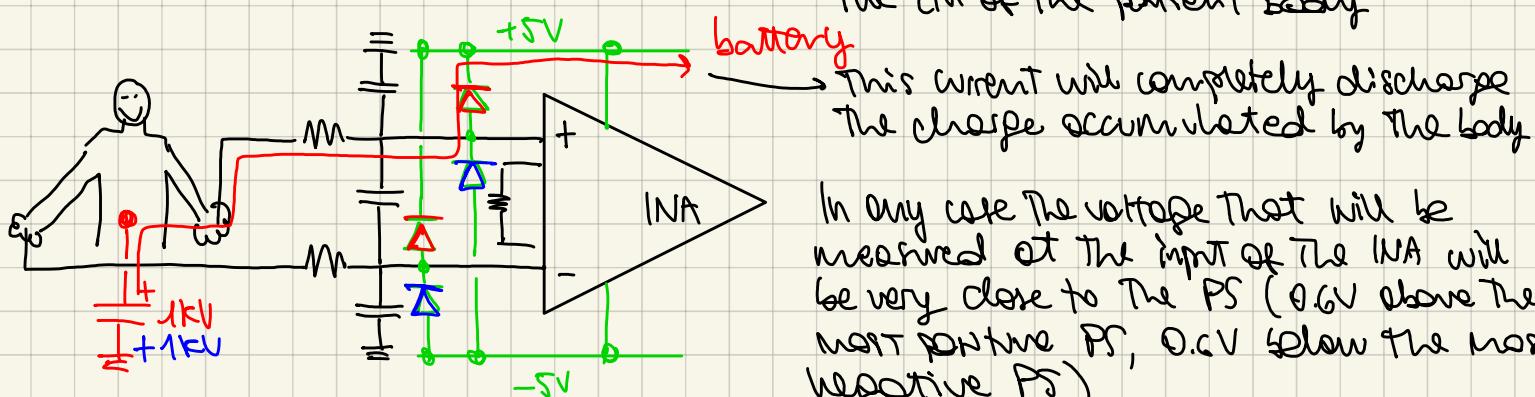in this way we are able to counterbalance the CM of the patient body



In any case the voltage that will be measured at the input of the INA will be very close to the PS (0.6V above the most positive PS, 0.4V below the most negative PS)

## ISO: TECHNIQUES

We told that in principle IMRR should be infinite but is not.  
In real circuits it's very high, up to 160dB ( $10^3$ )

ISSUE OF THE ISO: The rejection is very strong just for DC values and it decreases a lot for increasing frequencies

$$\rightarrow @ 1\text{MHz} \quad \text{IMRR} \approx 60\text{dB} = 10^3$$

Also TRANSIENT IMMUNITY could be an issue  $\rightarrow$  if the two power supplies change very quickly in a really short time, the output of the ISO could show some glitches, fluctuations and some spikes that could destroy the following electronics

$$TI < 1000\text{V/ms} \quad (\text{ISO122})$$


There are mainly 3 techniques to properly isolate the input from the output

### ① OPTICAL COUPLING


An OPTO COUPLER is an IC that contains inside one LED and one transistor

- if LED is OFF (it doesn't provide current)  
 $\rightarrow$  The transistor has no  $I_S$   $\Rightarrow I_C = \beta I_S = 0$
- if LED is ON (the LED emits internally some light)  
 $\rightarrow$  we have injection of carriers into the base of the transistor  
 $\rightarrow I_S \neq 0 \rightarrow I_C \neq 0$

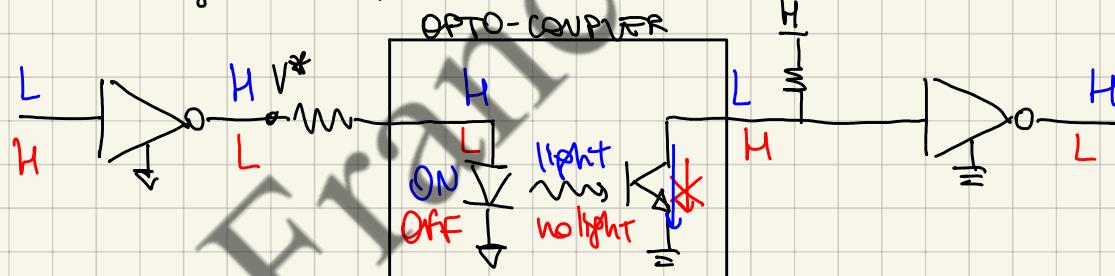Opto coupling scheme for digital information transfer:




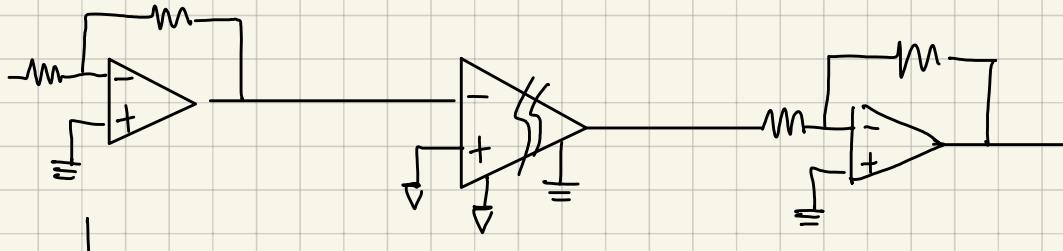Optical coupling scheme for analog information transfer:



This is the final solution, but let's reach this final solution step by step


1.

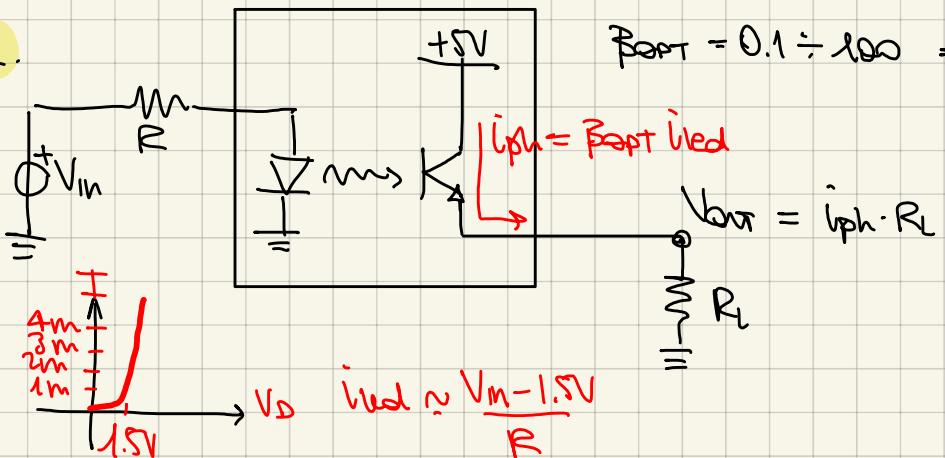

$\beta_{opt} = 0.1 \div 100 \Rightarrow$  it drifts/changes a lot  
(very high degree of mismatch)

Unfortunately this is not a good ISO amplifier b/c the relationship b/w input and output is not linear


2.

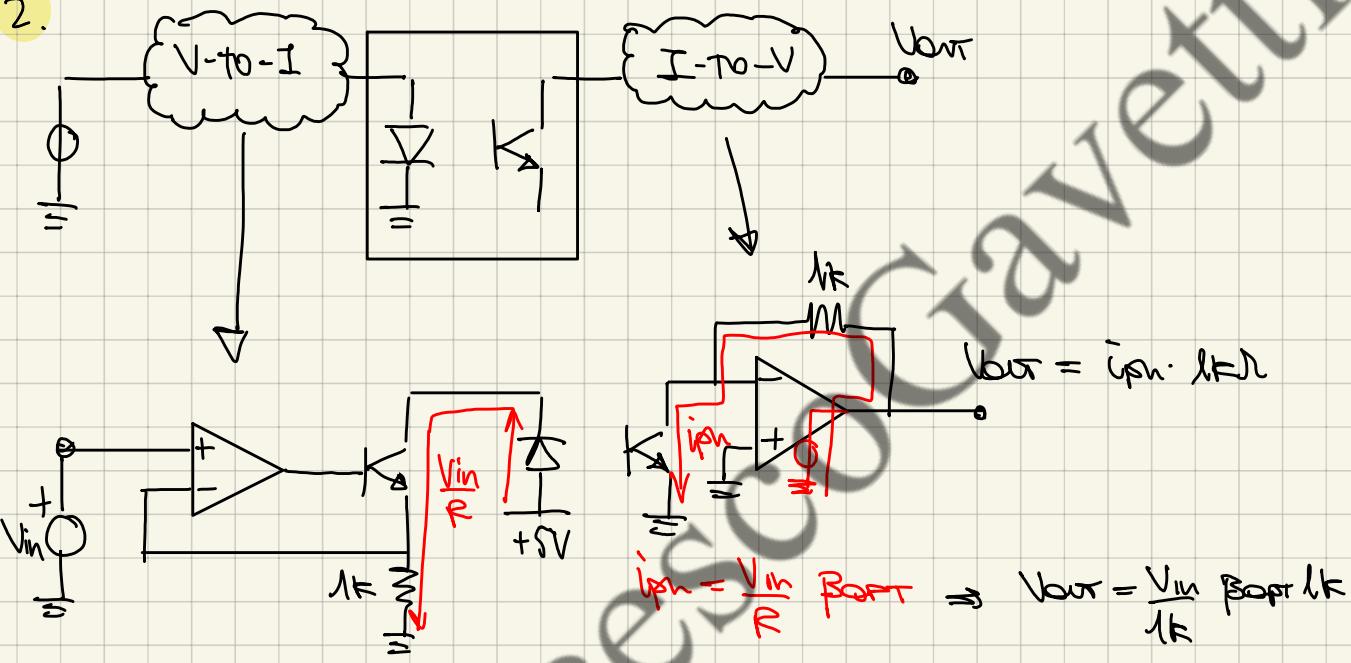


Since  $\beta_{opt}$  drifts a lot, the optoisolator is not a good component, we can exploit its non-ideality trying to compensate its non-ideality

↓  
let's use two opto-couplers which try to compensate each other

3.

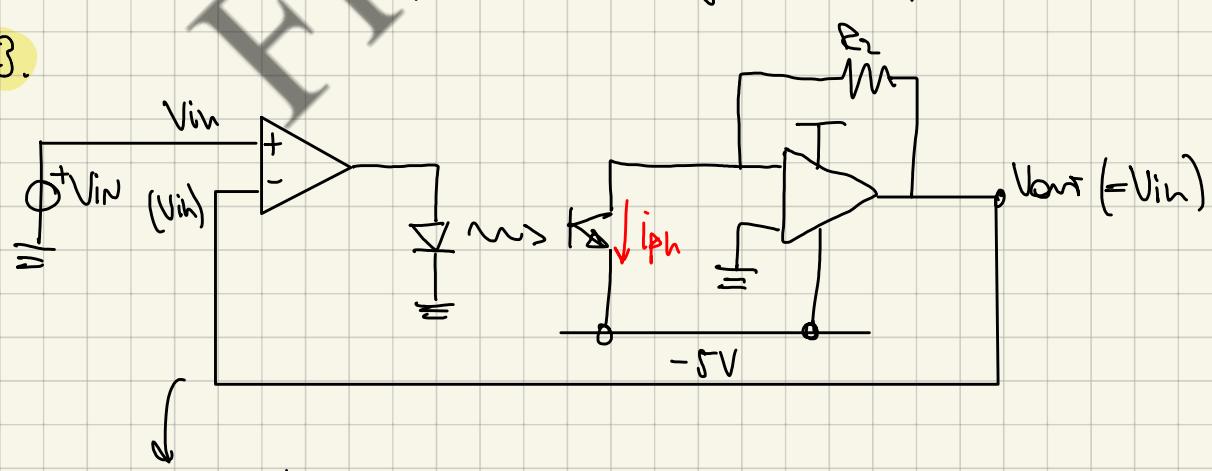

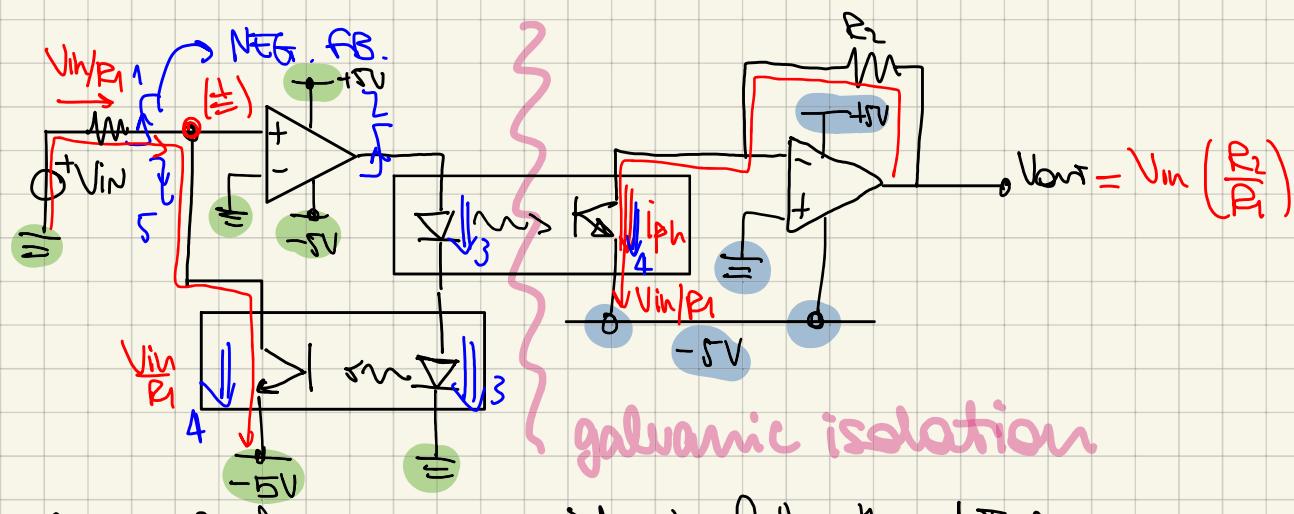we don't want a wire that connects the input to the output, b/c we want galvanic isolation




let's place a 2nd opto-coupler identical to the 1st one


$$G_t = R_2/R_1$$

$\oplus$   
galvanic isolation 

## EXAMPLE:

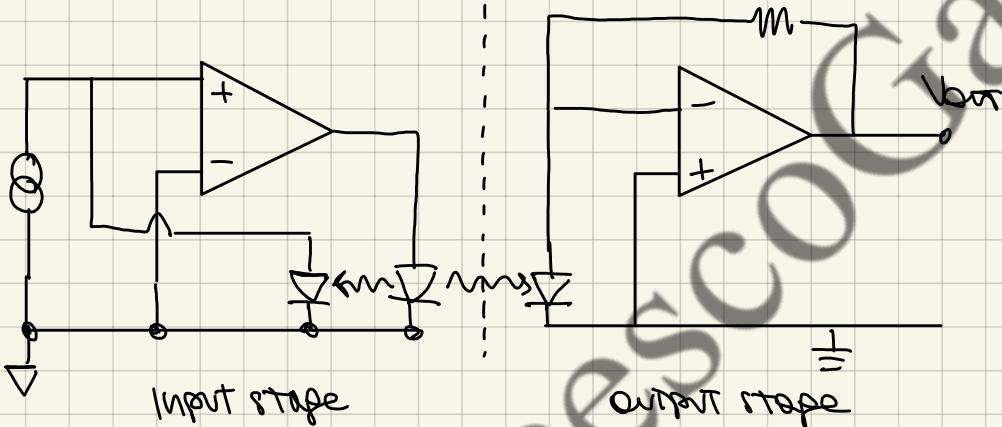


PGA

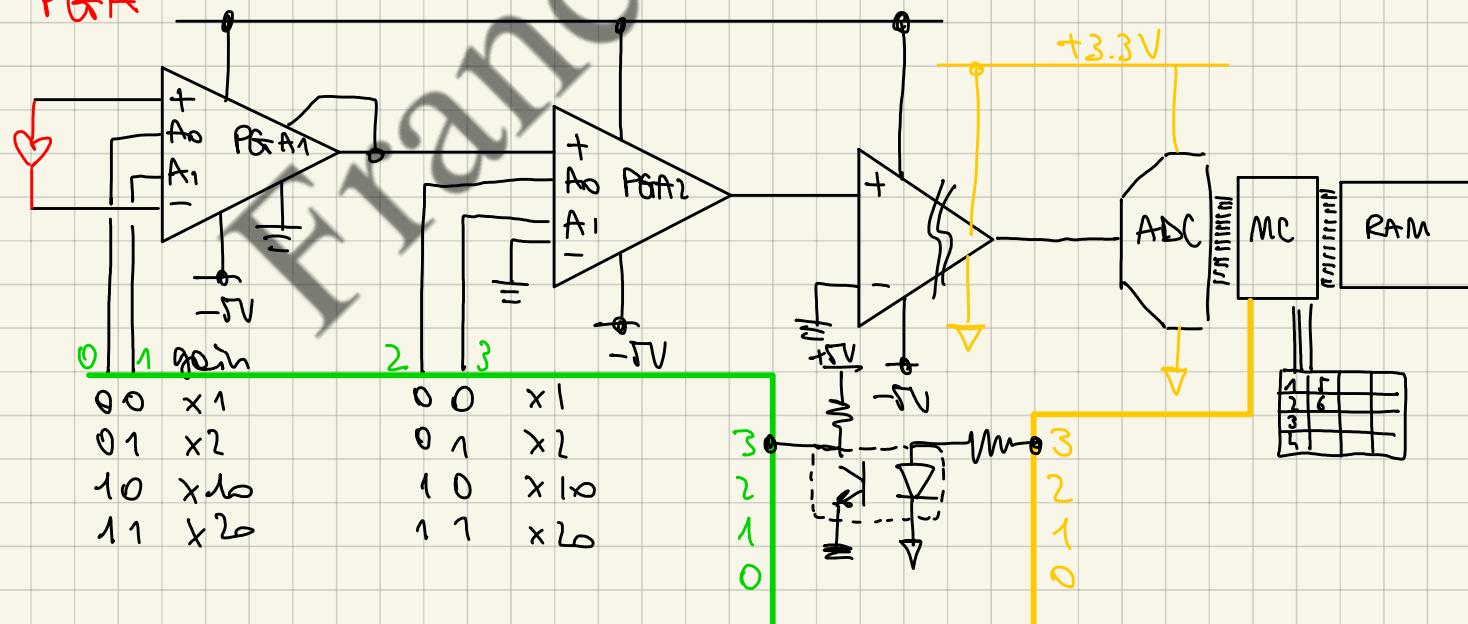



## ② MAGNETIC COUPLING

Transformer:

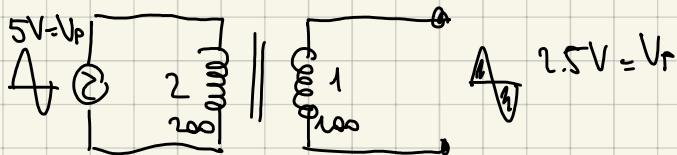

ISSUE: we cannot apply a DC signal

↓  
if we want to apply a DC value we need a kind of MODULATION which transforms the DC value into a variable signal, then it will provide a variable output which will finally be reconverted into a DC value

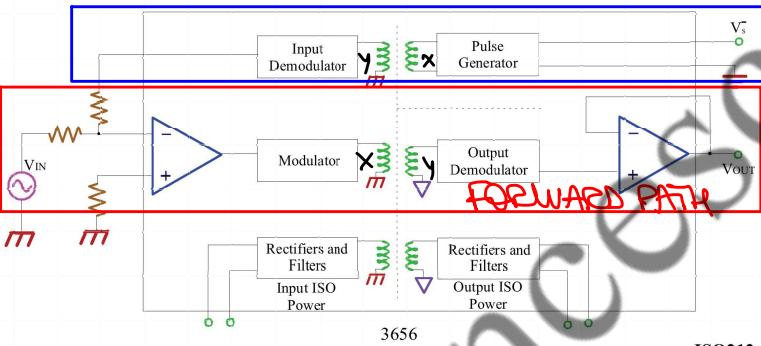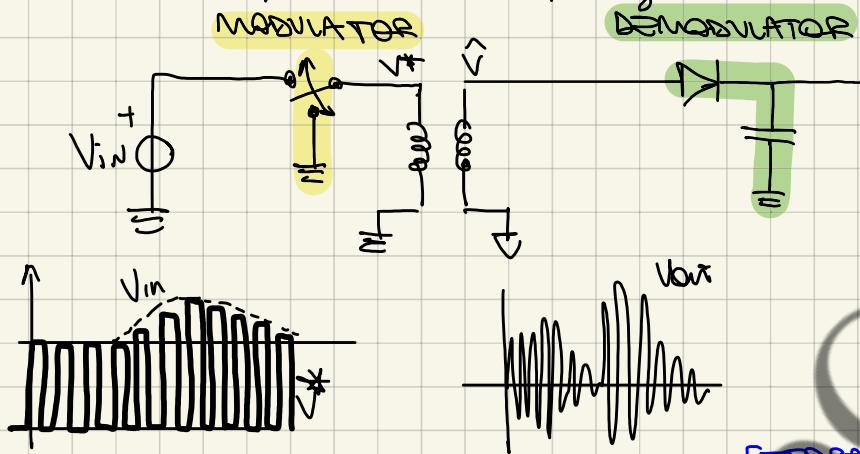

ISO212

**FEEDBACK PATH** → it sense the output signal and brings it back to the input through another modulator and another demodulator

↓

The input demand of the FB path is identical to the output demand of the forward path

Even the transformers must be identical


If these conditions are verified the FB path and the forth one compensate each other and eventually any mismatch will be cancelled

Obviously we need two dedicated PS: one for the input stage and another for the output one

↓  
to spare components we can use another transformer **How?** **IDK**

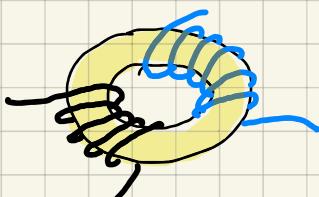**How transformers are made?**


A typical transformer could be based on a TOROID


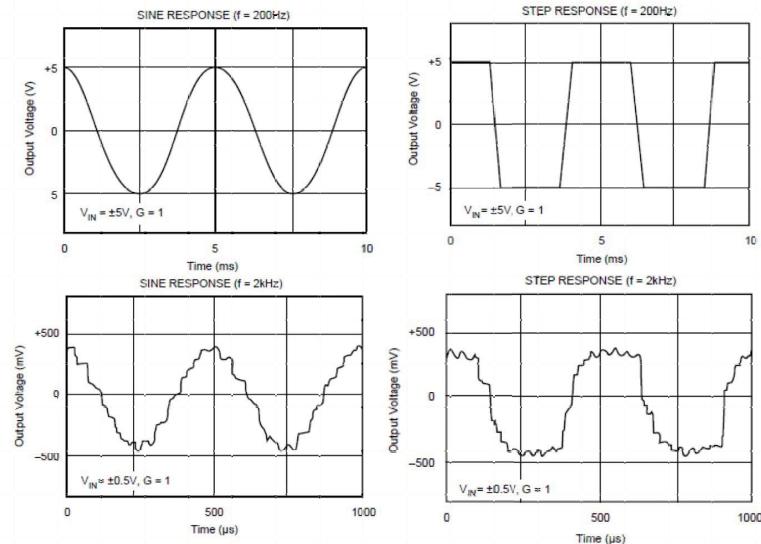
# PROBLEM OF THE ISOLATION AMPLIFIER BASED ON MAGNETIC COUPLING

↓  
we need modulators and demodulators

↓  
this means that we have a fluctuation inside the chip, a RIPPLE



In case of large signal it doesn't appear

But in case of small signals we have residual ripple at the output


↓  
fluctuations in the zero crossings could badly impact the performance of the circuit

→ we should perform a kind of filtering at the output → LPF
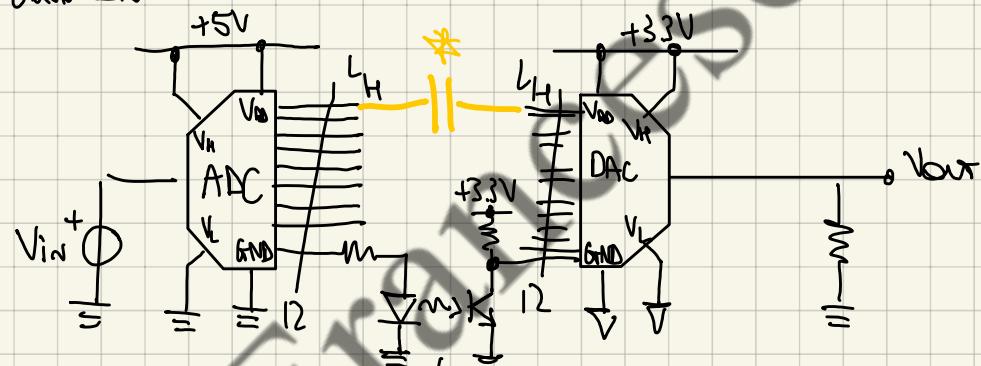
## ③ CAPACITIVE COUPLING

We can transfer information by charging and discharging a capacitor

To do so we can feed an ADC whose output is a digital bus, then this digital bus can be connected to another DAC to bring back the signal in the analog domain







for each bit we have an opto-coupler like this

To connect the two pins we can also use a capacitor \*

if we apply on high level in input we'll have a pitch bit then the output will remain low but there's no DC information that can pass through the capacitor

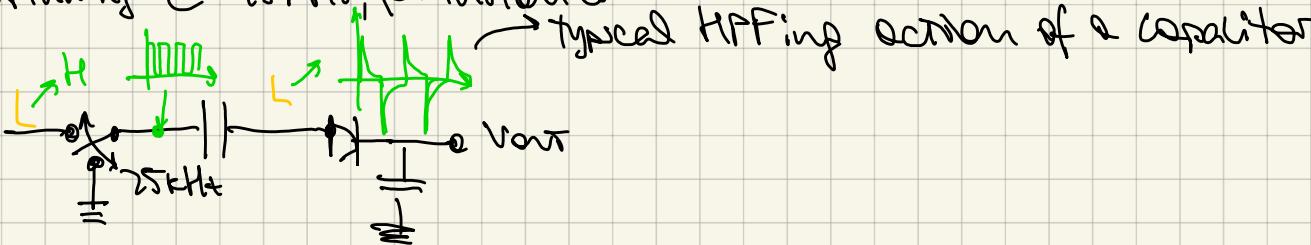→ To pass DC values we need a commutator at the input which keeps switching @ 25kHz, for instance





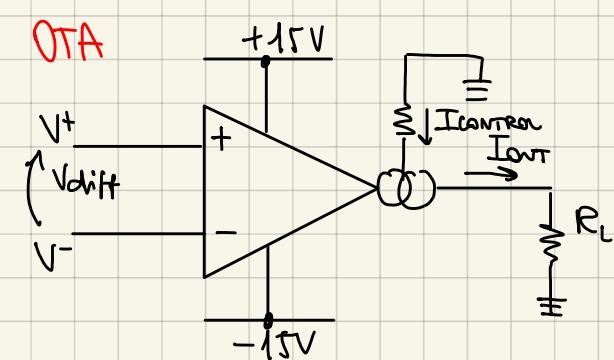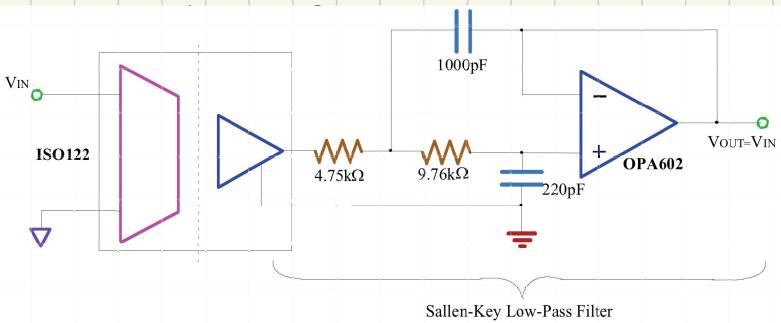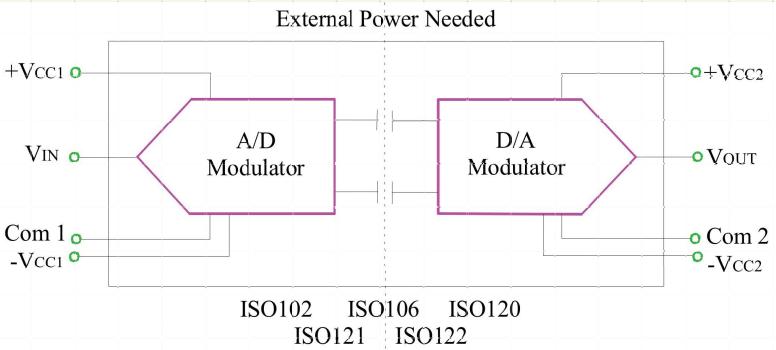

$$I_{out} = g_m(I_{control}) \cdot V_{diff} = \frac{I_{control} \cdot V_{diff}}{2kT/q} = \frac{I_{control} \cdot V_{diff}}{25mV}$$

The output current is linearly related to  $V_{diff}$  in this equation bct we assumed the transconductance to be linear

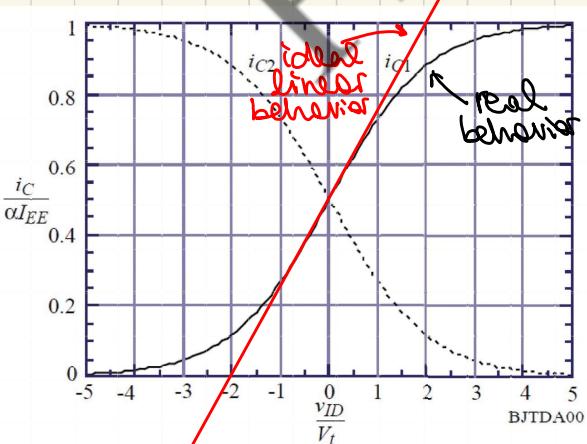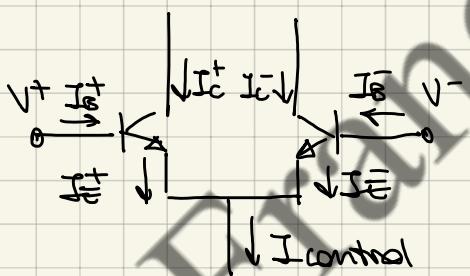But we have seen that the transconductance is not really linear



LINEARIZATION

By varying  $V_{diff}$ , the current flowing through one branch, or the other, goes as the hyperbolic tangent of  $V_{diff}$

$$I_{out} = I_C^+ - I_C^- = I_{control} \tanh\left(\frac{V_{diff}}{2kT/q}\right)$$



So it's not true we can apply whatever  $V_{diff}$  we want

The OTA works linearly if  $V_{diff}$  is in the range of  $V_{th} = kT/q$


$$\text{if } |V_{diff}| \leq V_{th} \Rightarrow \text{LINEAR} \Rightarrow -25mV \leq V_{diff} \leq +25mV$$

if  $V_{diff} \sim 2V_{th}$  → the linear behavior differs a lot from the real one.

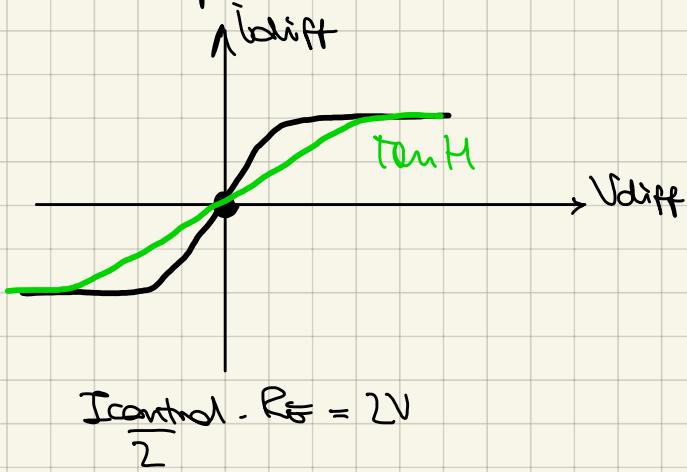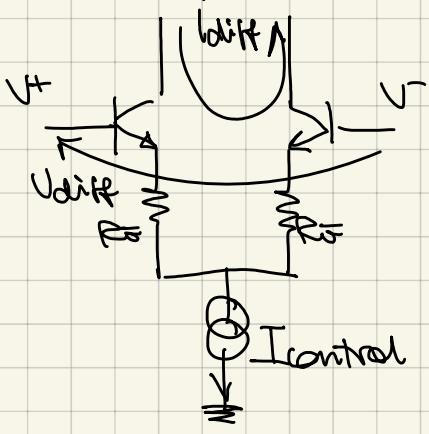In order to improve the linearity we can add 2 resistors in series to the input transistors




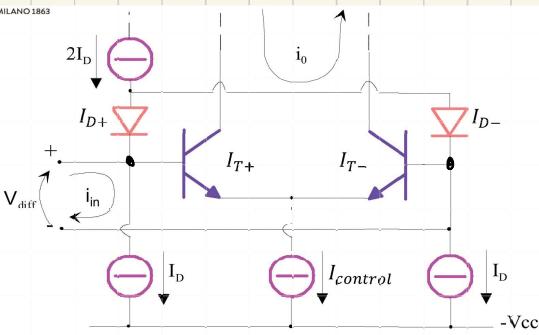Another better solution relies on a loop made by diodes




if The slope is balanced ( $V_{diff} = 0$ )  $\Rightarrow i_m = 0$

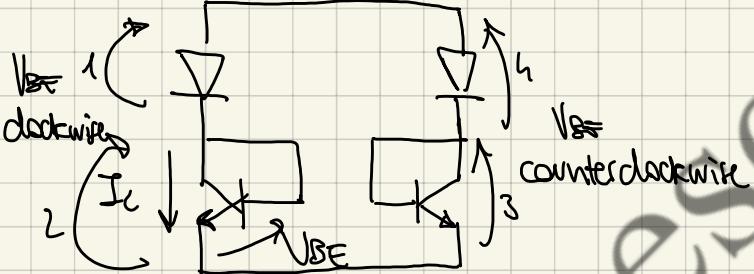if  $V_{diff} \neq 0 \Rightarrow i_m \neq 0$


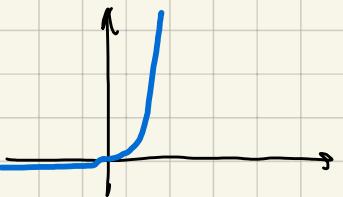
$$\begin{aligned} \frac{kT}{q} \ln\left(\frac{I_{c1}}{I_d}\right) + \frac{kT}{q} \ln\left(\frac{I_{c2}}{I_d}\right) &= \frac{kT}{q} \ln\left(\frac{I_{c3}}{I_d}\right) + \frac{kT}{q} \ln\left(\frac{I_{c4}}{I_d}\right) \\ \sum_i \ln(I_{ci}) &= \sum_j \ln(I_{cj}) \quad \Rightarrow \ln(I_{c1} \cdot I_{c2}) = \ln(I_{c3} \cdot I_{c4}) \end{aligned}$$



$$V_{BE1} + V_{BE2} = V_{BE3} + V_{BE4}$$


$$\cancel{\frac{kT}{q} \ln\left(\frac{I_{c1}}{I_d}\right)} + \cancel{\frac{kT}{q} \ln\left(\frac{I_{c2}}{I_d}\right)} = \cancel{\frac{kT}{q} \ln\left(\frac{I_{c3}}{I_d}\right)} + \cancel{\frac{kT}{q} \ln\left(\frac{I_{c4}}{I_d}\right)}$$

$$\sum_i \ln(I_{ci}) = \sum_j \ln(I_{cj}) \quad \Rightarrow \ln(I_{c1} \cdot I_{c2}) = \ln(I_{c3} \cdot I_{c4})$$

↓

TRANSLINEAR  
PRINCIPLE
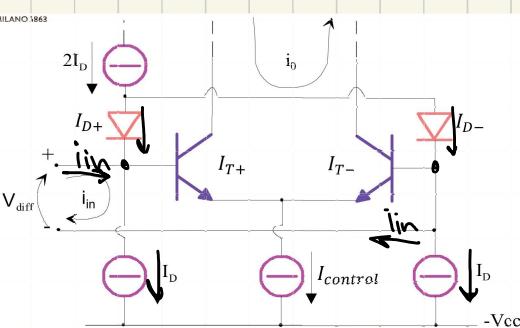
$$\prod_{i \text{ clockwise}} I_{ci} = \prod_{j \text{ counter-clockwise}} I_{cj}$$



$$\Rightarrow I_D^+ \cdot I_T^+ = I_T^- \cdot I_D^-$$

Then let's look at the nodes:



$$I_D^+ - I_D^- - I_{IN} \quad I_D^- = I_D + I_{IN}$$

$$I_{in} = I_D^+ - I_D^- = - (I_D^+ - I_D^-) \Rightarrow I_{in} = I_D^- - I_D^+$$


$$I_{out} = I_T^+ - I_{control} = I_{control} - I_T^-$$

$$I_{out} = I_C^+ - I_C^- = \frac{I_{control}}{I_d} \cdot I_{in} \Rightarrow \text{LINEAR!!!}$$

Everytime we find on OTA like this:

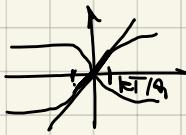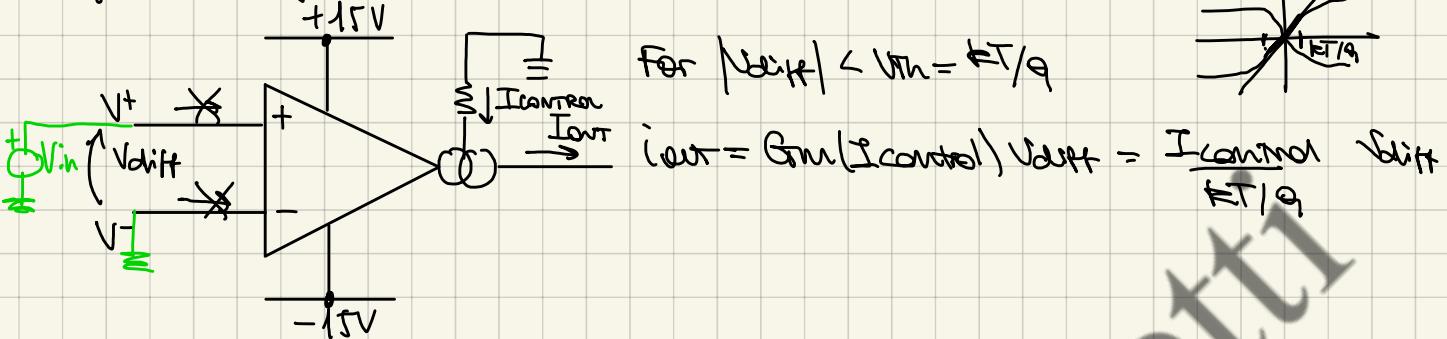


Instead, if we have on OTA like this:

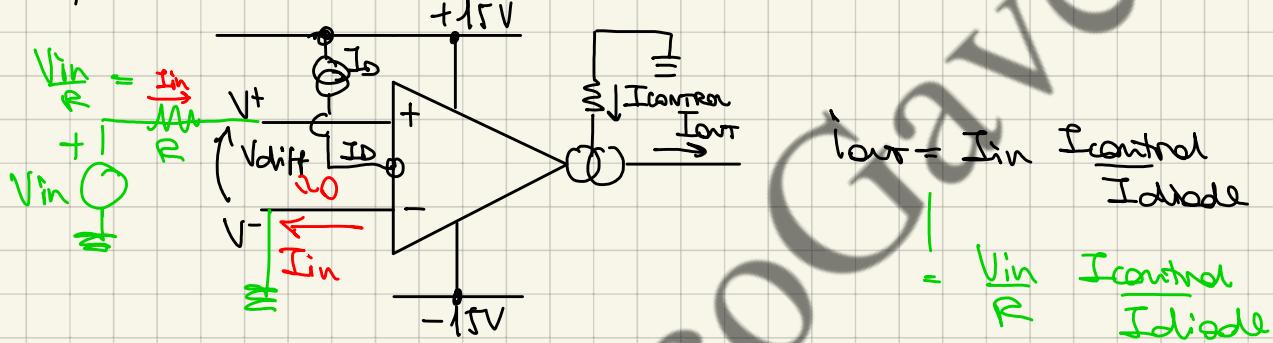

02/11/2021

# INTRODUCTION TO SAMPLING

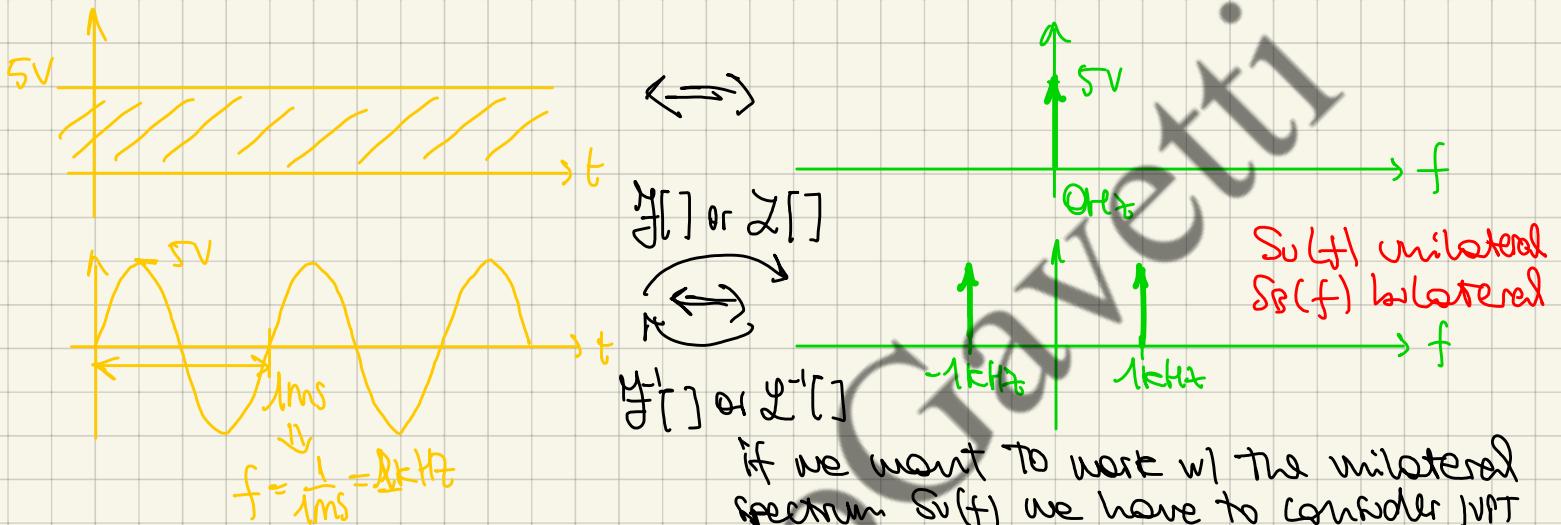


If we want to work w/ the unilateral spectrum  $S_U(f)$  we have to consider JVF one delta @ 1kHz w/ TU amplitude.

If we want to work w/ The bilateral spectrum instead, we have to consider two sinusoids respectively @  $1\text{kHz}$  and  $-1\text{kHz}$  w/ amplitude  $5/2 = 7.5\text{V}$



train of  $S(t)$

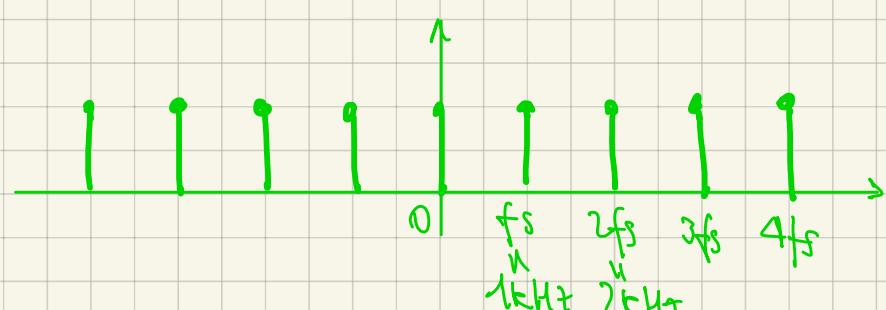


Notice : if  $T_s = 1 \mu s \Rightarrow f_s = 1 MHz$

$\Rightarrow$  if in the time domain the deltas are very close to each other, they will be very spread in frequency (and vice versa)

if  $T \rightarrow \infty \Rightarrow f_S = \frac{1}{T} \rightarrow 0 \Rightarrow$  will have a constant distribution in freq.
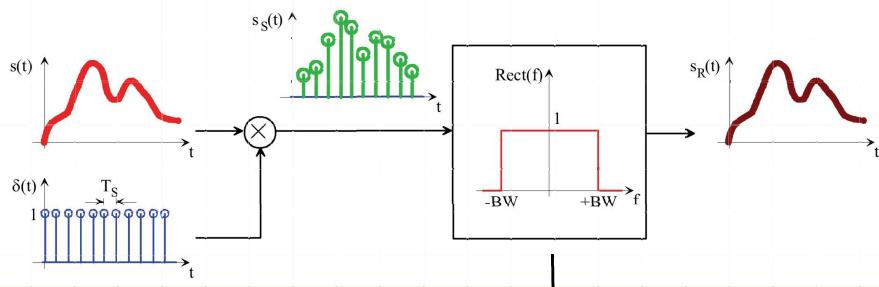
# SAMPLING & THEORY


"if a **function  $s(t)$**  has no frequency components above  $BW$  Hz,  
then it is fully **determined** by its **values**, sampled every  $T_S = \frac{1}{2BW}$ "




The filter will kill all replicas

POLITECNICO MILANO 1863

## Sampling:

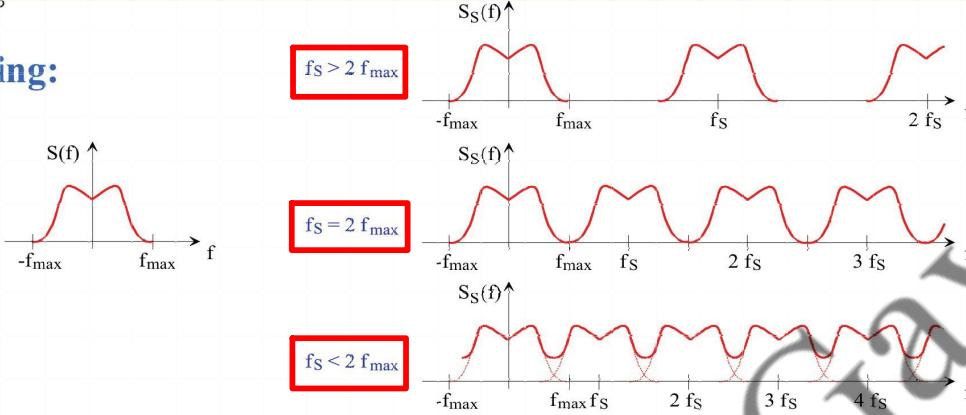


## Reconstruction:

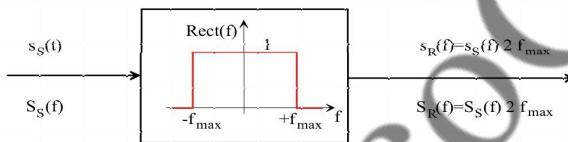

$$f_s > 2f_{\max} \equiv T_S < \frac{1}{2f_{\max}} : \text{OVERSAMPLING}$$

$$f_s = 2f_{\max} \equiv T_S = \frac{1}{2f_{\max}} : \text{SHANNON}$$
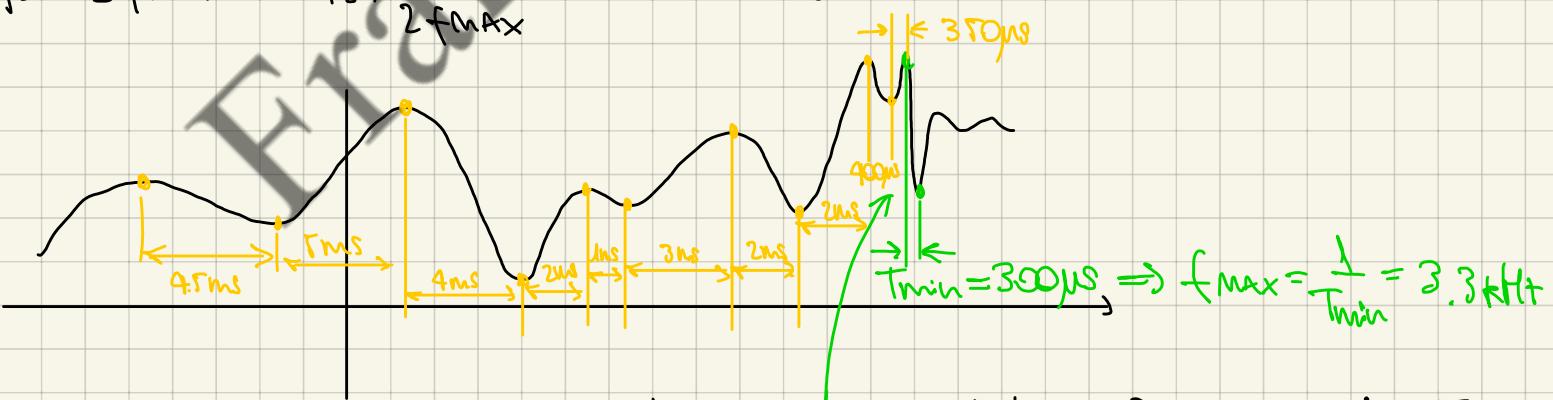
$$f_s < 2f_{\max} \equiv T_S > \frac{1}{2f_{\max}} : \text{UNDERSAMPLING} \rightarrow \text{ISSUE: Aliasing}$$



$$\Rightarrow T_S \leq \frac{T_{\min}}{2} \quad \text{SAMPLING TIME}$$


$$f_s \geq 2f_{\max} = \frac{2}{T_{\min}} \quad \text{SAMPLING FREQUENCY}$$

$f > \frac{f_s}{2}$  ( $f_s < 2f$ )  $\Rightarrow$  Aliasing



↓  
↓  
AVOID!!

Beware: There are also spurious frequency components and if  $f_{spur} > f_s/2$  it will corrupt our signal




## SAMPLING

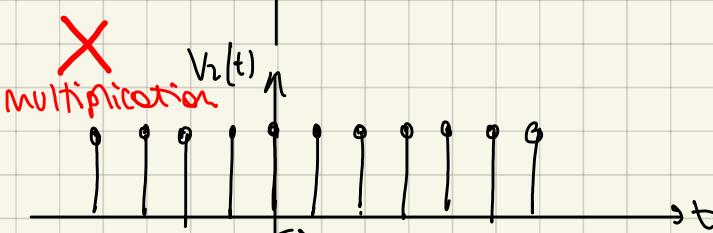

$$= v_i(t) \cdot v_s(t) = v_s(t)$$

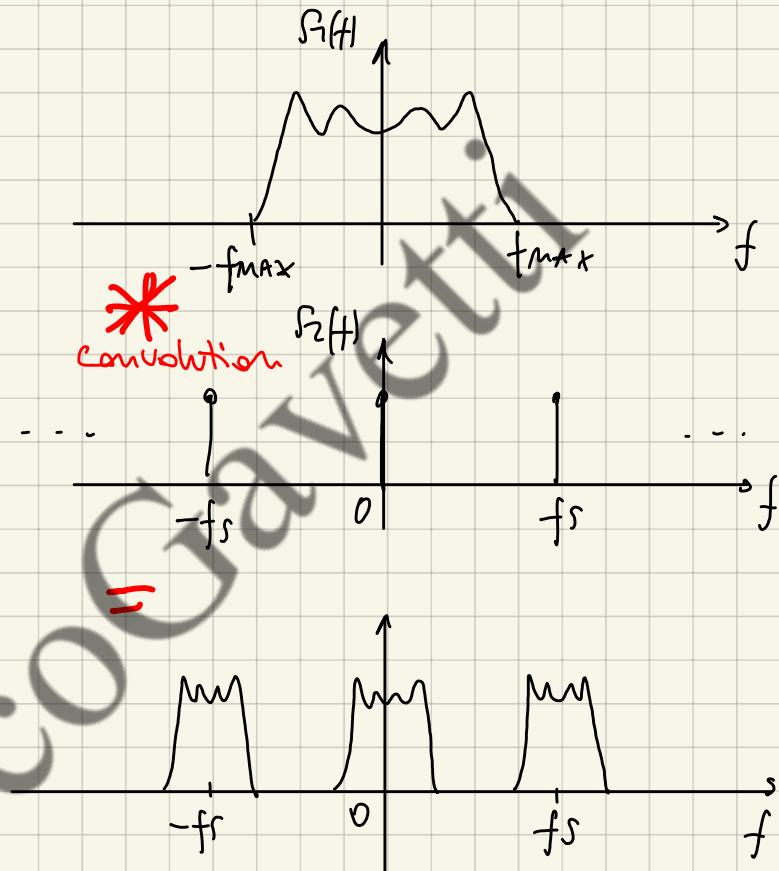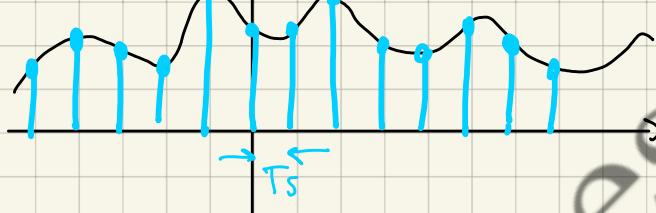


## S&H - SAMPLING AND HOLD

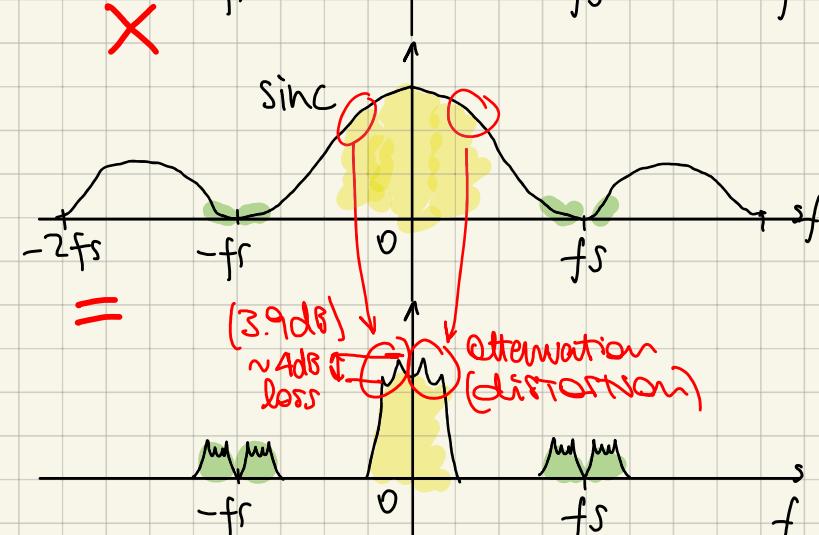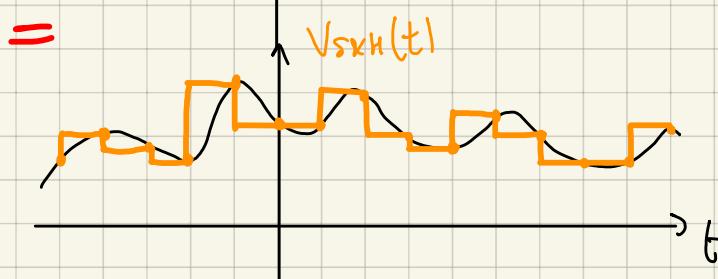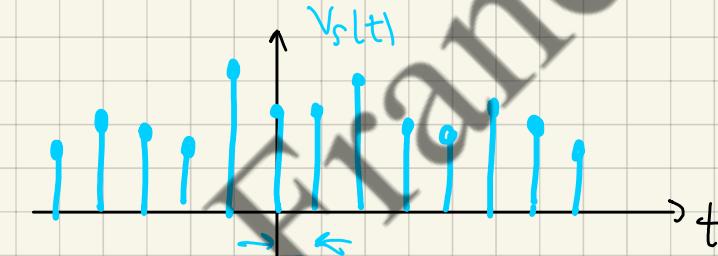

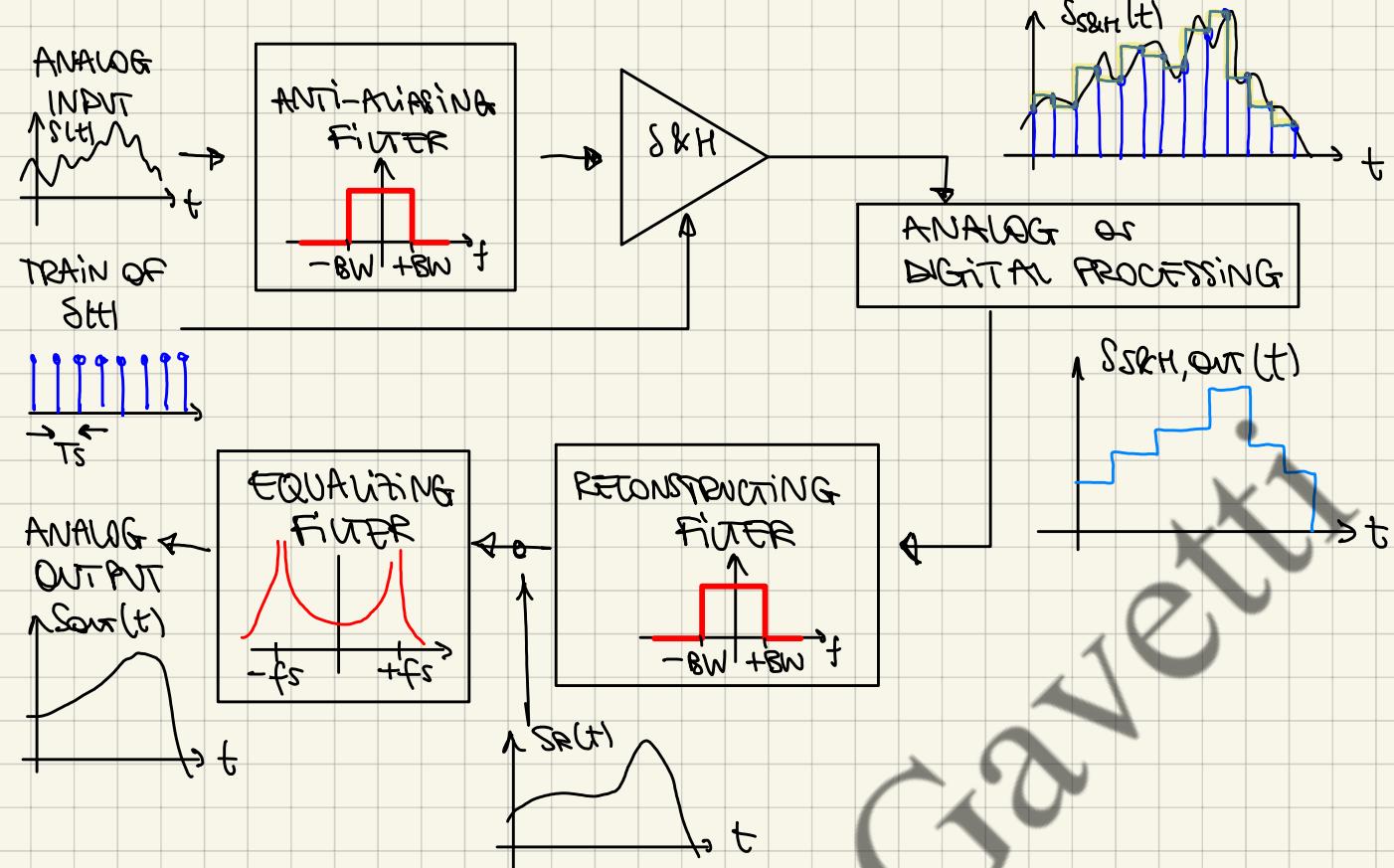
(3.9dB)

To recover the 4dB loss (due to the sinc) we have to use an EQUALIZATION FILTER (to compensate the distortion)




### ANALOG FILTER

We have to kill all the replicas

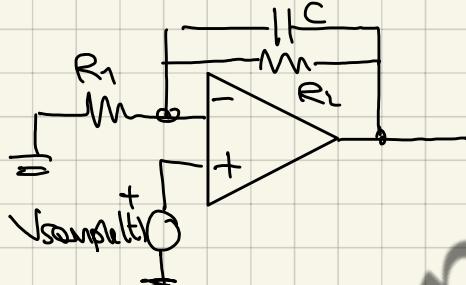

$$\text{pole} = \frac{1}{2\pi C R_2}$$

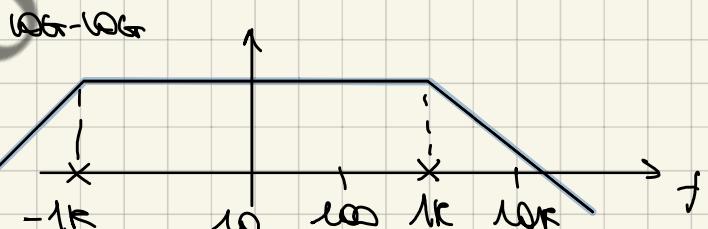



The amplitude of the filter at the pole freq ( $1KHz$ ) is  $1/\sqrt{2}$  compared to the max height

A LPF like that in the LIN-LIN PLOT is not a 1st order LPF!!!


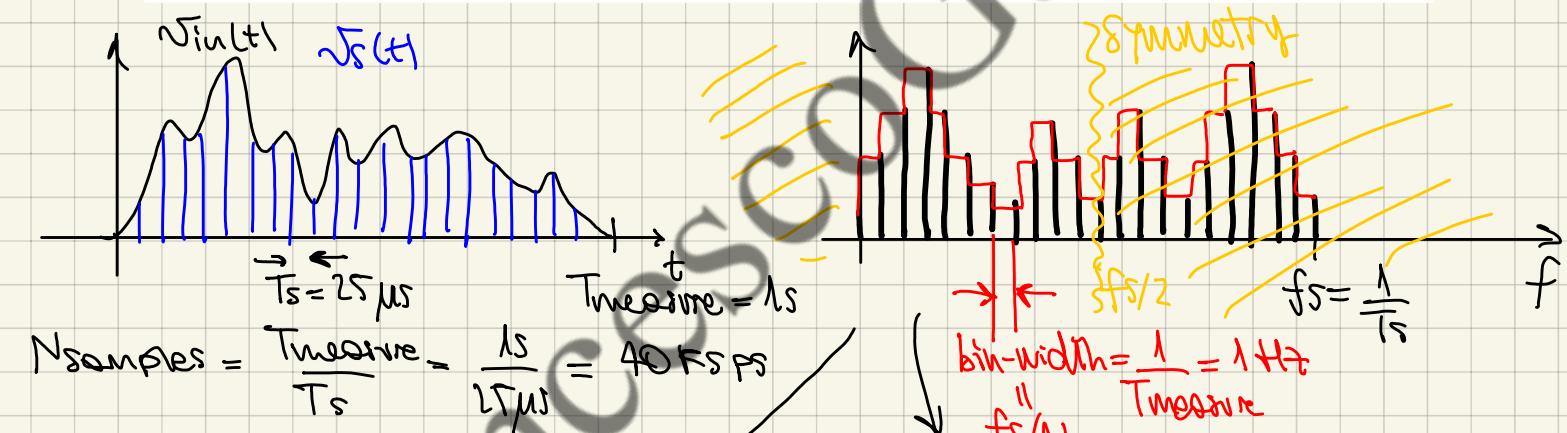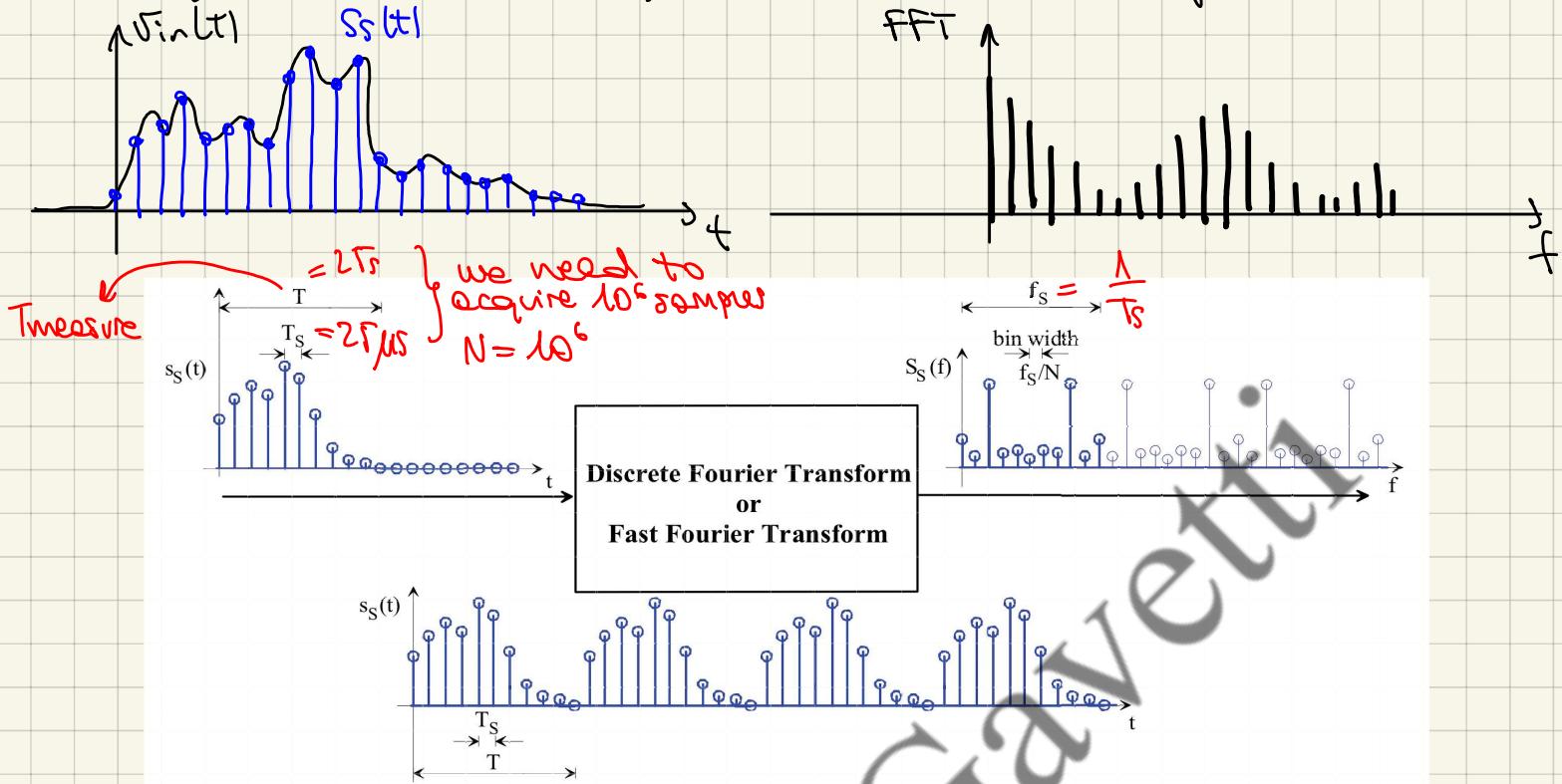
# HOW TO COMPUTE THE SPECTRUM (FFT)

A FFT (FAST FOURIER TRANSFORM) is a mathematical algorithm where:



$$N_{samples} = \frac{T_{measure}}{T_s} = \frac{1s}{2\mu s} = 40 \text{ ksp}$$


We have  $N$  samples also in the freq domain ( $\Delta f$  and  $f_s$ )

$$N = \frac{f_s}{\text{bin-width}} = \frac{1/T_s}{1/T_{measure}} = \frac{1}{T_s} T_{measure} = 40 \text{ ksp}$$

Thanks to the symmetry we can stop to  $f_s/2$  !!.

NOTICE: The FFT algorithm consider the input signal periodic, hence the FFT spectrum is for the periodic version of our input signal and not the original one !!

## ERRORS IN THE FFT

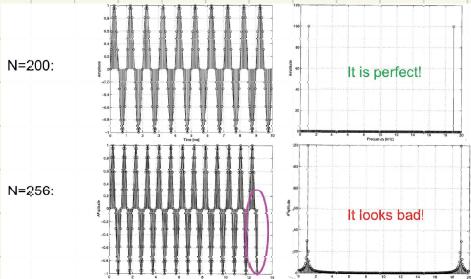

W/  $N = 200$  we have a perfect connection b/w the beginning and the ending of the sequence while w/  $N = 256$  samples (or a number different from an integer number of  $f_s/f_{fin}$ ), the periodic sequence has an abrupt connection

Beware: The problem is that these truncations are not predictable when we have an unknown input signal



"SOLUTION": to alleviate this problem, we can smooth the values of the sequence at the ending of the interval before applying the FFT algorithm



**WINDOWING BEFORE FFT** } To do so we can use the WINDOWING TECHNIQUE according to which the samples' weight becomes less and less as we approach the extreme of the interval



The windowing technique alleviates the problem of the connection and therefore improves the accuracy of the spectrum computed by the FFT

Types of windows:

- RECTANGULAR → not good, it doesn't smooth out external samples at all!  
 $\text{window}(n) = 1$
- TRIANGULAR →  $\text{window}(n) = 1 - \frac{|n|}{M}$  for  $-M \leq n \leq M$  and 0 elsewhere
- HAMMING → ...
- BLACKMAN → ...