

## NOISE AND POWER SPECTRUM

$$x(t) = s(t) + n(t) + d(t)$$


$s(t)$  = signal  
 $n(t)$  = noise  
 $d(t)$  = distortion

Noise is a random process of which we cannot define an instantaneous value. What we can define is the noise distribution.

GAUSSIAN DISTRIBUTION :

$$p(x) = \frac{1}{\sqrt{2\pi}\sigma} e^{-\frac{x^2}{2\sigma^2}}$$

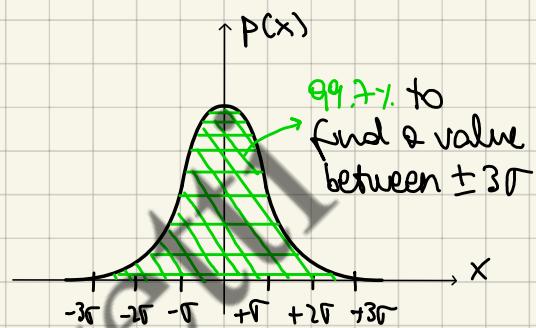where  $\int_{-\infty}^{+\infty} p(x) dx = 1$



noise peak-to-peak value =  $6\sigma$

FULL-WIDTH AT HALF MAXIMUM :  $\text{FWHM} = 2.35 \sqrt{\sigma}$

Since noise is a random process, instantaneous value is nonsense, but it's better measuring power:

NOISE POWER :  $P = \frac{1}{T} \int_0^T |x(t)|^2 dt$

We are looking only for ergodic processes (time average = sample average) and gaussian, w/ nil mean value.

POWER = VARIANCE = MEAN SQUARED VALUE

$$\bar{x}^2 = \langle x^2(t) \rangle = \frac{1}{T} \int_0^T x^2(t) dt = \int_0^\infty S(f) df$$

Where  $S(f)$  = power spectrum / power spectral density

ROOT MEAN SQUARE VALUE (RMS) :  $x_{\text{rms}} = \sqrt{\bar{x}^2} = \sqrt{\sigma}$

measures the width of the Gaussian distribution that describes the noise process

CORRELATION AMONG NOISE SOURCES :

TWO NOISE SOURCES :  $v_t(t) = v_1(t) + v_2(t)$

MEAN TOTAL VALUE :  $\langle v_t(t) \rangle = 0$  (ergodic Gaussian process w/ nil mean value)

TOTAL VARIANCE  $\langle v_t^2(t) \rangle = \langle [v_1(t) + v_2(t)]^2 \rangle = \langle v_1^2(t) \rangle + 2\langle v_1(t)v_2(t) \rangle + \langle v_2^2(t) \rangle$

- in case of no correlation  $\rightarrow \langle v_1(t) \cdot v_2(t) \rangle = 0 \Rightarrow \langle v_t^2(t) \rangle = \langle v_1^2(t) \rangle + \langle v_2^2(t) \rangle$
- in case of total correlation  $\rightarrow v_1(t) = v_2(t) \Rightarrow \langle v_t^2(t) \rangle = 4 \langle v_1^2(t) \rangle$

**How can we say if two sources are correlated or not?**

If we miss the correlation we write an error equal to 100% in terms of power which corresponds to an error of 41% in terms of rms

So let's consider all noise sources as uncorrelated !!

$$\Rightarrow \sigma_{\text{tot}}^2 = \sigma_1^2 + \sigma_2^2 + \sigma_3^2 + \sigma_h^2 + \dots = \sum_i \sigma_i^2 \quad \text{where } i = \text{noise sources}$$


## TYPES OF NOISE

### ① SHOT (GRANULAR) NOISE (or POISSON NOISE)

↓ (quantization)  
it's due to "granularity" of charge flowing through a junction

The current flow is given by the electrons transition, but the electrons pass in a random way, so the current flows is not a perfect sequence of deltas equally separated, but it's a random sequence of them

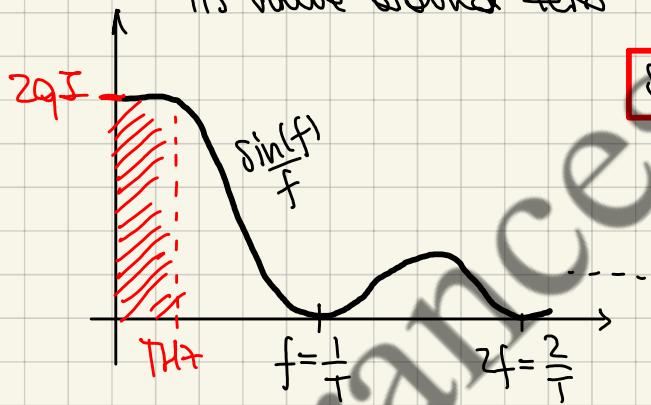↓  
The power spectrum is a kind of sinc function which is almost constant up to very high frequencies ( $\sim THz$ ) for this reason we can approximate it w/ its value around zero



$$S(f) \approx S(0) = 2qI$$

SHOT NOISE POWER SPECTRUM

$$q = 1.6 \cdot 10^{-19} C$$

ELECTRON'S CHARGE

- Notice:
- independent of operating freq  
→ white noise
  - shows up only if there's a current flow

SHOT NOISE POWER (MSV):  $\Gamma^2 = \langle i^2 \rangle = 2qI \cdot \Delta f$

where  $\Delta f$  = BANDWIDTH OF THE INSTRUMENTATION USED TO MEASURE THE NOISE

↳ Beware: it's not the operating frequency  $\rightarrow \Gamma_{\text{shot}}$  is independent of  $f$

REMEMBER:

- if  $I = 50 \mu A \rightarrow \Gamma = 4 \text{ PA}/\sqrt{\text{Hz}}$
- if  $I = 5 \text{ mA} \rightarrow \Gamma = 40 \text{ PA}/\sqrt{\text{Hz}}$

} The rms value increases w/  $\sqrt{I}$

if we increase the current the noise power and rms increase, but also the SNR does

$$\text{SNR} = \frac{I}{\Gamma} = \frac{I}{\sqrt{2q} \cdot \sqrt{I}} = \frac{\sqrt{I}}{\sqrt{2q}} \div \sqrt{I}$$

## ② THERMAL (JOHNSON) NOISE

↓



it's caused by the random thermal motion of electrons within the electronic component

- This random motion doesn't depend on the presence of a DC current
- The rms value depends on the squared root of the temperature  $\sqrt{T}$  and of the resistive value  $\frac{1}{R}$
- It's independent of frequency → white noise 

**THERMAL NOISE POWER:**  $\text{V}_v^2 = \langle v^2 \rangle = 4kT R \Delta f$

$$\text{or } \text{V}_i^2 = \langle i^2 \rangle = \frac{4kT \Delta f}{R}$$

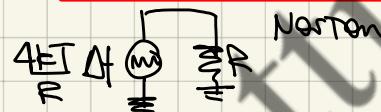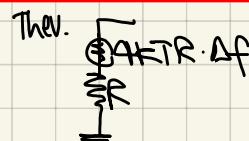where  $4kT = 1.66 \cdot 10^{-20} \frac{\text{V}^2}{\text{K}^2 \Omega}$



**THERMAL NOISE RMS:**


$$\text{V}_v = \sqrt{4kT R \Delta f}$$

$$\text{or } \text{V}_i = \sqrt{\frac{4kT}{R} \Delta f}$$

REMEMBER: • if  $R = 1\text{k}\Omega \rightarrow \text{V} = 4\text{nV}/\sqrt{\text{Hz}}$

• if  $R = 100\text{k}\Omega \rightarrow \text{V} = 40\text{nV}/\sqrt{\text{Hz}}$

## ③ FLICKER ( $1/f$ ) NOISE

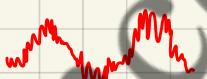- It's proportional to the current flow
- The power spectrum depends on  $1/f$
- It's a colored noise  (pink noise) → higher @ low freq, and lower @ HF

$1/f$  NOISE POWER

$$\text{V}_i^2 = \langle i^2 \rangle = k \frac{I^2}{f^b} \Delta f$$

• constant power for each decade:  $P = \int_{f_1}^{f_2} \frac{kI}{f} df = kI \ln\left(\frac{f_2}{f_1}\right)$

if we consider 1 decade ( $f_2 = 10f_1$ ) →  $\text{P}_{\text{one decade}} = kI \ln(10) = kI \cdot 2.3$

• from a mathematical stand point flicker noise diverges @ 0 Hz, but in reality it doesn't

$$f_{\text{real lower}} = \frac{1}{24 \text{h} \cdot 60 \text{min} \cdot 60 \text{sec}} \approx 10^{-7} \text{Hz} \neq \infty$$

• it's comparable to white noise @ noise corner frequency


## ④ BURST (POP-CORN) NOISE

 → it's no more Gaussian

BURST NOISE POWER

$$\sigma^2 = \langle i^2 \rangle = k_b \frac{I^c}{1 + \left(\frac{f}{f_c}\right)^2} \Delta f$$
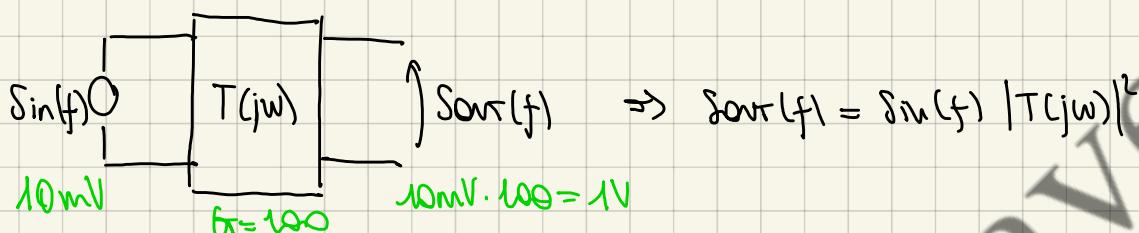
## NOISE IN-OUT TRANSFER (FREQUENCY RESPONSE)




For noise only "power" transfer (modulus) matters (independent of phase):

Input noise:




Output noise:

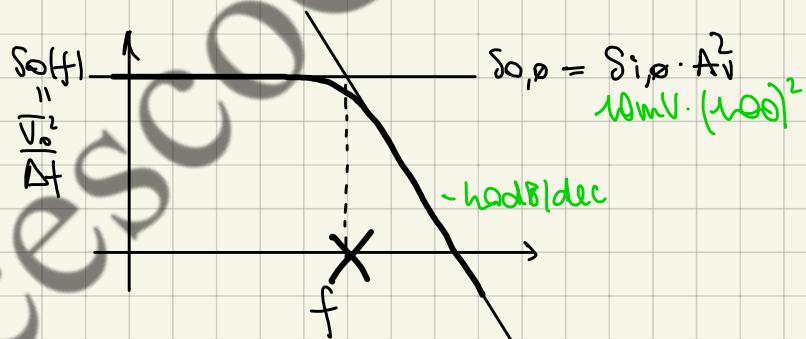

TOTAL OUTPUT NOISE POWER:

$$\langle v_o^2 \rangle = \int_0^\infty S_o(f) df = \int_0^\infty |A_v(f)| \cdot S_{i,\infty} df = S_{i,\infty} \int_0^\infty |A_v(f)|^2 df$$


## NOISE EQUIVALENT BANDWIDTH

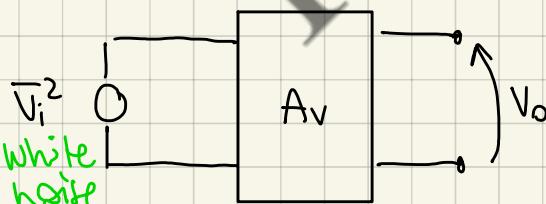

$$\langle v_o^2 \rangle = S_{i,\infty} \cdot A_{v,\infty}^2 f_N$$

↓ constant

where  $f_N = \Delta f$  to consider

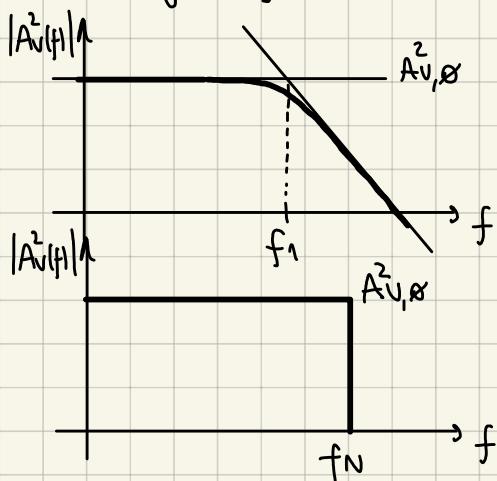


NOISE EQUIVALENT BANDWIDTH:  $f_N = \frac{1}{A_{v,\infty}^2} \int_0^\infty |A_v(f)|^2 df$

SIMPLE CASES:

- 1 pole:  $f_N = \frac{\pi}{2} f_1 = 1.57 f_1$

- 2 poles:  $f_N = 1.22 f_1$


example:

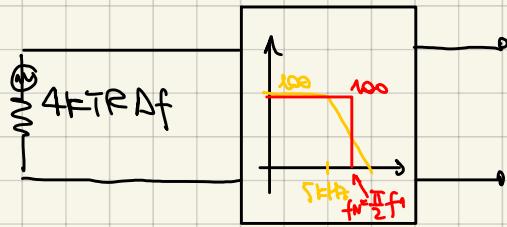

$$\text{V}_{\text{out}}^2 = \underbrace{4\text{kT}}_{S_i, \infty} \cdot \underbrace{\left( \frac{1}{2} \text{kH} \cdot \frac{\pi}{2} \right)}_{f_N} \cdot \underbrace{100}_{A_V, \infty}$$

"WEIRD" RESULT

simple RC network

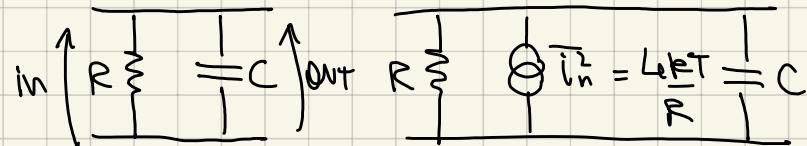

• Full computation:

$$T(j\omega) = R \parallel C = \frac{R \parallel C}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega RC}$$

$$\Rightarrow S_0(f) = \frac{4kT}{R} |T(j\omega)|^2 = \frac{4kT}{R} \frac{R^2}{1 + \omega^2 C^2 R^2}$$

$$\langle V_{\text{out}}^2 \rangle = \int_0^\infty S_0(f) df = \frac{4kT}{R} \int_0^\infty \frac{R^2}{1 + \omega^2 C^2 R^2} df = \dots = \frac{kT}{C}$$

• Equivalent computation:

$$\langle V_{\text{out}}^2 \rangle = \frac{4kT}{R} \cdot R^2 \underbrace{\frac{\pi}{2}}_{\downarrow} \underbrace{\frac{1}{2\pi RC}}_{\text{C}} = \frac{kT}{C} \rightarrow \text{the output noise power doesn't depend on the resistor but just on the capacitor}$$

$$|G^2(j\omega)| \underbrace{f_1}_{\text{f}_N = \Delta f} \Rightarrow \sigma = \sqrt{\frac{kT}{C}}$$

## NOISE EQUIVALENT GENERATORS


Since every active electronic component introduces its own sources of noise (white and hot), when dealing w/ complex circuits it's often useful to model the noise of each single sub-circuit w/ a couple of "equivalent" noise generators:

- one modelling current noise sources
- one for voltage ones


## REAL CIRCUIT



## EQUIVALENT CIRCUIT

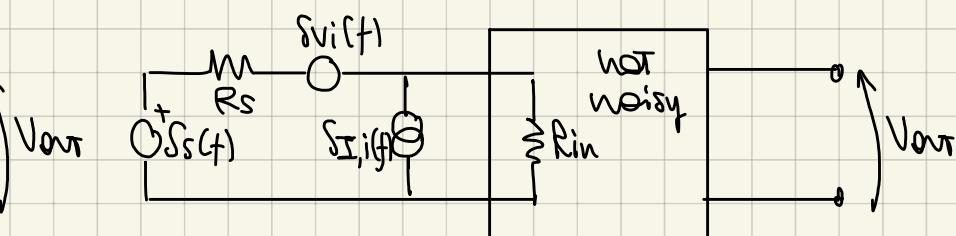


Example:

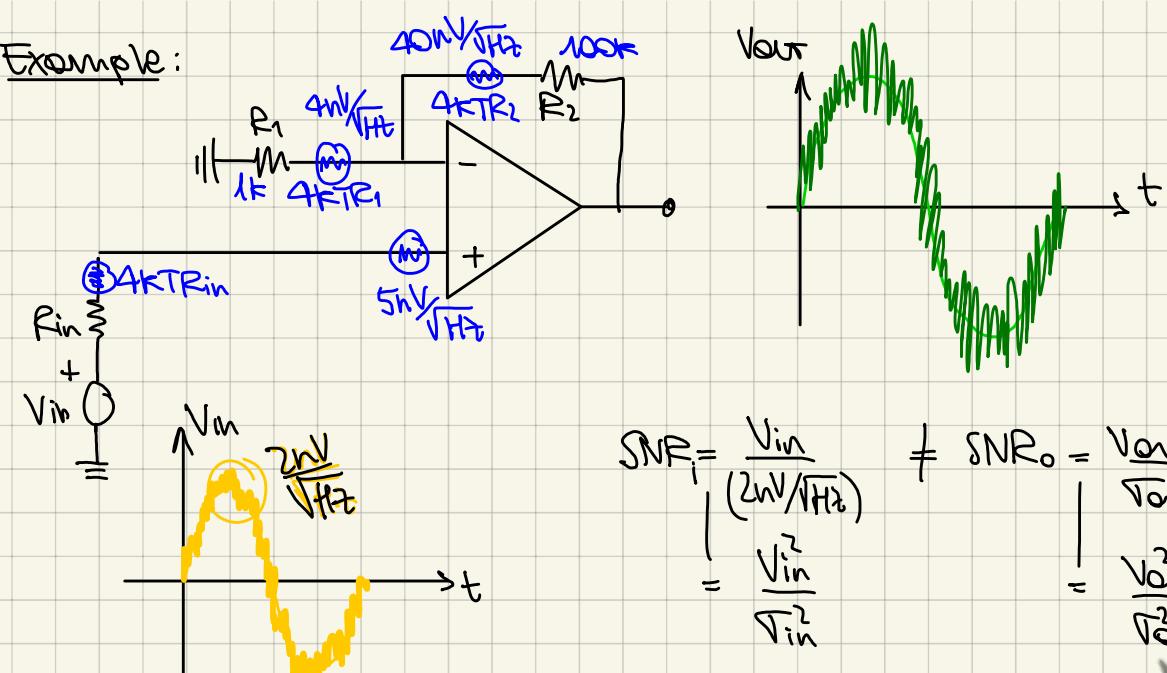


NOISE FIGURE (FACTOR)

$$NF = \frac{SNR_i}{SNR_o} \geq 1 \quad (\text{ideally } NF=1)$$

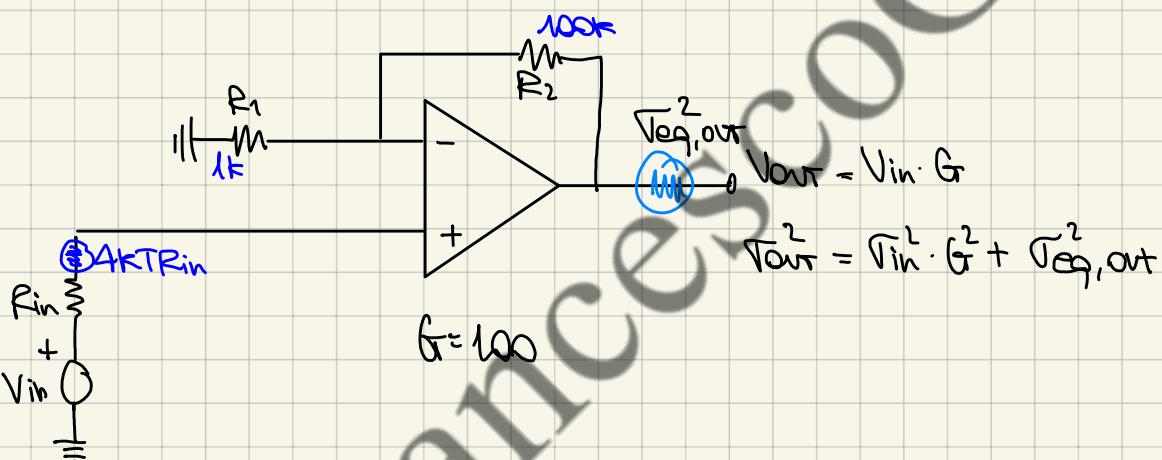let's compute the total effect of the noise sources @ the output:



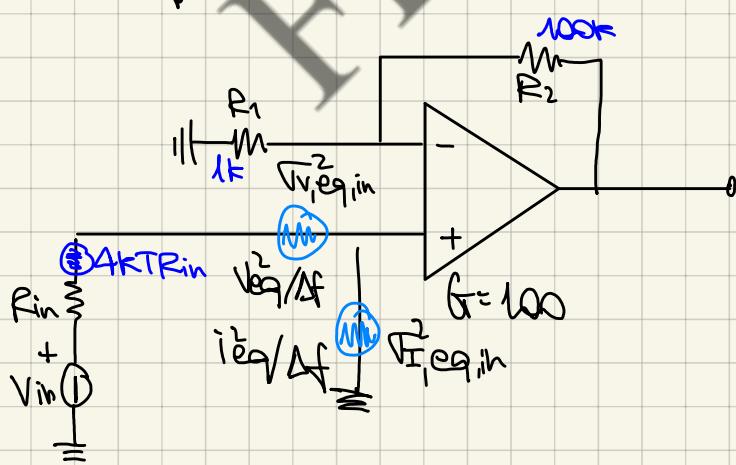Now we want to bring the noise generators @ the input





$$V_{in,eq}^2 = 4\text{KTR}_s \Delta f + \frac{V_b^2}{4f} \cdot \Delta f + \frac{i_b^2}{4f} \cdot R_s \Delta f \quad \text{TOTAL INPUT REFERRED NOISE POWER}$$

## NOISE FIGURE (FACTOR)

$$NF = 10 \cdot \log_{10} \left[ \frac{\text{total input noise}}{\text{only the source noise}} \right]$$

$$\begin{aligned} NF &= 10 \log_{10} \left[ \frac{4kT R_s + V_{eq}^2 + i_{eq}^2 \cdot R_s^2}{4kT R_s} \right] = \\ &= 10 \log_{10} \left[ 1 + \frac{V_{eq}^2}{4kT R_s} + \frac{i_{eq}^2}{4kT / R_s} \right] \geq 0 \text{dB } (1) \end{aligned}$$
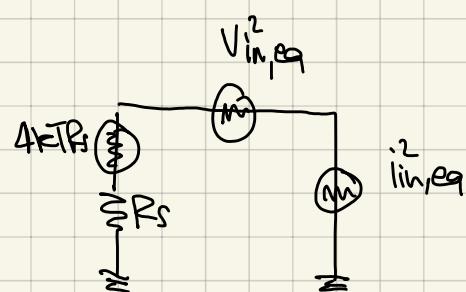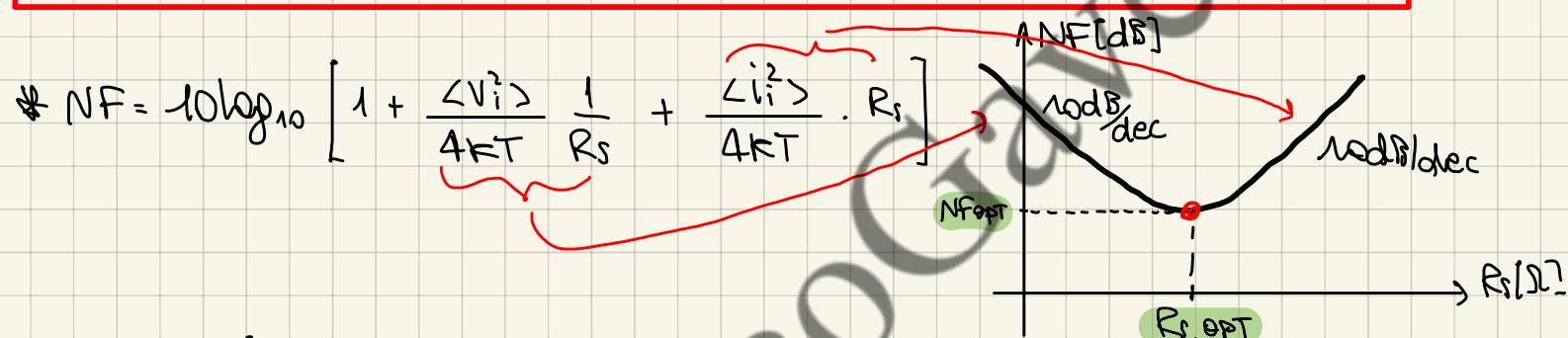
$$\begin{aligned} NF &= \frac{SNR_i}{SNR_o} - \frac{\delta_i}{N_i} \cdot \frac{N_o}{S_o} = \frac{S_i}{N_i} \cdot \frac{N_o}{G S_i} = \frac{N_o}{G N_i} = \frac{\text{total output noise}}{\text{total output noise just due to } R_s} = \\ &= \frac{\text{Total input noise}}{4kT R_s} \end{aligned}$$



$$NF = 10 \log_{10} \left( 1 + \frac{V_{in,eq}^2}{4kTR_s} + \frac{i_{in,eq}^2}{4kTR_s} \cdot R_s^2 \right)$$


## OPTIMUM SOURCE RESISTANCE

$$\frac{V_{in,eq}^2}{4kTR_{s,opt}} = \frac{i_{in,eq}^2}{4kT} R_{s,opt}$$

$$R_{s,opt} = \sqrt{\frac{V_{in,eq}^2 / \Delta f}{i_{in,eq}^2 / \Delta f}}$$

$$V_{rms, \text{sinewoid}} = \frac{V_p}{\sqrt{2}}$$

EQUIVALENT CIRCUIT:

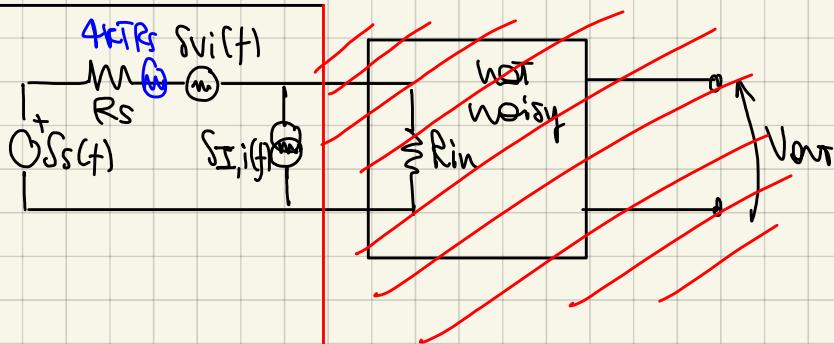





TOTAL INPUT REFERRED NOISE:  $S_{in}(f) = 4kT R_s + e_v^2 + i_{in}^2 \cdot R_s^2$   
(no  $R_{in}$ )

TOTAL OUTPUT NOISE:  $S_{out}(f) = |T(j\omega)|^2 \cdot \left\{ S_v(f) \cdot \frac{R_{in}^2}{(R_s + R_{in})^2} + S_i(f) \cdot \frac{R_{in}^2 R_s^2}{(R_s + R_{in})^2} \right\}$


There's no need to compute output noise... let's stop @ The input!

TOTAL INPUT NOISE
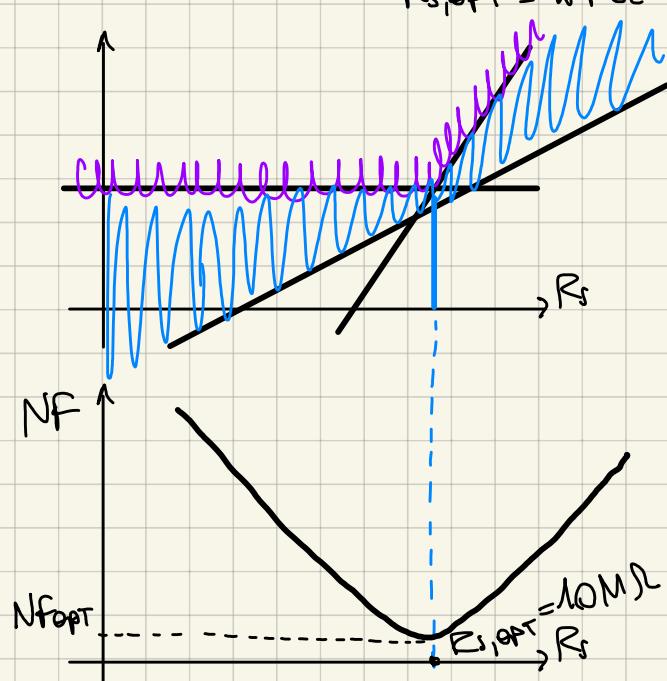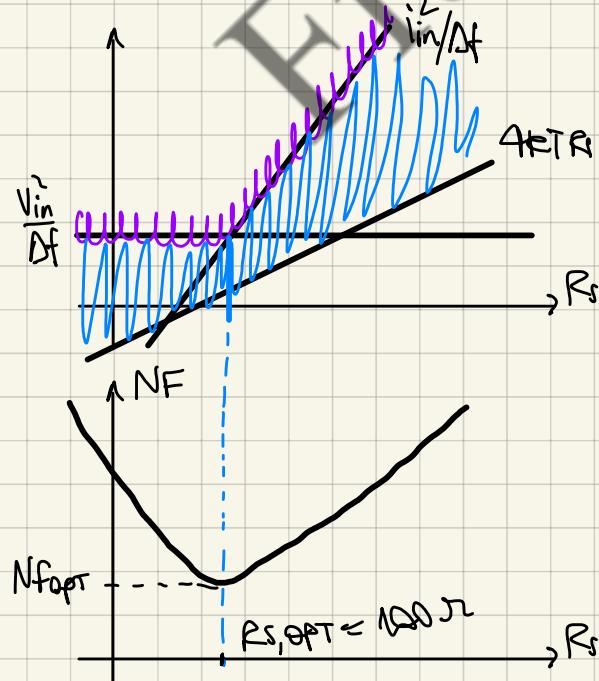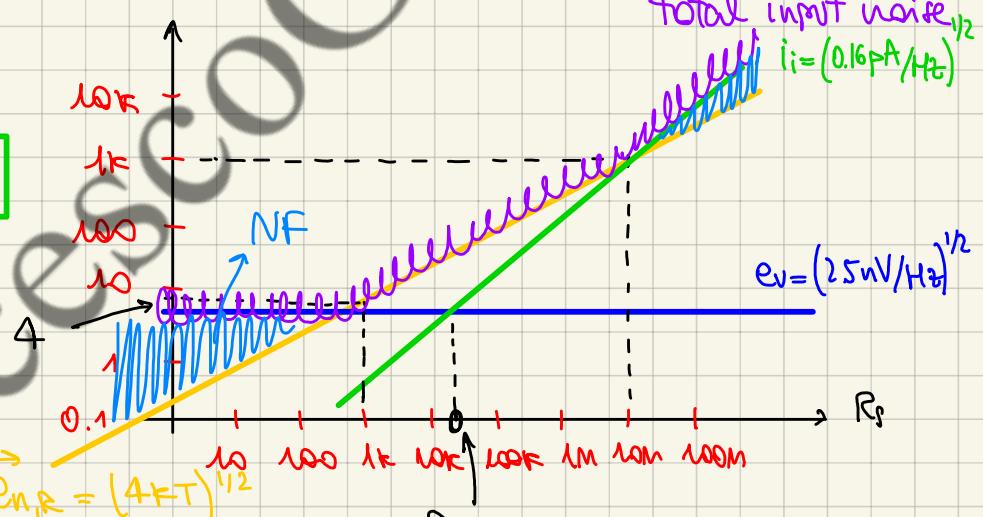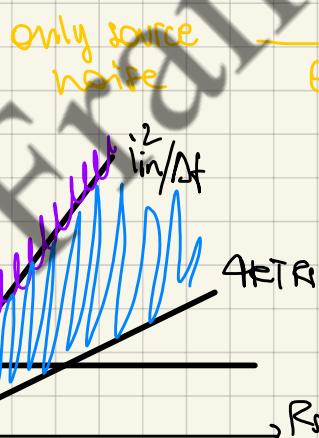
$$\underline{S_{in}(f)} = \boxed{4kT R_s} + \boxed{e_v^2} + \boxed{i_{in}^2 \cdot R_s^2}$$



# EXAMPLE 1

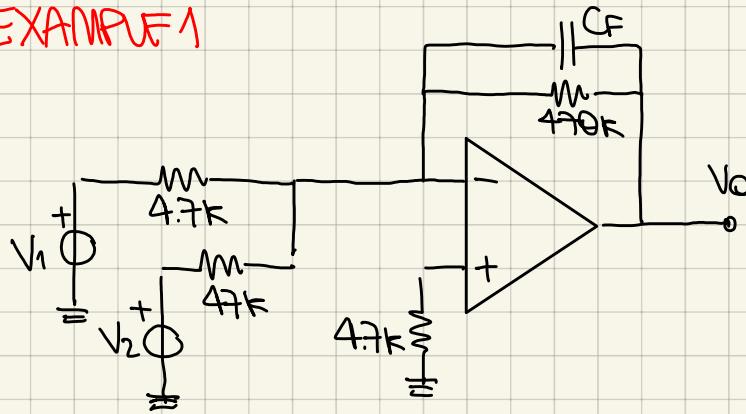


$$\frac{V_{in}^2}{\Delta f} = (8.9 \text{nV}/\sqrt{\text{Hz}})^2$$

$$\frac{i_{in}^2}{\Delta f} = (0.5 \text{ pA}/\sqrt{\text{Hz}})^2$$

$$CF = 1 \text{nF}$$

OpAmp ideal

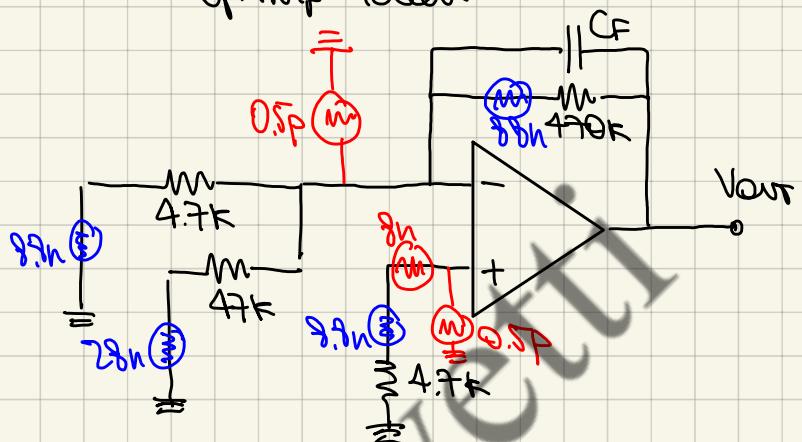


- Switch off the signal generators
- Draw all the noise generators

$$4FT \cdot 4.7 \text{k}\Omega = 1.66 \cdot 10^{-20} \cdot 4.7 \text{k}\Omega = (8.9 \text{nV}/\sqrt{\text{Hz}})^2$$

$$4FT \cdot 47 \text{k}\Omega = (8.9 \text{nV}/\sqrt{\text{Hz}})^2 \cdot \sqrt{10} \approx (28 \text{nV}/\sqrt{\text{Hz}})^2$$
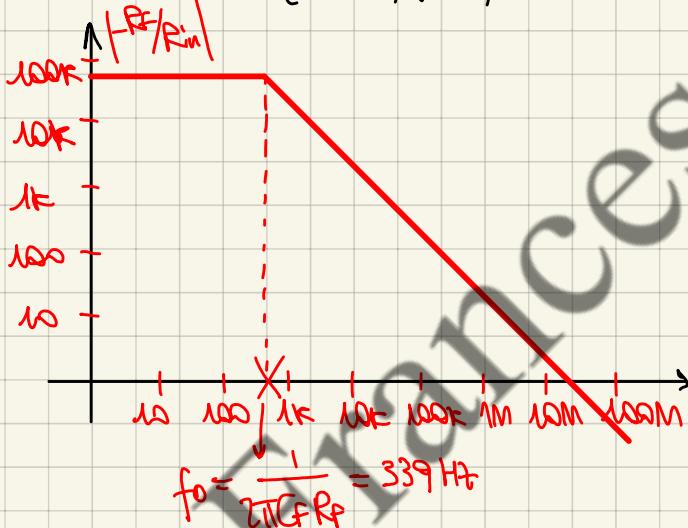
$$4FT \cdot 470 \text{k}\Omega = (8.9 \text{nV}/\sqrt{\text{Hz}})^2 \cdot \sqrt{100} \approx (89 \text{nV}/\sqrt{\text{Hz}})^2$$



$$NEBW = \frac{\pi}{2} f_0 = \frac{\pi}{2} 339 \text{Hz} \approx 532 \text{Hz}$$

$$\begin{aligned} \left( \frac{V_{in}}{\sqrt{\text{Hz}}} \right)^2 &= (8.9 \text{nV}/\sqrt{\text{Hz}})^2 \cdot \left( -\frac{470 \text{k}\Omega}{4.7 \text{k}\Omega} \right)^2 + (28 \text{nV}/\sqrt{\text{Hz}})^2 \cdot \left( -\frac{470 \text{k}\Omega}{4.7 \text{k}\Omega} \right)^2 + (89 \text{nV}/\sqrt{\text{Hz}})^2 \cdot (1)^2 + \\ &+ \left[ \left( 8.9 \text{nV}/\sqrt{\text{Hz}} \right)^2 + (9 \text{nV}/\sqrt{\text{Hz}})^2 \right]^2 \cdot \left( 1 + \frac{470 \text{k}\Omega}{4.7 \text{k}\Omega \cdot 47 \text{k}\Omega} \right)^2 + \\ &+ (0.5 \text{ pA}/\sqrt{\text{Hz}})^2 \cdot (4.7 \text{k}\Omega)^2 \cdot \left( 1 + \frac{470 \text{k}\Omega}{4.7 \text{k}\Omega \cdot 47 \text{k}\Omega} \right)^2 + (0.5 \text{ pA}/\sqrt{\text{Hz}})^2 \cdot (470 \text{k}\Omega)^2 \\ &= (8.9 \text{n} \cdot 100)^2 + (28 \text{n} \cdot 10)^2 + (89 \text{n})^2 + (11.9 \text{n} \cdot 100)^2 + (0.5 \text{ p})^2 \cdot (4.7 \text{k})^2 \cdot (100)^2 + (470 \text{k})^2 \\ &= (890 \text{n})^2 + (280 \text{n})^2 + (89 \text{n})^2 + (1.3 \mu)^2 + (255 \text{n})^2 + (135 \text{n})^2 \end{aligned}$$


$$\begin{aligned} \left( \frac{V_{in}}{\sqrt{\text{Hz}}} \right)^2 &= (8.9 \text{n} \cdot 100)^2 + (28 \text{n} \cdot 10)^2 + (89 \text{n})^2 + (11.9 \text{n} \cdot 100)^2 + (0.5 \text{ p})^2 \cdot (4.7 \text{k})^2 \cdot (100)^2 + (470 \text{k})^2 \\ &= (890 \text{n})^2 + (280 \text{n})^2 + (89 \text{n})^2 + (1.3 \mu)^2 + (255 \text{n})^2 + (135 \text{n})^2 \end{aligned}$$

$$\stackrel{!}{=} (1.63 \mu\text{V}/\sqrt{\text{Hz}})^2$$

$$V_{\text{out}, \text{nm}} = \sqrt{(1.63 \mu\text{V}/\sqrt{\text{Hz}})^2 \cdot \Delta f} = \sqrt{V_{\text{out}}^2} = (1.63 \mu\text{V}/\sqrt{\text{Hz}}) \sqrt{\Delta f} \approx 37.7 \mu\text{V}$$

$$\text{OUTPUT noise P-T-P value} = 6 \sqrt{V_{\text{out}}} = 6 \cdot 37.7 \mu\text{V} \approx 0.226 \text{ mV}$$

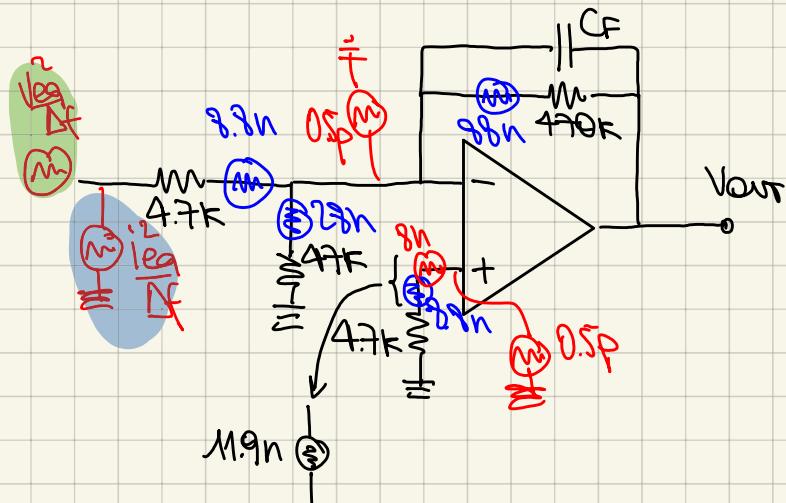
④ Compute The noise equivalents for input  $V_i$



SUPERPOSITION OF EFFECTS

$$\bullet \frac{V_{\text{in}, \text{eq}}^2}{\Delta f} = ?$$

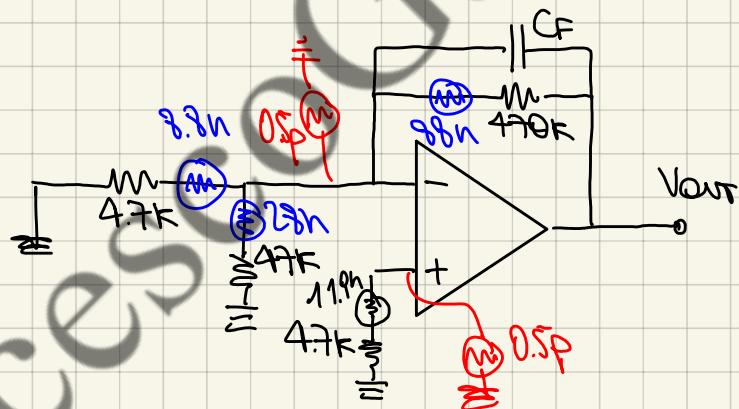- short-circuit The input
- turn-off  $i_{\text{in}, \text{eq}}/\Delta f$




$$\text{real output noise} = (1.63 \mu\text{V}/\sqrt{\text{Hz}})^2$$

$$\text{equivalent output noise} = \frac{V_{\text{in}, \text{eq}}^2}{\Delta f} \left( -\frac{470\text{k}}{4.7\text{k}} \right)^2 \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{They must be equal}$$

$$\frac{V_{\text{in}, \text{eq}}^2}{\Delta f} (100)^2 = (1.63 \mu\text{V}/\sqrt{\text{Hz}})^2 \Rightarrow \frac{V_{\text{in}, \text{eq}}^2}{\Delta f} = \frac{(1.63 \mu\text{V}/\sqrt{\text{Hz}})^2}{(100)^2} = (1.63 \text{nV}/\sqrt{\text{Hz}})^2$$

$$\bullet \frac{i_{\text{in}, \text{eq}}^2}{\Delta f} = ?$$

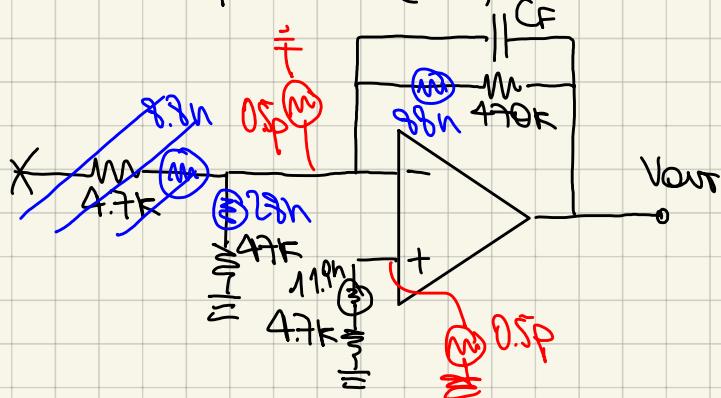- open-circuit The input
- turn-off  $V_{\text{in}, \text{eq}}/\Delta f$



real output noise = ? \*

$$\text{equivalent output noise} = \left( \frac{i_{in,eq}}{\Delta f} \right) (470k)^2$$



$$\begin{aligned} * \left| \frac{v_{out}}{\sqrt{Hz}} \right|^2 &= \cancel{\left( 8.3mV \sqrt{Hz} \right)^2} \cdot \cancel{\left( -\frac{470k}{4.7k} \right)^2} + \left( 28mV \sqrt{Hz} \right)^2 \left( -\frac{470k}{47k} \right)^2 + \left( 88mV \sqrt{Hz} \right)^2 \cdot (1)^2 + \\ &+ \left( 11.9mV \sqrt{Hz} \right)^2 \cdot \left( 1 + \frac{470k}{4.7k \cdot 47k} \right)^2 + \left( 0.5pA \sqrt{Hz} \right)^2 \cdot (4.7k)^2 \cdot \left( 1 + \frac{470k}{4.7k \cdot 47k} \right)^2 + \\ &+ \left( 0.5pA \sqrt{Hz} \right)^2 (470k)^2 \\ &= \left( 280mV \sqrt{Hz} \right)^2 + \left( 88mV \sqrt{Hz} \right)^2 + \left( 11.9mV \sqrt{Hz} \right)^2 (11)^2 + \left( 2.3mV \sqrt{Hz} \right)^2 (11)^2 + \left( 23mV \sqrt{Hz} \right)^2 \\ &\Downarrow \\ &= \left( 400mV \sqrt{Hz} \right)^2 \end{aligned}$$

$$\left( \frac{i_{in,eq}}{\Delta f} \right) (470k)^2 = \left( 400mV \sqrt{Hz} \right)^2 \Rightarrow \left( \frac{i_{in,eq}}{\Delta f} \right)^2 \approx \left( 850pA \sqrt{Hz} \right)^2$$

$$R_{s,opt} = \sqrt{\frac{(V_{in,eq}/\Delta f)}{(i_{in,eq}/\Delta f)}} = \sqrt{\frac{(16.3mV/\sqrt{Hz})^2}{(850pA/\sqrt{Hz})^2}} \approx 19.7 \Omega$$

$$\begin{aligned} NF_{opt} &= 10 \log_{10} \left( 1 + \frac{V_{in,eq}/\Delta f}{4kT R_{s,opt}} + \frac{i_{in,eq}/\Delta f}{4kT} R_{s,opt} \right) = \\ &= 10 \log_{10} \left( 1 + 2 \frac{\sqrt{(V_{in,eq}/\Delta f) \cdot (i_{in,eq}/\Delta f)}}{4kT} \right) \end{aligned}$$

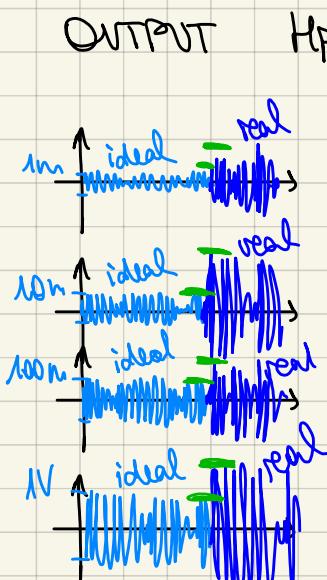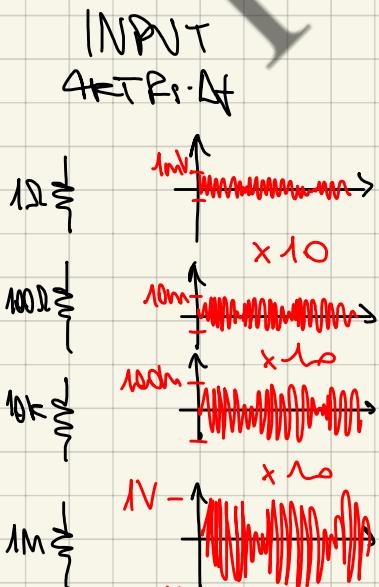$R_{s,opt}$  is not the resistance for which we have the minimum noise @ the output  
 → let's see what it is:




$$NF = \frac{\text{real}}{\text{ideal}}$$

↔ (IMPI!)

$R_{s,opt}$  is the input resistance for which at the output the real noise differs as less as possible from the ideal one, so the resistance for which we have the  $NF_{opt}$

## EXAMPLE 2

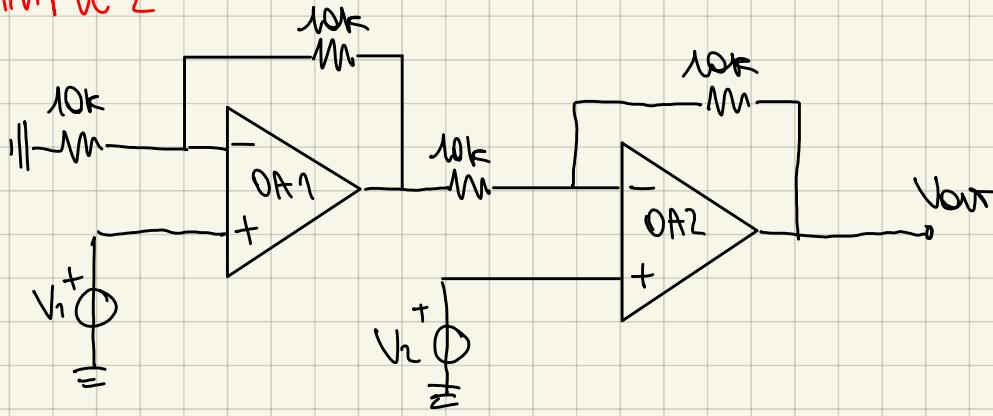

$$A_0 = 1000 \text{ dB} = 10^5, G_{FBWP} = 10 \text{ MHz} \quad V_{in}^2 / \Delta f = (1 \text{nV}/\text{Hz})^2 \quad i_{in}^2 / \Delta f = (1 \text{ pA}/\text{Hz})^2$$


A) Compute output spectral density neglecting 4FTR contributions

$$f_0 \cdot A_0 = G_{FBWP} \rightarrow f_0 = \frac{10 \text{ MHz}}{10^5} = 100 \text{ Hz}$$

$$\rightarrow \Delta f = f_N = NFBW = \frac{\pi}{2} f_0 \cong 157 \text{ Hz}$$

GOAL: we want to amplify a voltage difference b/w two nodes of the circuit

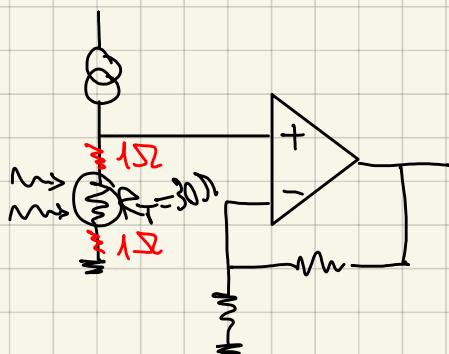for example we need to amplify a voltage across a photoresistor, so we have to pump a current through it:



Any possible parasitic in series w/ that  $R_T$  will cause an error in the reading

let's suppose to have two parasitic resistors equal to  $1\Omega$


so what we read is the voltage across  $R_T$  equal to  $32\Omega$

$$\text{Since } R_T = 30\Omega (@ 0^\circ\text{C}) + 0.15\Omega / ^\circ\text{C}$$


A parasitic term of  $2\Omega$  corresponds to a misreading of  $\frac{2}{0.15} \approx 14^\circ\text{C}$

How can we improve the configuration in order to decrease the dependence on the parasitics?

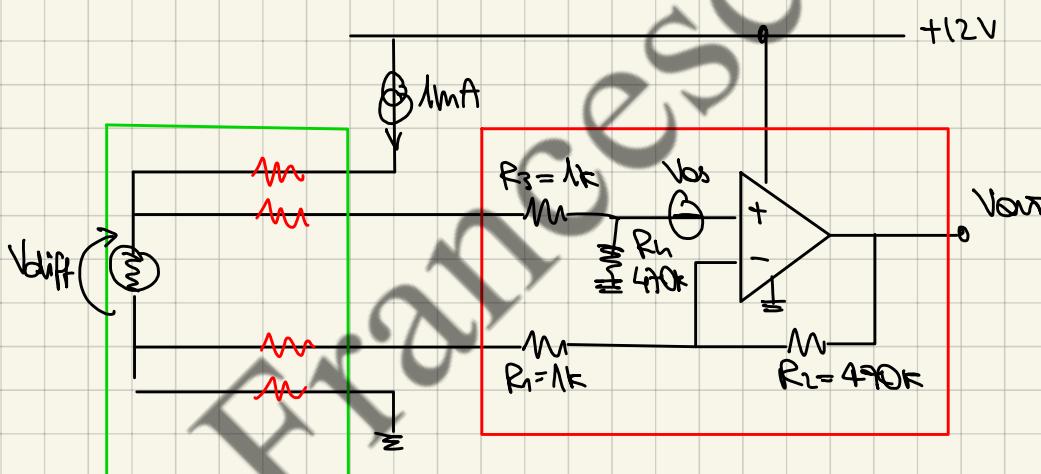SOLUTION ①: KELVIN CONNECTION → we use 4 wires instead of 2



it's a voltage difference amplifier

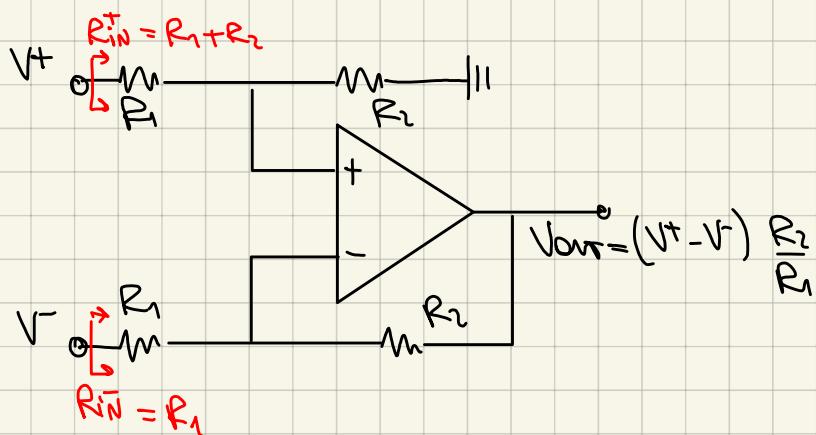


Since  $R_{in}^+ \neq R_{in}^-$ , there will be an unbalance current flow through the amplifier's input connections and the two currents will differ from each other so the voltage drops across the parasitic resistances will not compensate each other



How can we introduce a perfect symmetry of the slope?

↳ By introducing two buffers:

SOLUTION ②

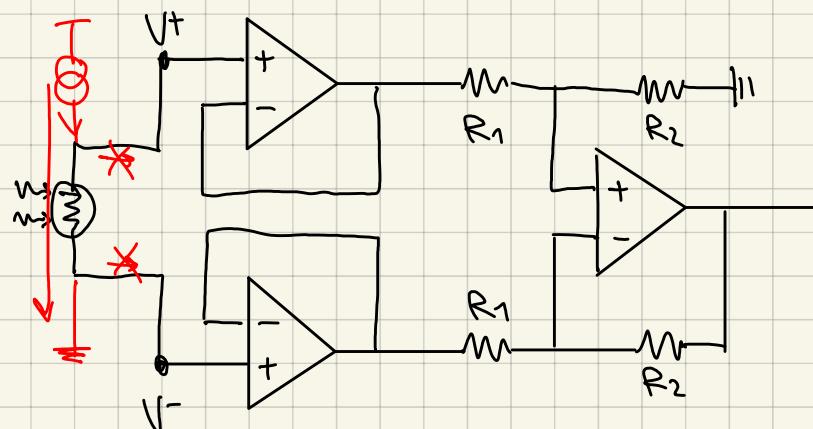


This solution is not suitable too but we are introducing too many noisy components (the buffers are noise sources and have their own offsets)




SOLUTION ③


DON'T DO THAT!!

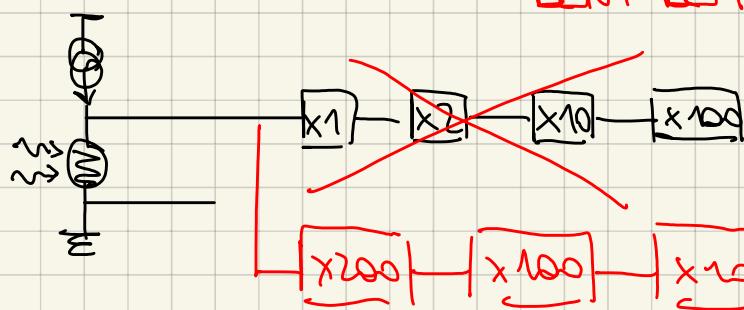

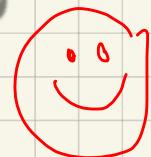→ it's better to place first the slope w/ the highest gain in this way we make somehow negligible the noise coming from the following stages



→ Amplify as soon as possible!!

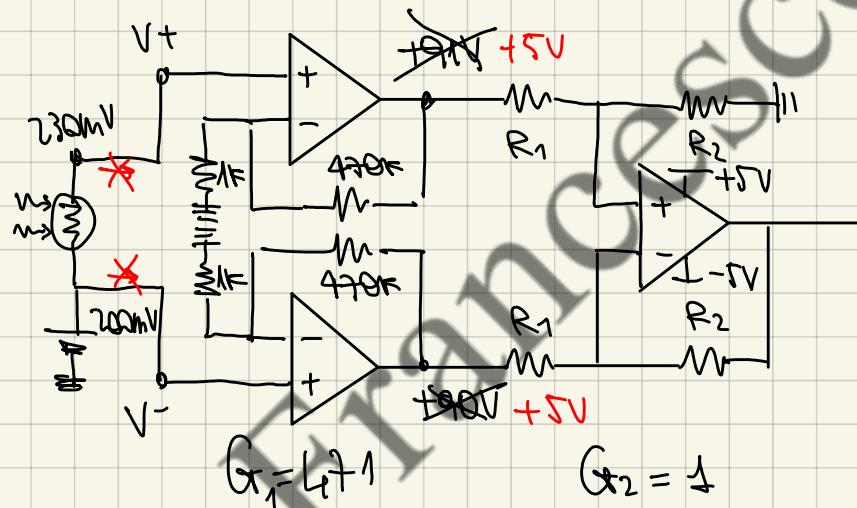

$$G_{T1} = 671$$


ISSUE: The common mode voltage could cause saturation of the input stage



SOLUTION ④ → We'd like to have  $G_{cm} = 1$  (very low)  $G_{diff} = h+1$  (very high)

How can we amplify the signal and not the common mode signal?

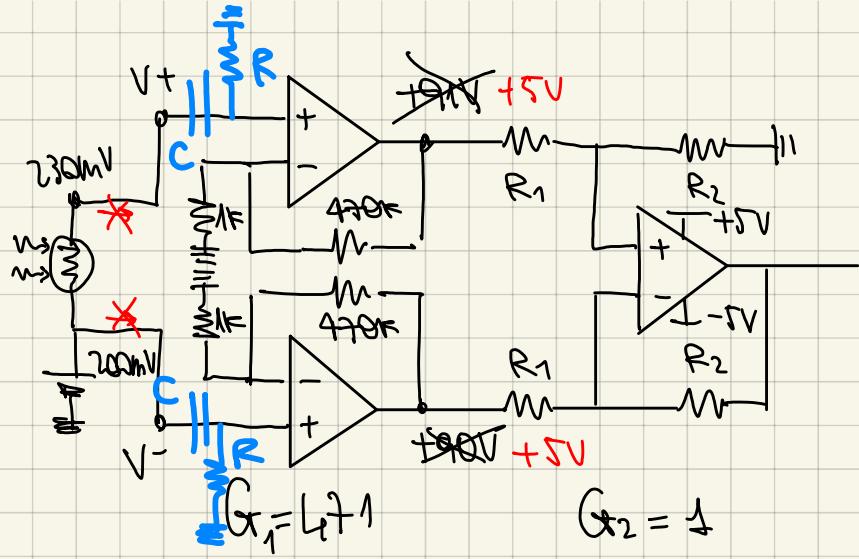↳ we can introduce a DC stop component → a capacitor




$$G_{t1} = 471$$

ISSUE: in our example the input signal can be also a DC signal and in this way it would be stopped by the capacitor

⇒ This solution is not suitable too! 😞

### Solution 5

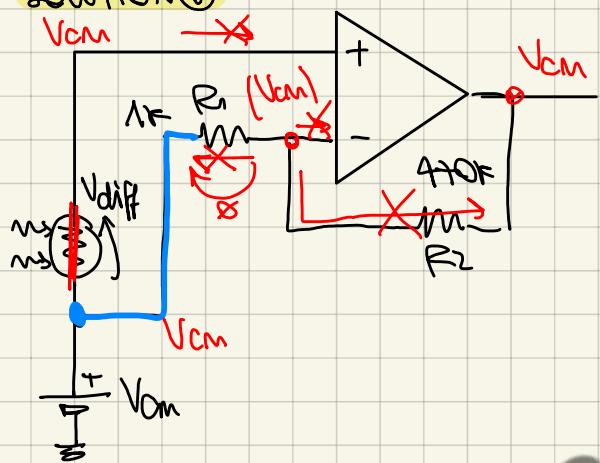


- if  $V_{diff} = 0$  we have  $V_{cm}$  at both inputs of the OpAmp


$$\Rightarrow G_{cm} = 1 \quad \text{😊}$$


- if  $V_{cm} = 0 \rightarrow V_{out} = V_{diff} \left( 1 + \frac{R_2}{R_1} \right)$

$$\Rightarrow G_{diff} = 471$$

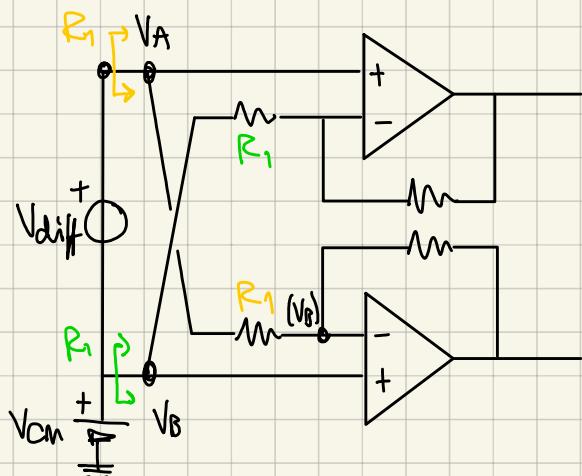

### Solution 6

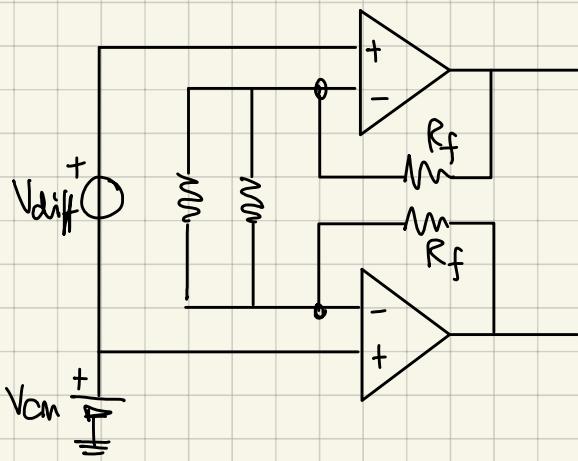

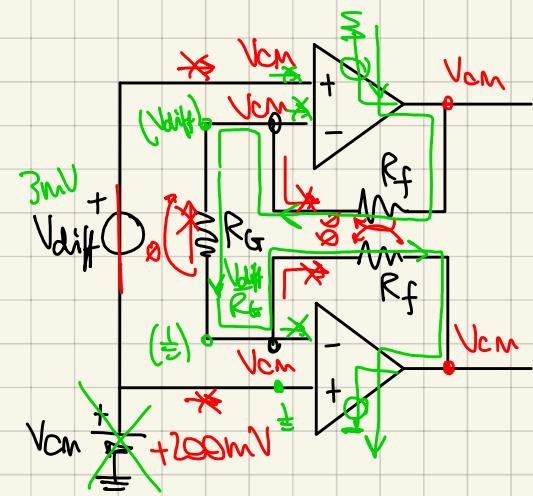


$G_{cm} = 1$  (not high)

$G_{diff} = ?$

$$V_{out,diff} = \left( \frac{V_{diff}}{R_{in}} \right) (R_f + R_G + R_f)$$

$$G_{diff} = \left( 1 + \frac{2R_f}{R_{in}} \right)$$


## INA - INSTRUMENTATION AMPLIFIER

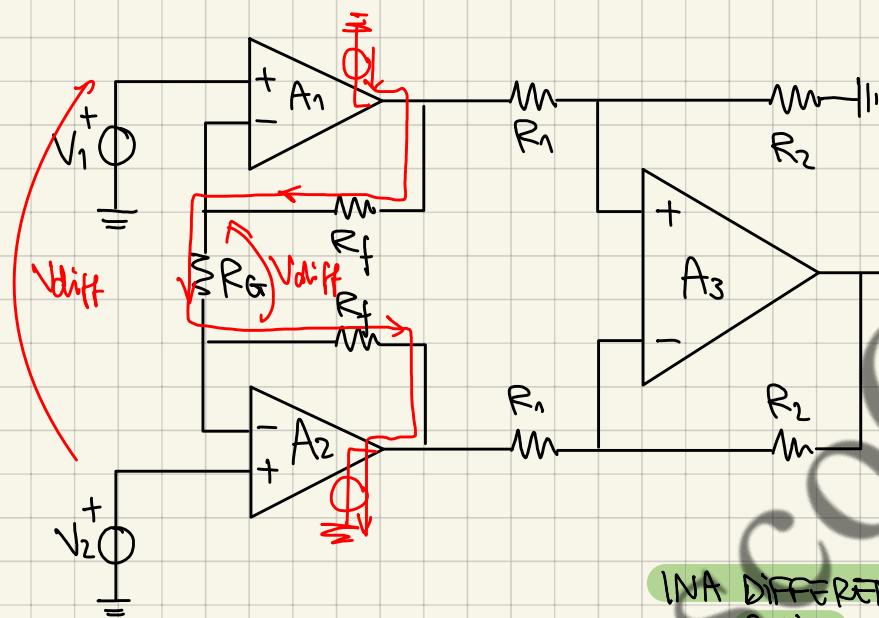



INA DIFFERENTIAL GAIN

$$G_{diff} = \left( 1 + \frac{2R_f}{R_G} \right) \left( \frac{R_2}{R_1} \right)$$


$$G_{cm} \approx 0$$

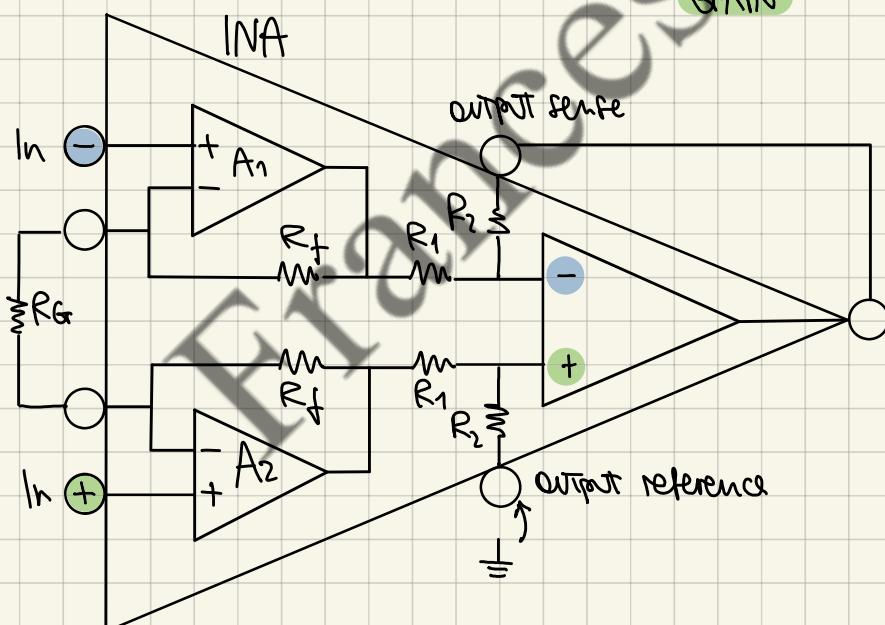

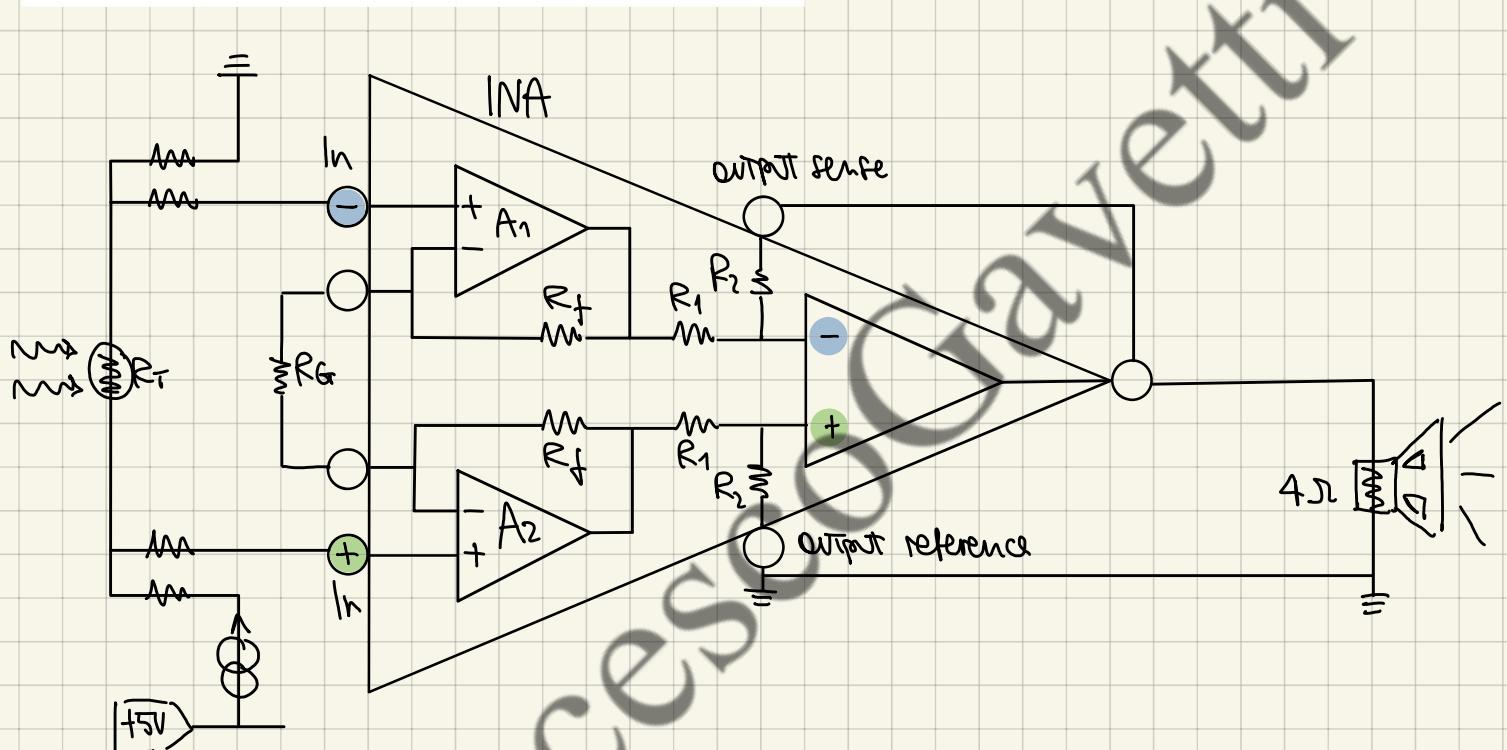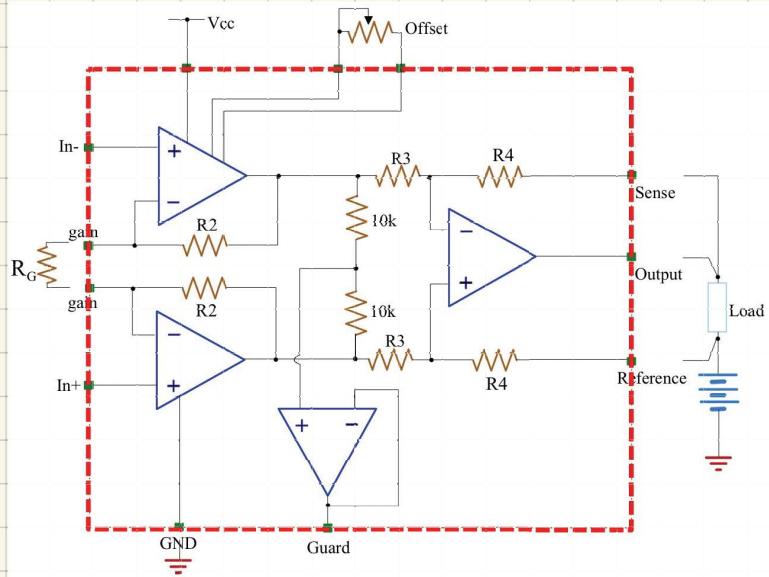
In principle if the offset were perfectly deterministic the INA would cancel it out, but since it's not, but it presents a mismatch, even an INA will have its offset.



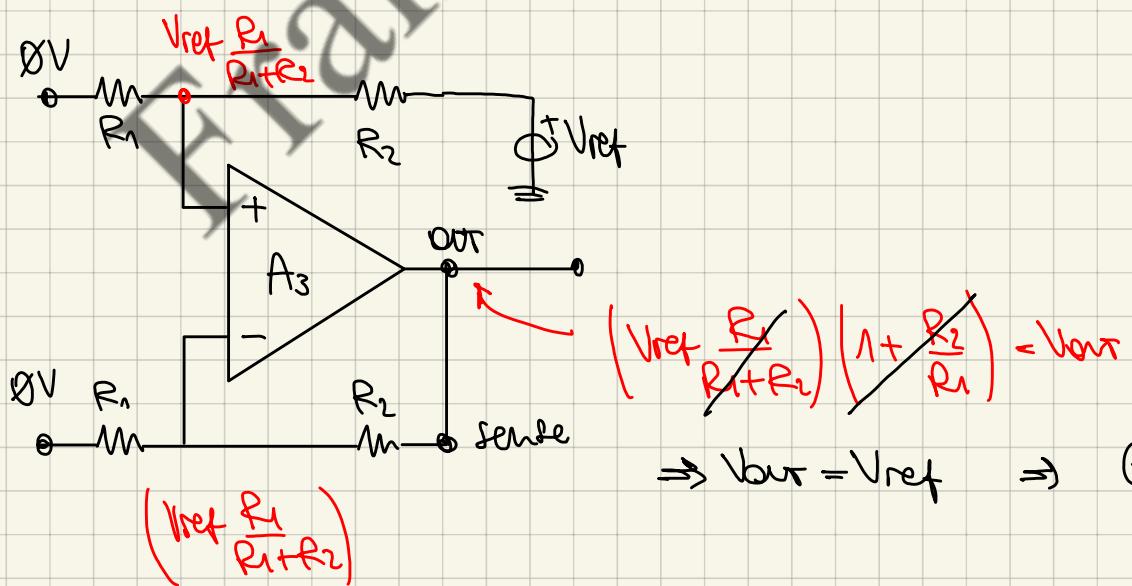What's the gain b/w The reference pin and The output pin?




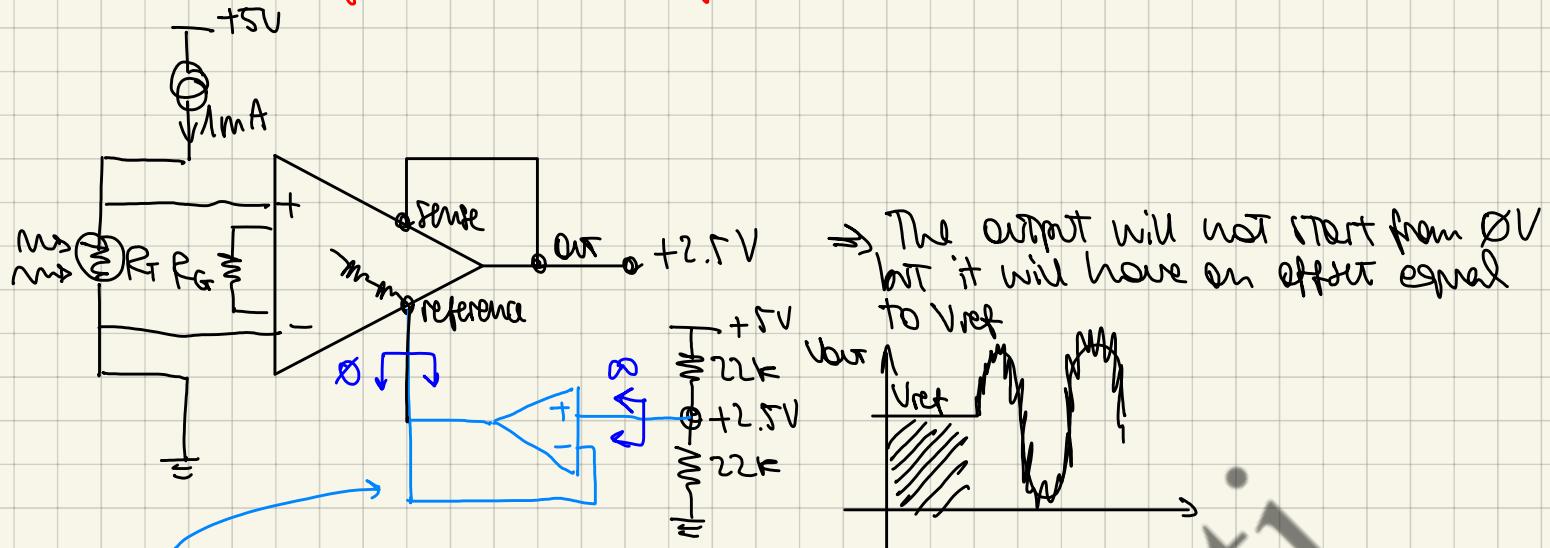How can we change the output voltage w.r.t  $V_{ref}$ ?



It's better to add a buffer because in this way  $R_L \approx R_{out}$

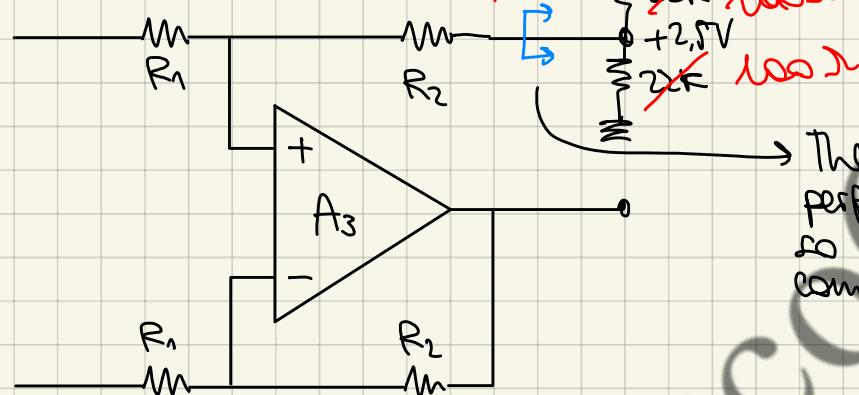If we do not use the buffer:  ~~$50\Omega$~~   ~~$1k\Omega$~~   ~~$22k\Omega$~~   ~~$100\Omega$~~   ~~$22k\Omega$~~   ~~$100\Omega$~~  negligible w.r.t  $R_2$



The 2nd stage is no longer a perfect voltage difference amplifier so at the output we'll have a common mode signal and so on...

So if we want to spend money and not use the buffer let's ensure that we use small resistances \*



There's still a big issue → in this way we have a direct path from PS to ground, so we discharge our battery very quickly if the two resistors are low


Two current calculations are shown:

$$I = \frac{5V}{200\Omega} = 0,025 = 25mA$$

$$I = \frac{5V}{44k} = 114 \mu A$$

→ let's choose a resistors' value in the middle which is high enough to determine a low leakage current and low enough to be negligible w.r.t  $R_2$  or (if you have enough money) let's use a buffer


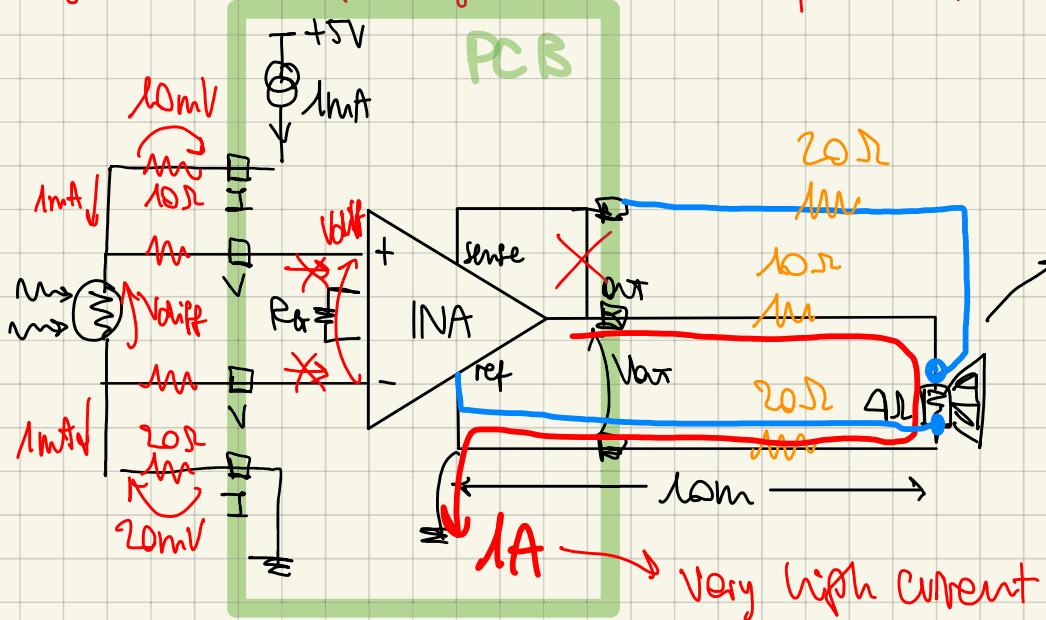
Why did The manufacturer give us The sense, The output and The reference pins?



let's connect The sense pin as close as possible to The load

There's also another pin called GUARD PIN


What's The guard pin useful for?

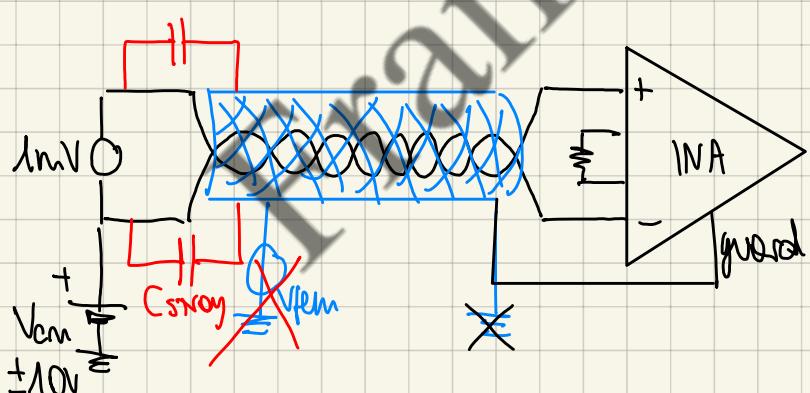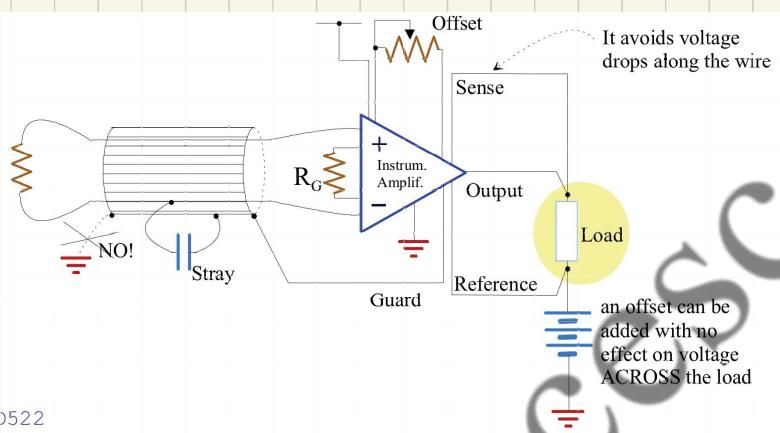

The guard pin is useful to provide a constant voltage to the coaxial cable or even better to provide a voltage that is independent of  $V_{stray}$ , but depends only on  $V_{cm}$  in order to reject the detrimental effects of  $C_{stray}$ .

How can we design an INA w/ a very low residual offset?


## CAZ, COMMUTATING AUTO ZEROING

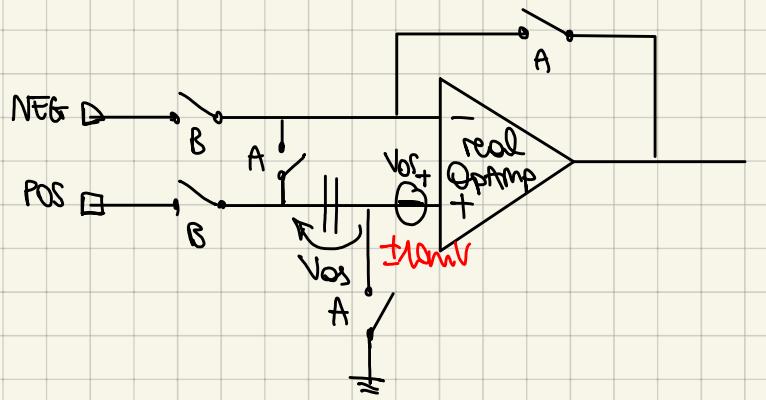


$$I_B = C \frac{dV}{dt}$$

$$C < \frac{Q}{V}$$

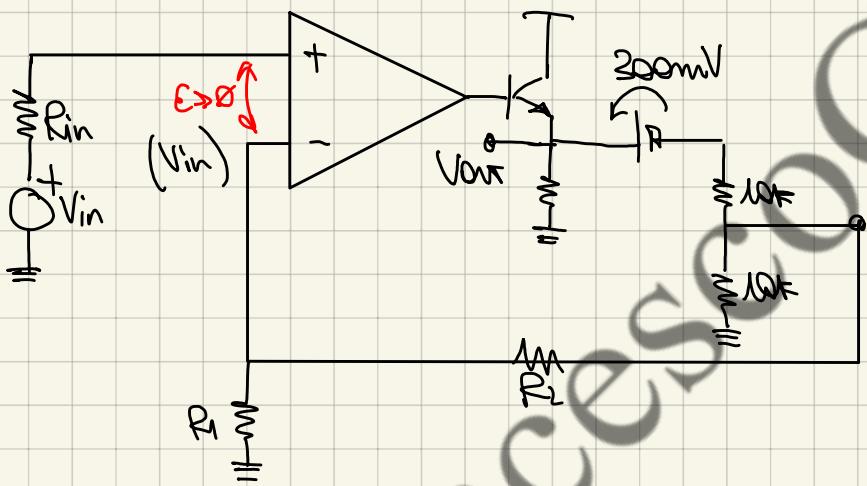We should do computations in anticlockwise direction:




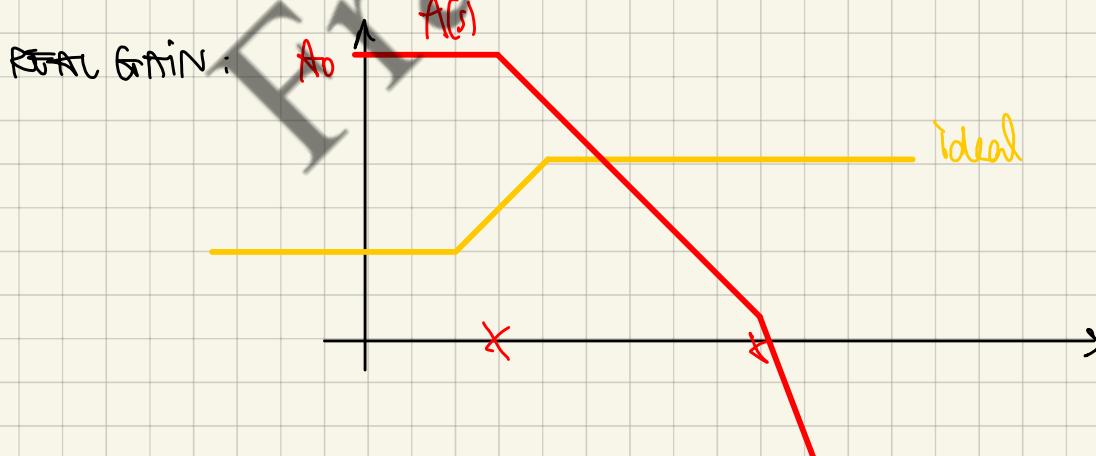
$$\text{IDEAL GAIN: } V_{out} = V_{in} \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{10k + 10k}{10k} \right) + 300mV$$


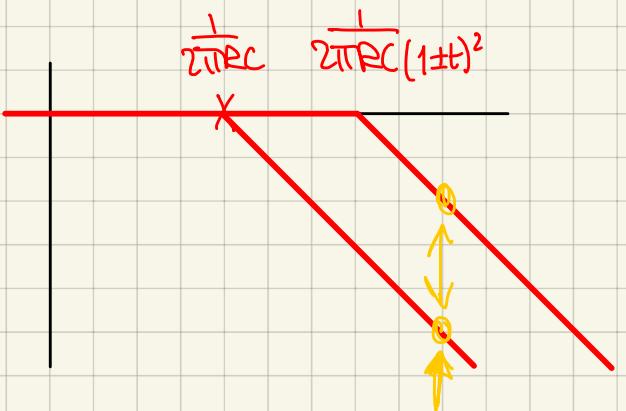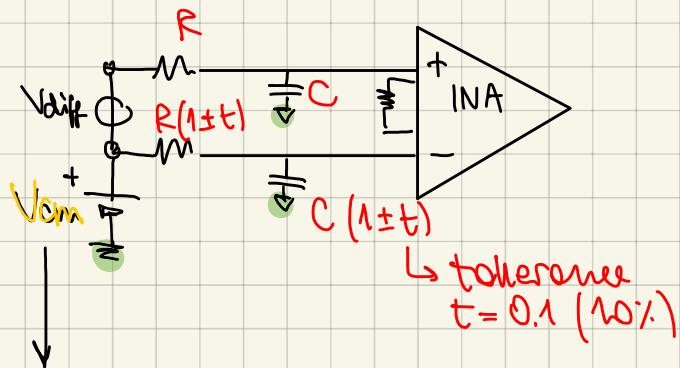
# INA - POSSIBLE CAUSES OF MISMATCHES AND ERRORS

Hp: Let's assume we want to low pass our signal





if  $V_{cm}$  is not a DC term, but it's applied at a given freq higher than those ones of the two poles, it will get differently amplified due to the mismatch

So this disturbance will appear at the output due to the mismatch even if  $V_{diff} = 0$


How can we solve this issue? How can we remove this residual value at the output?

↓  
we can use just one capacitor

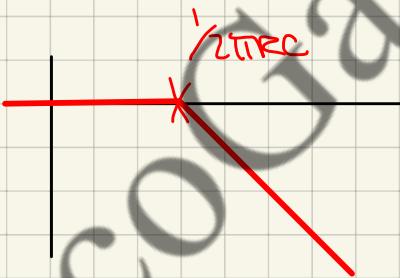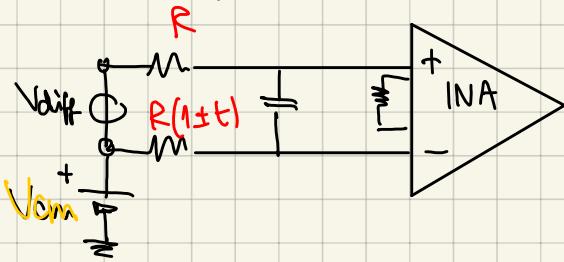

20/10/2021

## EXAMPLE 1

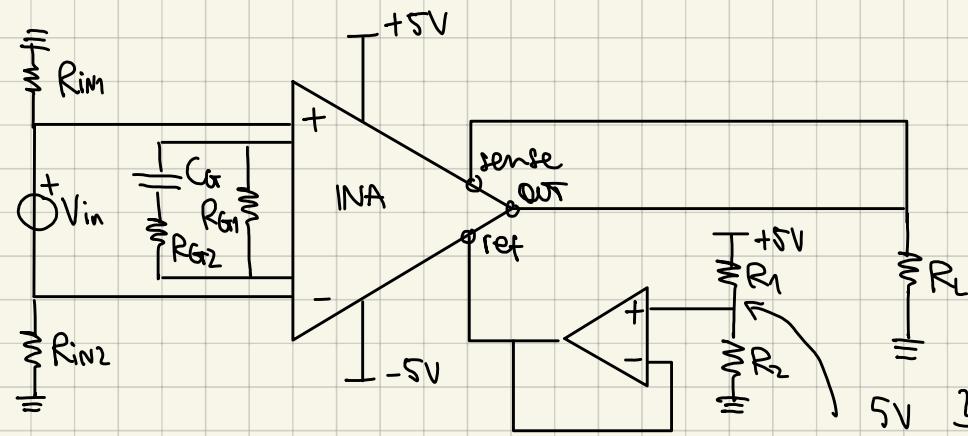

$$R_{in1} = R_{in2} = 100k\Omega$$

$$R_{G1} = 10k\Omega \quad R_{G2} = 1k\Omega$$

$$C_G = 1.6nF$$

$$R_1 = 3.3k\Omega \quad R_2 = 2.2k\Omega$$


$$R_L = 1k\Omega$$

All the resistors inside the INA are  $100k\Omega$

$$\frac{2.2k}{5.5k} = 2V \Rightarrow V_{ref} = 2V$$

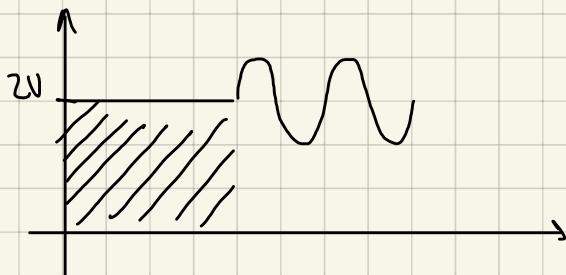(A) Compute  $V_{out}$  for  $V_{in} = 0$

$V_{out}$  is equal to  $V_{ref}$  @ the beginning  $V_{ref} = 5V \cdot \frac{2.2k}{5.5k} = 2V$



(B) Compute the ideal gain  $V_{out}(t)/V_{in}(t)$




$$G_{inA} = \left(1 + \frac{2R_f}{R_G}\right) \left(\frac{R}{R_f}\right) = 1 + \frac{200k}{10k} = 21$$

$$G_{inA}(0) = 1 + \frac{200k}{10k} = 21$$

$$G_{inA}(\infty) = 1 + \frac{200k}{10k} = 1 + \frac{200k}{99.1} = 221$$

There must be a zero and a pole


POL:

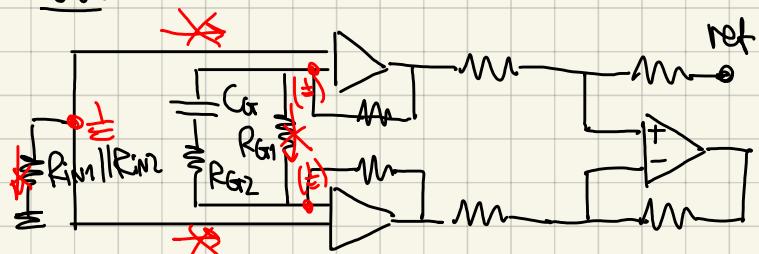


$$f_p = \frac{1}{2\pi C_G R_{G2}} = 99.5\text{kHz}$$

$$f_z = \frac{f_p}{21} = \frac{99.5}{21} = 9.4\text{kHz}$$

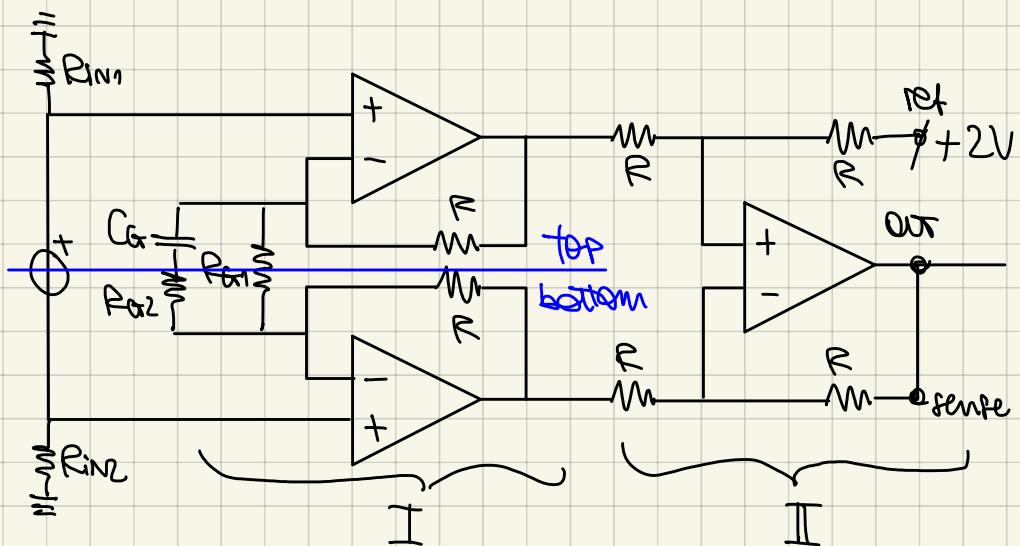To compute the real gain we have to open the INA:



1st stage half-circuit :

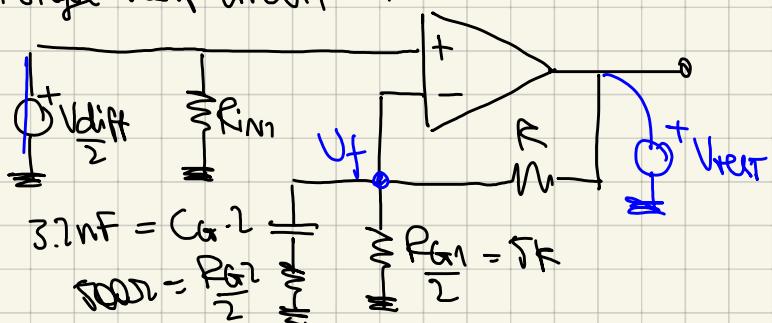


$$3.7\text{nF} = C_G \cdot 2 \quad \frac{R_{G1}}{2} = 5\text{k}$$

$$A_0 = 10000 \quad G_BW_P = 50\text{MHz}$$

$$f_0 = \frac{G_BW_P}{A_0} = \frac{50 \cdot 10^6}{10^5} = 500\text{Hz}$$

$$\beta_{HC}(s) = ? \quad \begin{cases} \beta_{HC}(0) = \frac{5\text{k}}{10\text{k}} = \frac{1}{2} \Rightarrow \frac{1}{\beta} \beta_{HC}(0) = 2 \\ \beta_{HC}(\infty) = \frac{5\text{k} \parallel 500}{100\text{k} + 5\text{k} \parallel 500} = \frac{454 \cdot 54}{100\text{k} + 454 \cdot 54} = 5.52 \cdot 10^{-3} \Rightarrow \frac{1}{\beta} \beta_{HC}(\infty) = 221 \end{cases}$$

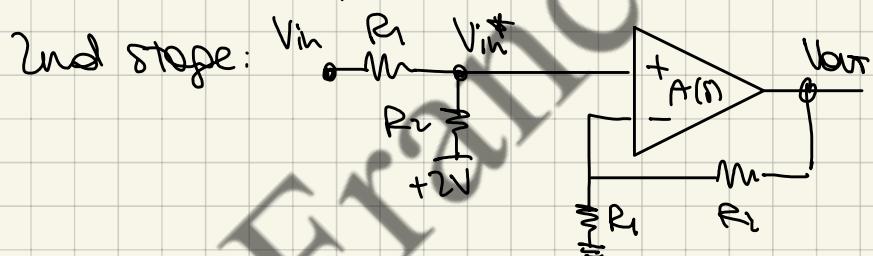
$$f_{2,p} = \frac{1}{2\pi C_G \cdot 2 \cdot R_{G1/2}} = 99.5\text{kHz} \quad f_{P,P} = 9.4\text{kHz}$$



$$\text{ideal gain: } V_{in*} = V_{in} \quad \frac{R_2}{R_1+R_2} = \frac{1}{2} V_{in} \quad \left. \right\} G_{i,2}(s) = 1$$

$$V_{out} = \frac{1}{2} V_{in} \left( 1 + \frac{R_2}{R_1} \right) = \frac{1}{2} V_{in} \cdot 2 = V_{in}$$
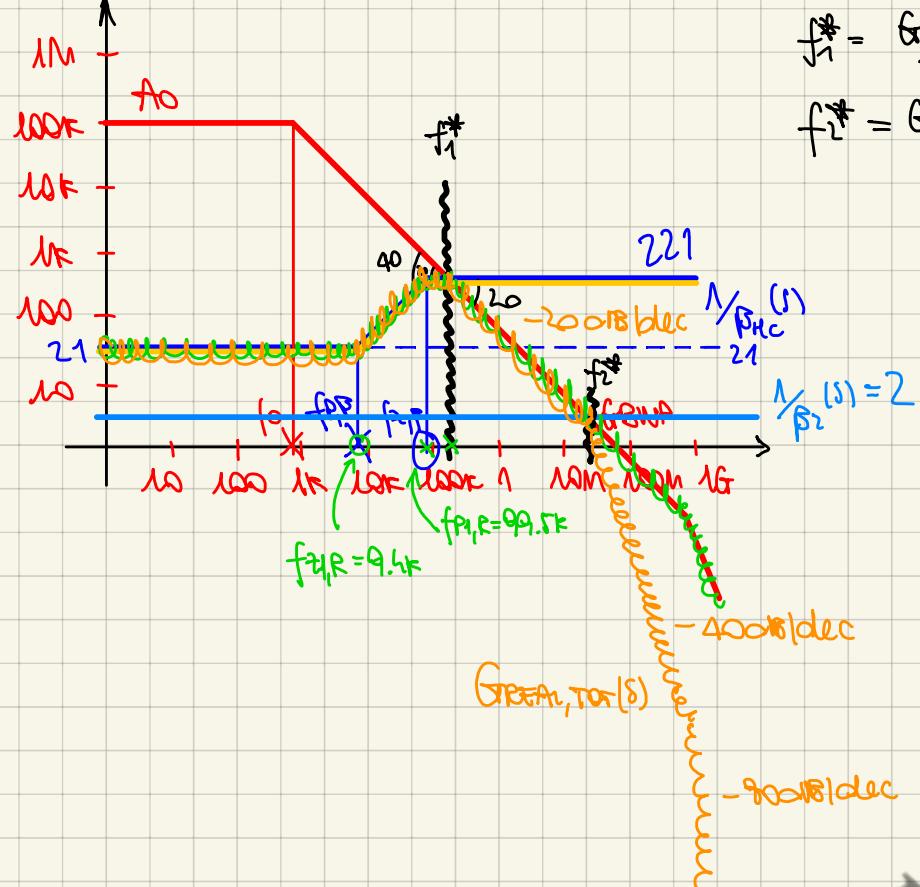
$$\beta_2(s) = \frac{1}{2} \Rightarrow \frac{1}{\beta_2} (s) = 2$$




$$f_1^* = \frac{G_{FBWP}}{2\pi} \approx 226 \text{ kHz}$$

$$f_2^* = \frac{G_{FBWP}}{2} = 25 \text{ MHz}$$

$$\begin{aligned} PM_{REFIN1} &= 180^\circ - \tan^{-1}\left(\frac{f_1^*}{f_0}\right) - \tan^{-1}\left(\frac{f_1^*}{f_t}\right) + \tan^{-1}\left(\frac{f_2^*}{f_t}\right) \\ &\approx 180^\circ - 90^\circ - 90^\circ + \tan^{-1}\left(\frac{f_2^*}{f_t}\right) \approx 66^\circ \end{aligned}$$

## EXAMPLE 2

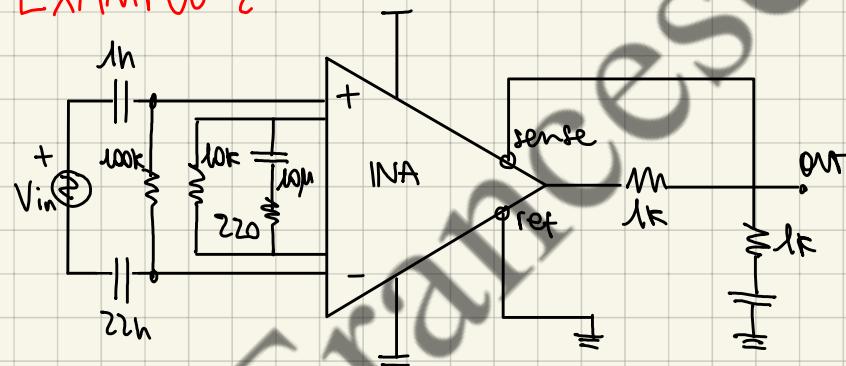


$$R_f = 100k\Omega$$

Ⓐ Plot the Bode diagram for  $V_{out}(f)/V_{in}(f)$  ideal gain


(let's divide the circuit in 2 stages)

1st stage:

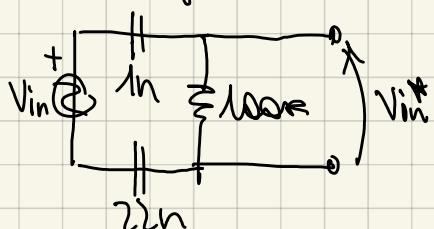


$$\frac{V_{in}^*}{V_{in}}(0) = \infty$$

$$\frac{V_{in}^*}{V_{in}}(\infty) = 1$$

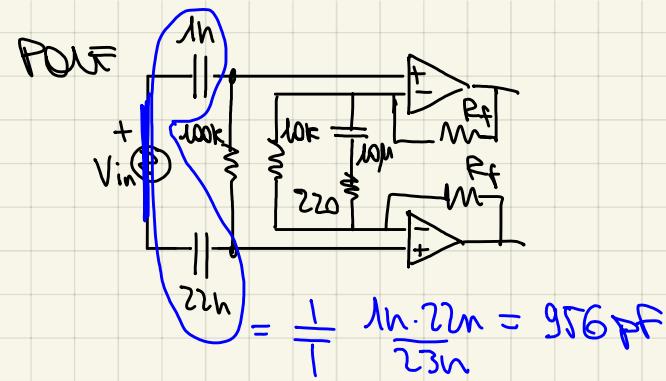
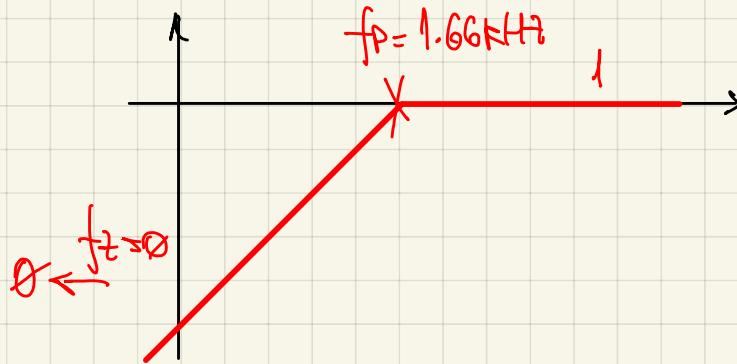
$$f_p = \frac{1}{2\pi Q\sqrt{f_p} \cdot 100k} = 1.66 \text{ kHz}$$




2nd stage  $\rightarrow$  INA:  $\rightarrow$  HP: internal INA's resistances are all equal

$$G_{i,INA}(s) = G_{diff} = \left(1 + \frac{2R_f}{R_G}\right) \left(\frac{R_L}{R_1}\right)$$

$$G_{i,INA}(0) = 1 + \frac{2R_f}{10k} = 1 + \frac{200k}{10k} = 21$$
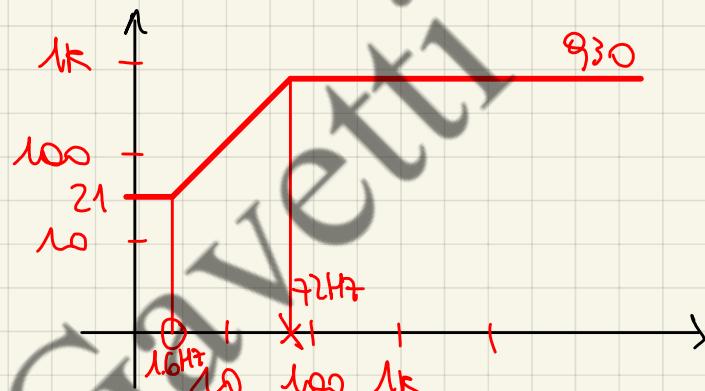
$$G_{i,INA}(\infty) = 1 + \frac{2R_f}{10k \parallel 220} \approx 930$$



There must be a zero and a pole, at least

$f_p,1INA = \frac{1}{2\pi 100\mu 220} = 72 \text{ Hz}$

$f_t,1INA = \frac{f_p,1INA}{930} = 1.6 \text{ Hz}$

We have to multiply these two points:

