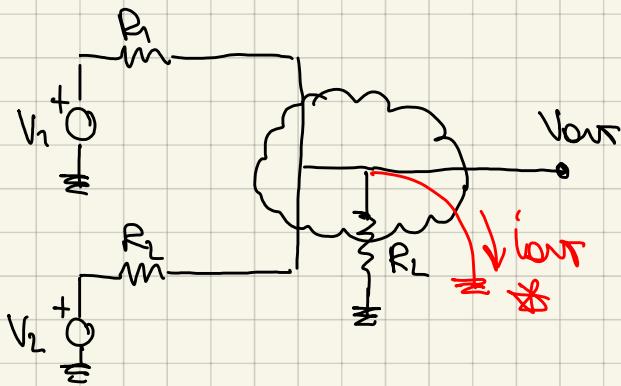


ES03 - OPAMP STAGES

VOLTAGE (AND CURRENT) ADDER




$$V_{\text{out}} = V_{\text{out}}(V_1) + V_{\text{out}}(V_2) = \\ \frac{V_1}{R_1 + R_2} \frac{R_L \parallel R_2}{R_1 \parallel R_2} + V_2 \frac{R_L \parallel R_1}{R_2 + R_L \parallel R_1}$$

We don't like this adding node bcz if V_1 stays the same, but V_2 changes also V_{out} changes. Furthermore, There is the cross-talk issue.


Another solution could be:

↳ This time $i_{\text{in}} = \frac{V_1}{R_1} + \frac{V_2}{R_2} \rightarrow$ There is no coupling (no cross-talk)
but this is not the amplification I'm
glad to have

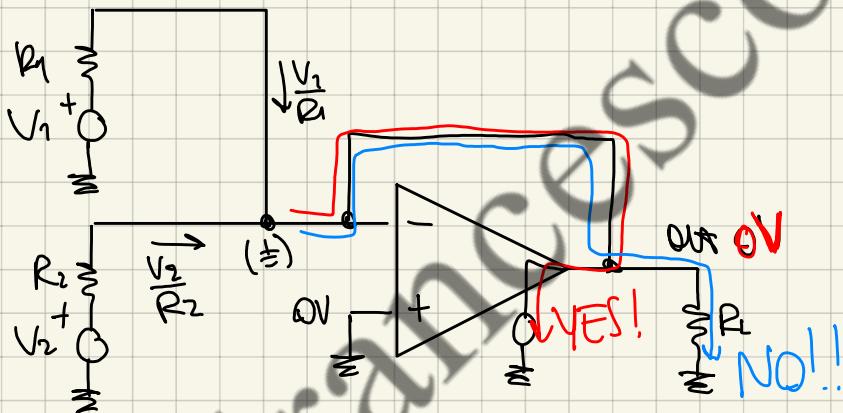→ I want a ground, but it has to be virtual



Now if I want the output not to be OV:

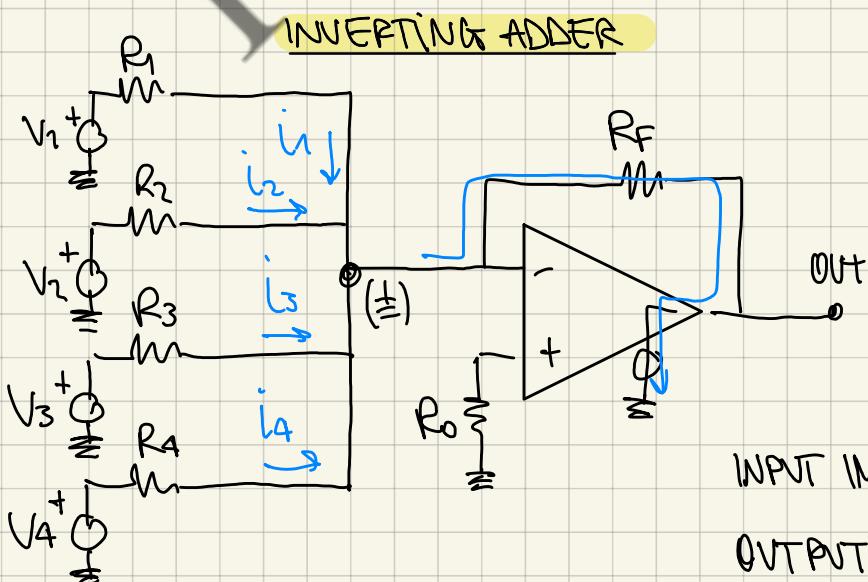


$$V_{\text{out}} = - \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_4}{R_4} \right) \cdot R_F$$

INPUT IMPEDANCE $Z_{\text{IN}} = R_1$

OUTPUT IMPEDANCE $Z_{\text{out}} = 0$

VOLTAGE SUBTRACTOR

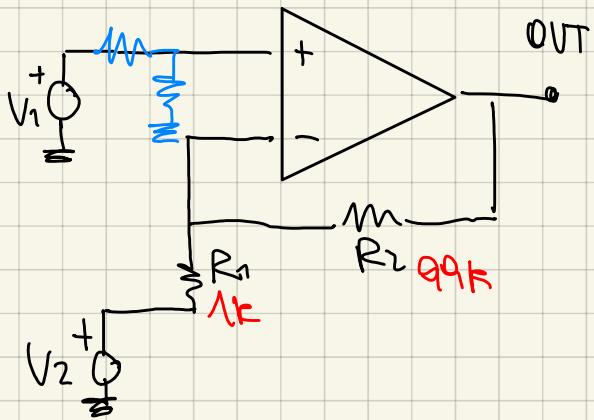

$$\begin{aligned} V_{out} &= V_1 \left(1 + \frac{R_2}{R_1}\right) + V_2 \left(-\frac{R_2}{R_1}\right) \\ &\doteq V_1 \left(1 + \frac{R_2}{R_1}\right) - V_2 \left(\frac{R_2}{R_1}\right) \end{aligned}$$


100 99

There is always a mismatch: The \oplus input gets amplified more than the \ominus input

How can we modify the circuit in order to have the same amplification?

Since V_1 gets amplified more than V_2 , we should attenuate it


Let's introduce an attenuator

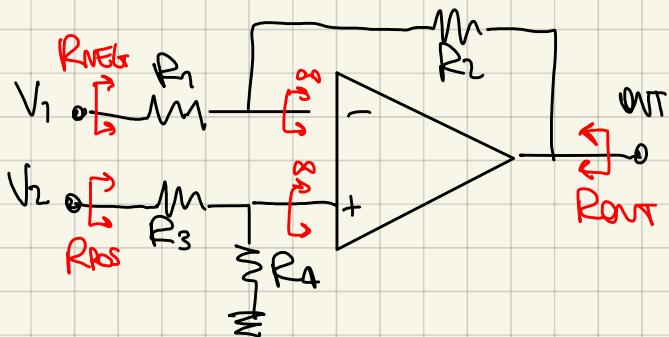

$$\begin{aligned} V_{out} &= V_2 \frac{R_4}{R_3+R_4} \left(1 + \frac{R_2}{R_1}\right) - V_1 \frac{R_1}{R_1} = V_2 \frac{1}{1 + R_3/R_4} \left(1 + \frac{R_2}{R_1}\right) - V_1 \frac{R_1}{R_1} \\ &= V_2 \frac{R_4/R_3}{1 + R_4/R_3} \left(1 + \frac{R_2}{R_1}\right) - V_1 \frac{R_1}{R_1} \end{aligned}$$

$$\text{When } \frac{R_2}{R_1} = \frac{R_4}{R_3} \rightarrow V_{out} = V_2 \frac{R_4}{R_3} - V_1 \frac{R_2}{R_1} = \frac{R_2}{R_1} V_{diff} \quad \text{where } V_{diff} = V_2 - V_1$$

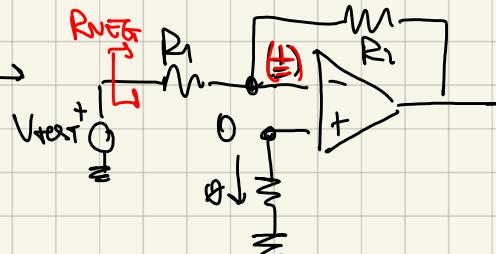
$$\text{INPUT IMPEDANCE } \left\{ \begin{array}{l} R_{POS} = R_3 + R_4 \\ R_{NEG} = R_1 \end{array} \right.$$



OUTPUT IMPEDANCE $R_{out} \approx 0$

$R_{NEG} \neq R_{POS} \Rightarrow \text{ISSUE} !!!$


IDEAL VOLTAGE INTEGRATOR

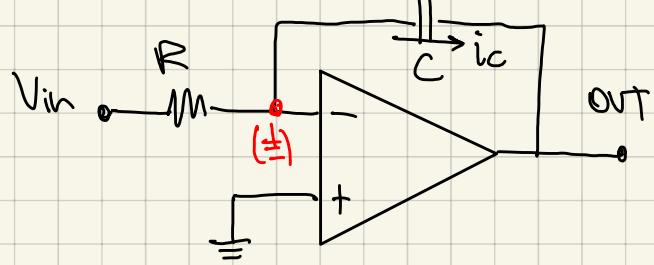

$$i_{IN} = \frac{V_{IN}}{R}$$

$$\begin{cases} V_{OUT} = V_C = -\frac{1}{C} \int i_C(t) dt \\ i_C = i_{IN} \end{cases}$$
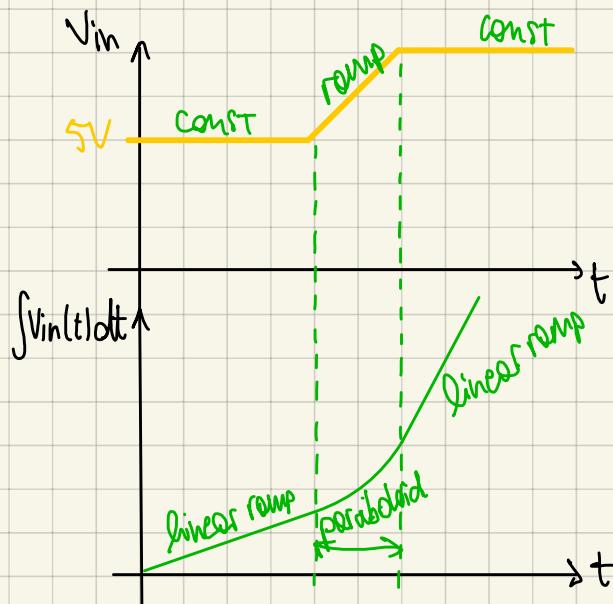
$$\rightarrow V_{OUT} = -\frac{1}{RC} \int V_{IN}(t) dt$$



$$R = V/I = [V/A] \quad I = \frac{dQ}{dt} = \left[\frac{C}{S} \right]$$

$$C = Q/V = [C/V]$$

$$\begin{aligned} RC &= [S] [F] = \left[\frac{V}{A} \right] \cdot \left[\frac{C}{V} \right] \\ &= \left[\frac{V}{A} \right] \left[\frac{C}{V} \right] = [S] \end{aligned}$$

$$\begin{aligned} A_V(s) &= \frac{V_{OUT}(s)}{V_{IN}(s)} = -\frac{Z_2(s)}{Z_1(s)} = -\frac{1/SC}{R} = -\frac{1}{SRC} \\ &= -\frac{1}{sT} \end{aligned}$$

inverting stage

$$s = \alpha + j2\pi f$$


$\frac{1}{s}$ = integration operator

@ DC \rightarrow C open $A_V(0) = -\frac{1}{SRC} \Big|_{s \rightarrow 0} \rightarrow \infty \Rightarrow$ hence eventually the OpAmp always saturates

↳ @ DC, since the capacitor is open and the input and output are not touching each other, the OpAmp cannot control its input so the v.g. can no longer exist for long period of time

How can we solve the issue that $A_V(0) \rightarrow \infty$?

REAL VOLTAGE INTEGRATOR

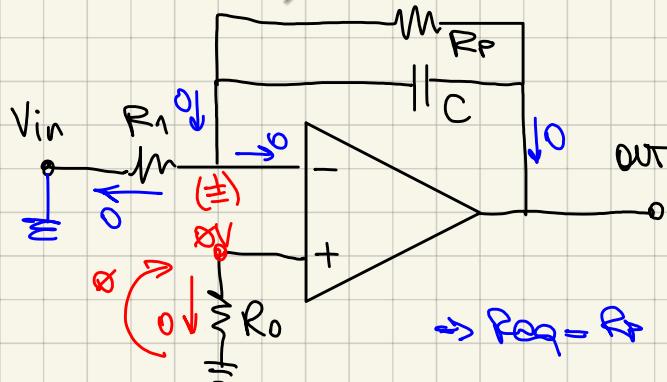


→ we add R_p in || to C in order to guarantee even @ DC a feedback path!!
 R_p causes a modification in the Bode diagram

Asymptotic analysis:



$$@DC \rightarrow C \text{ open} \rightarrow A_V(0) = -\frac{R_p}{R_1}$$

$$@HF \rightarrow C \text{ short} \rightarrow A_V(\infty) = 0$$



pole calculation

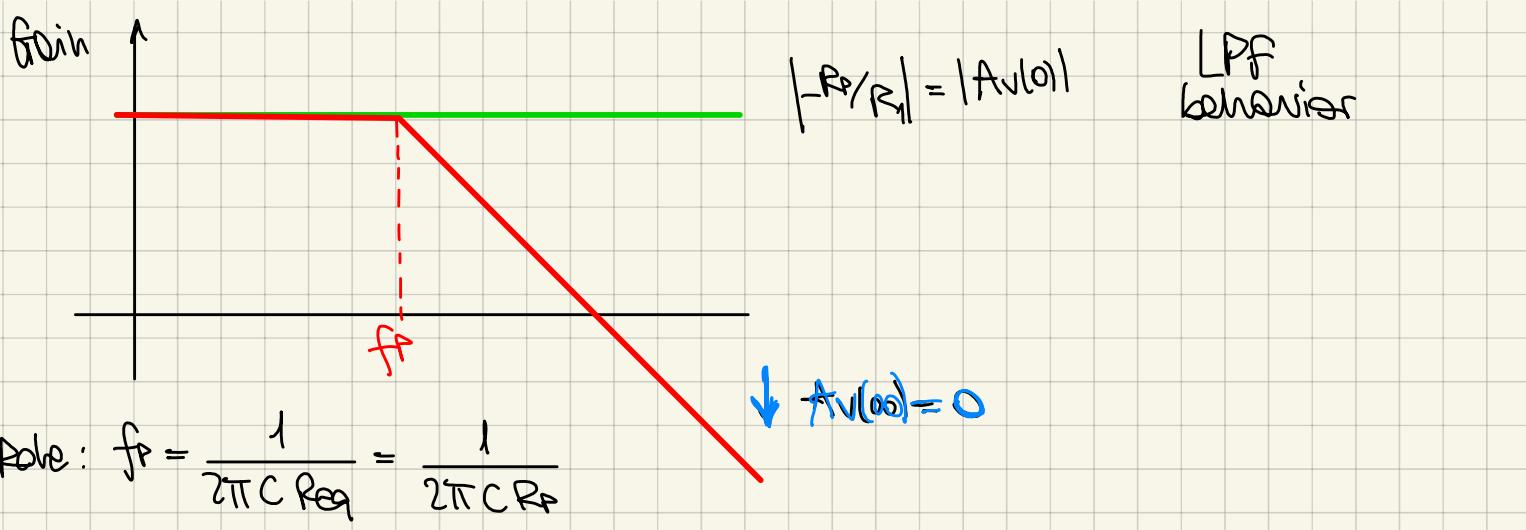

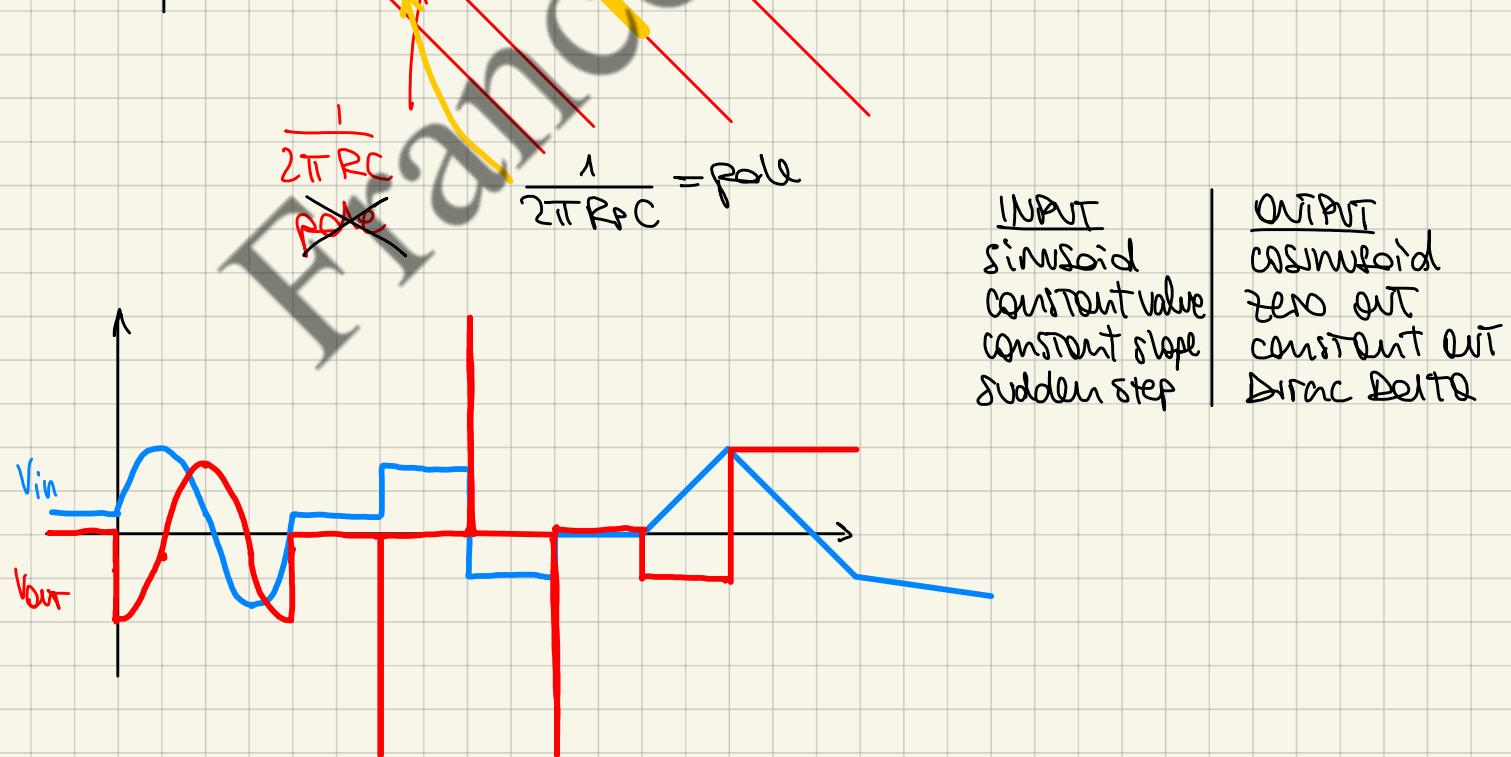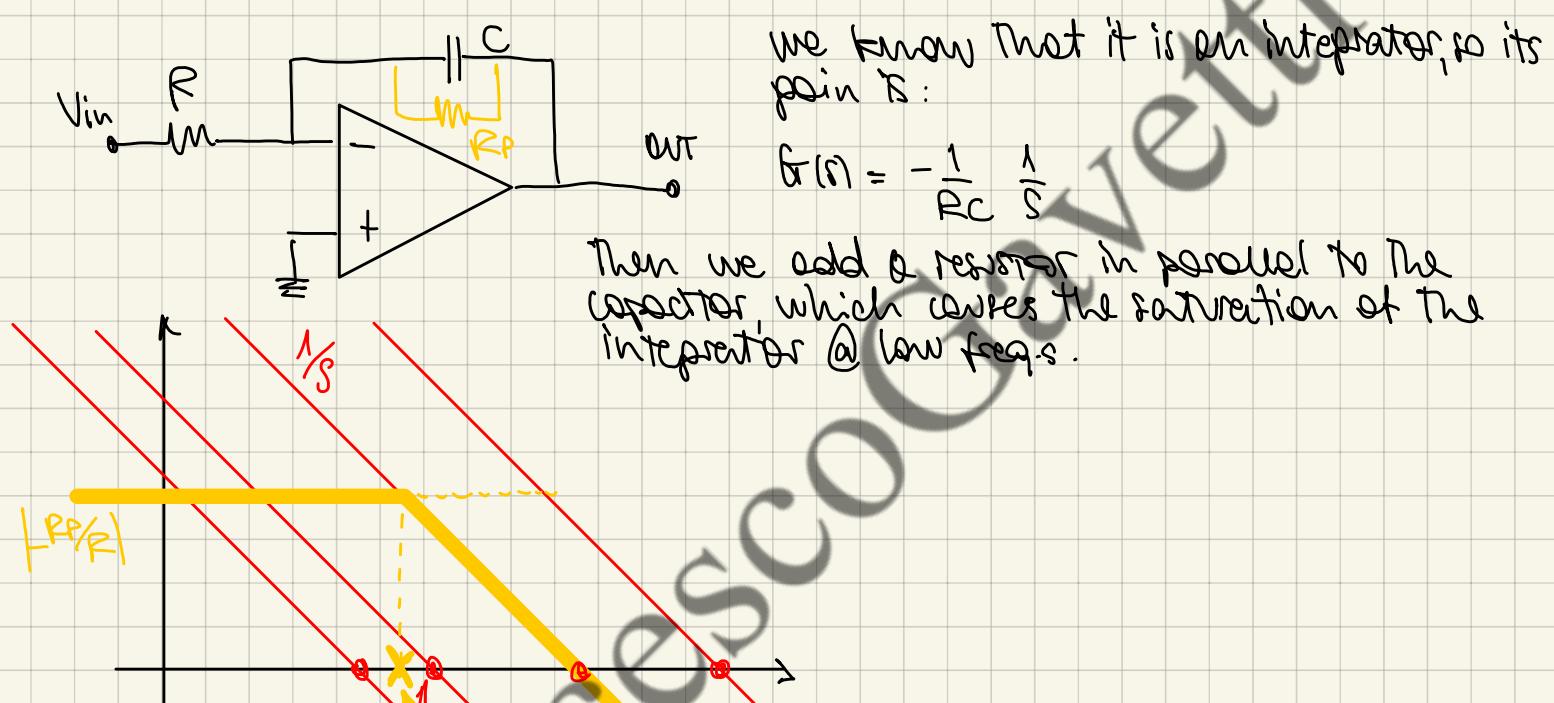There is also another way to study the circuit:



IDEAL VOLTAGE DERIVATOR

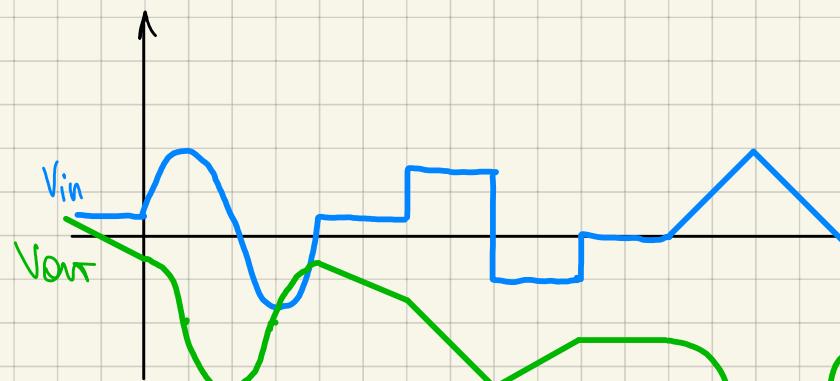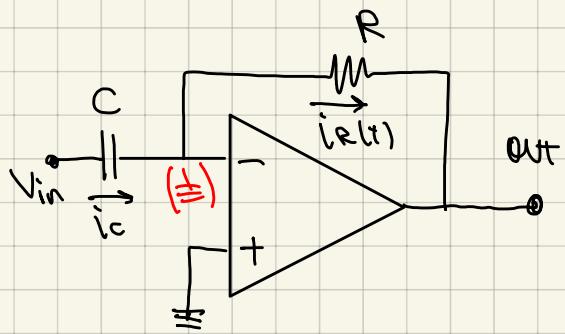


INPUT
constant value
zero value
ramp
sine

OUTPUT
ramp
zero value
paraboloid
cosine

@DC \rightarrow C is open $\rightarrow A_v(0) = 0$

@HF \rightarrow C is short $\rightarrow A_v(\infty) = \infty$ ISSUE!!

REAL VOLTAGE DERIVATOR

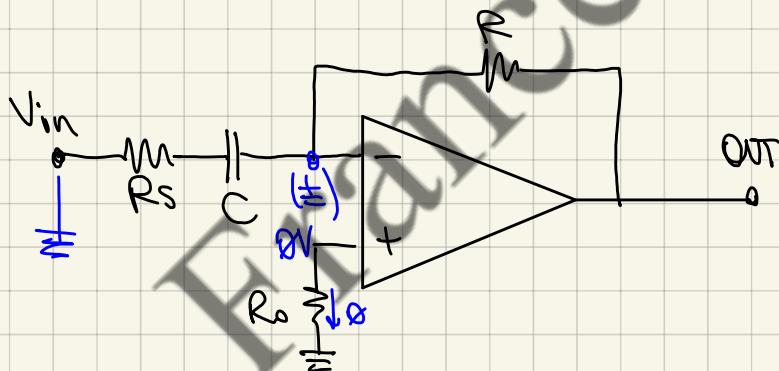


@DC $\rightarrow A_v(0) = 0$



@HF $\rightarrow A_v(\infty) = -R/R_s$

pole = ? *

$$R_{eq} = R_s$$

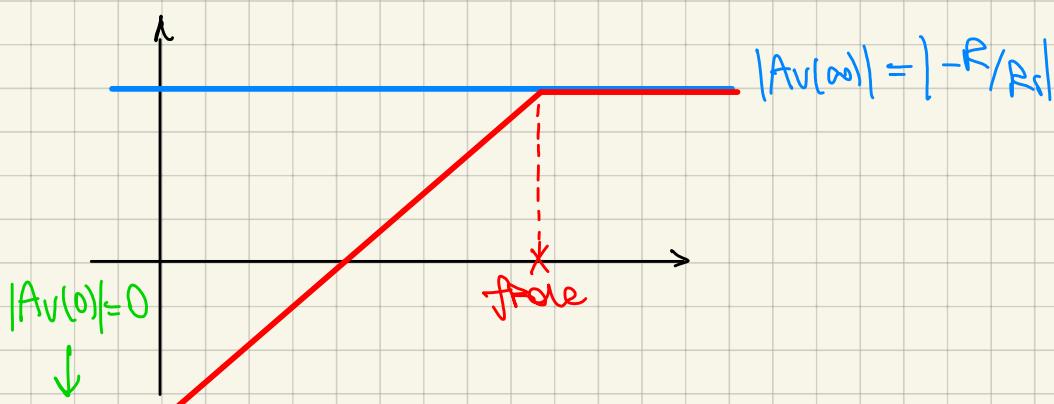
$$\rightarrow f_{pole} = \frac{1}{2\pi C R_s}$$



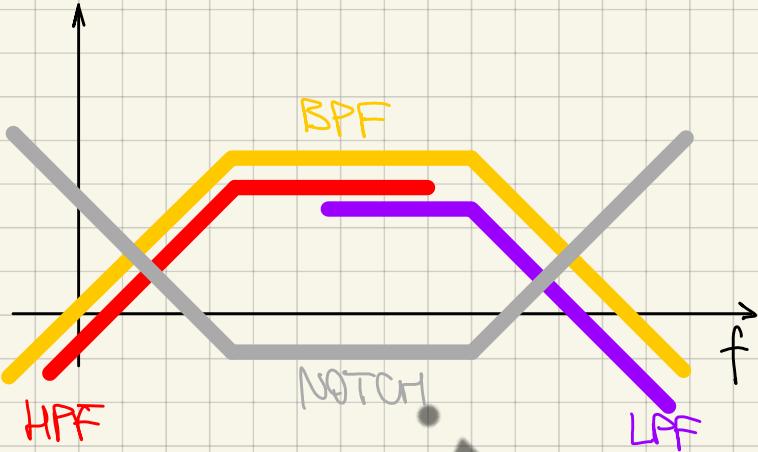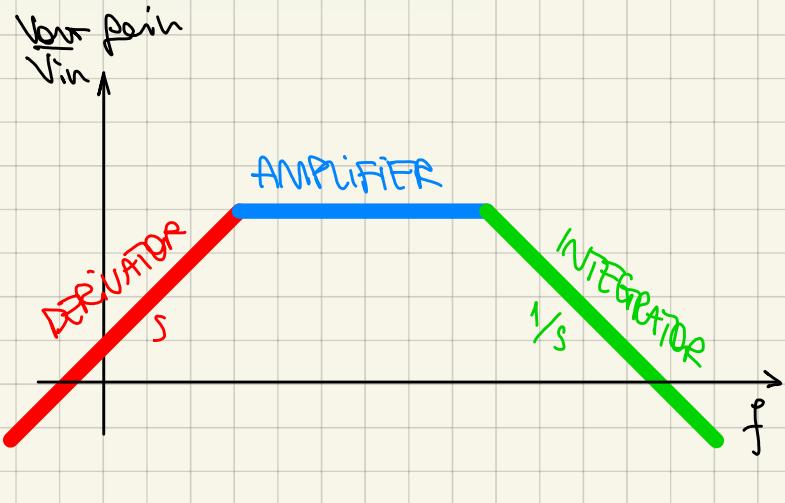

1ST AND 2ND ORDER ACTIVE FILTERS


• LOW-PASS FILTER (INTEGRATOR)

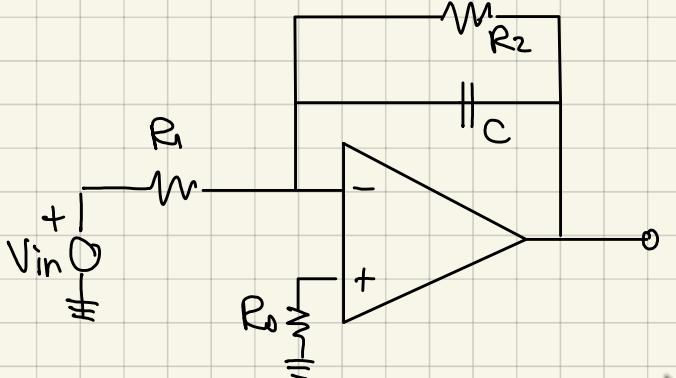


$$H_0 = -R_2/R_1$$

$$H_{\infty} = 0$$

$$f_{pole} = \frac{1}{2\pi C R_2}$$

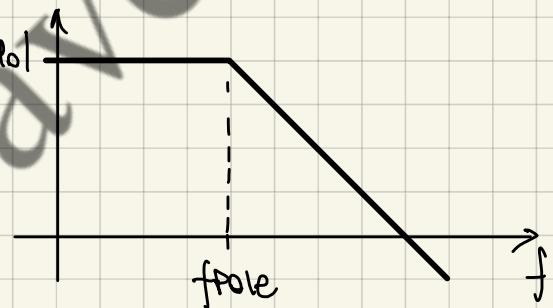


• HIGH-PASS FILTER (DERIVATOR)

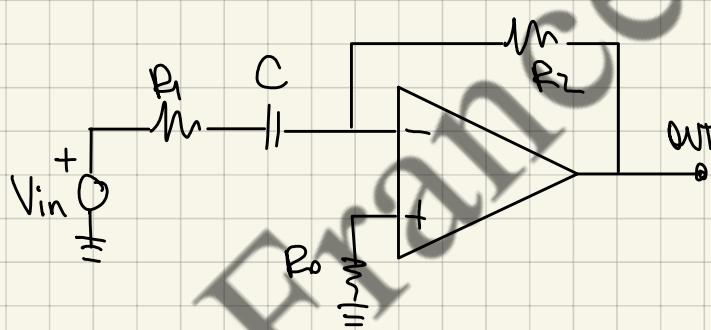


$$H_0 = 0$$

$$H_{\infty} = -R_2/R_1$$

$$f_{pole} = \frac{1}{2\pi C R_1}$$

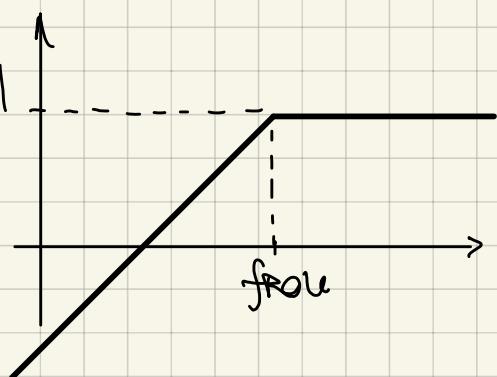


• BAND-PASS FILTER

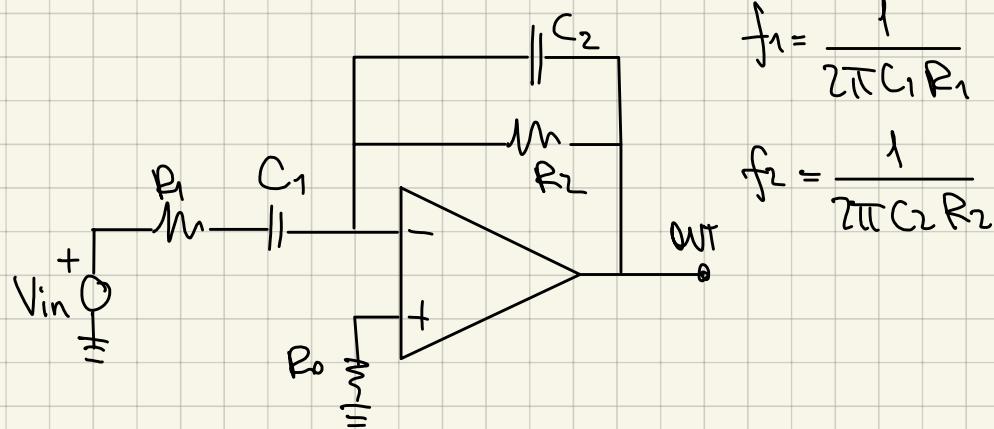


$$f_1 = \frac{1}{2\pi C_1 R_1}$$

$$f_2 = \frac{1}{2\pi C_2 R_2}$$

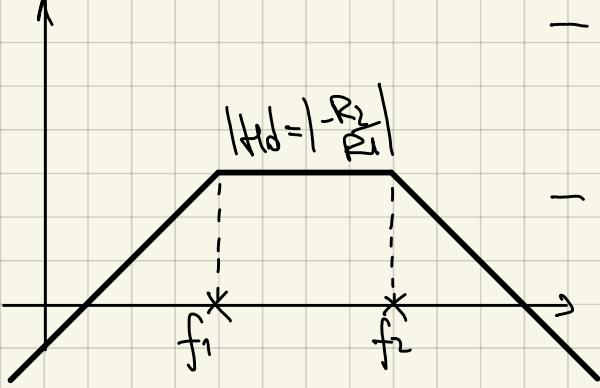- if $f_1 \ll f_2 \rightarrow \text{BSF} \Rightarrow$
 - if $f < f_1 \rightarrow G_1$ and G_2 are open
 - if $f_1 < f < f_2 \rightarrow G_1$ is short and G_2 is open
 $\rightarrow H_0 = -R_2/R_1$
 - if $f > f_2 \rightarrow G_1$ and G_2 are short



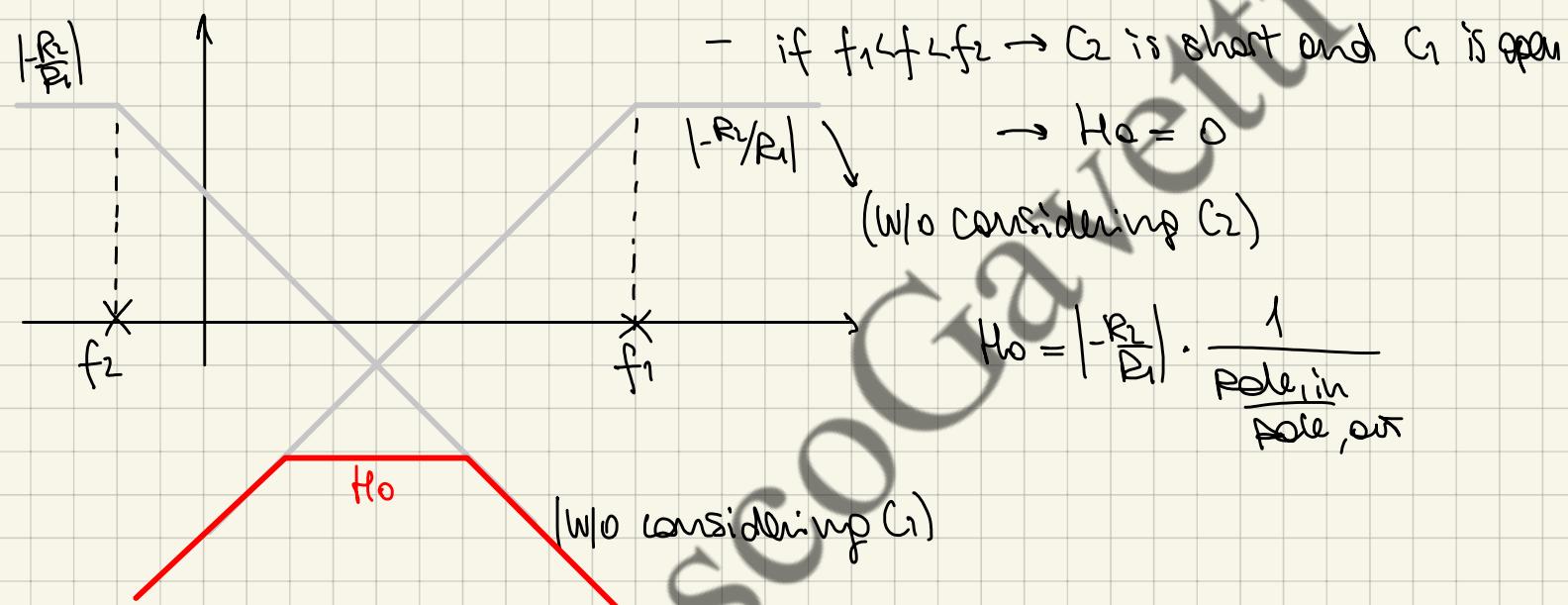- if $f_1 \gg f_2 \rightarrow \text{NOTCH} \Rightarrow$
 - if $f < f_2 \rightarrow G_1$ and G_2 are open
 - if $f_1 < f < f_2 \rightarrow G_2$ is short and G_1 is open
 $\rightarrow H_0 = 0$
 (w/o considering G_1)




CURRENT AND VOLTAGE CONVERTERS

- VOLTAGE - CURRENT CONVERTER (TRANSCONDUCTANCE AMPLIFIER)


~~Diagram of a simple voltage-current converter with a dependent source across a load resistor R_L .~~ \rightarrow This is a stupid converter b/c we are pretending that the voltage drop across the cell is zero
 \rightarrow DON'T USE IT!!

SOLUTION:

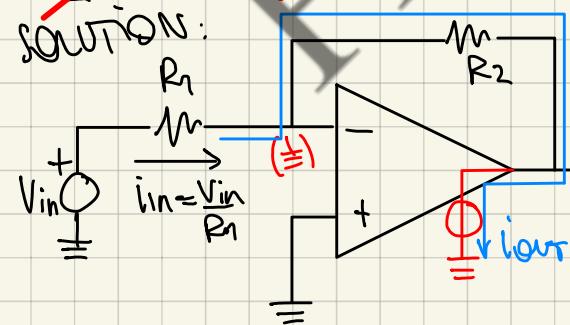


$$i_{out} = i_{in} = \frac{V_{in}}{R} \rightarrow i_{out} = \frac{1}{R} V_{in}$$

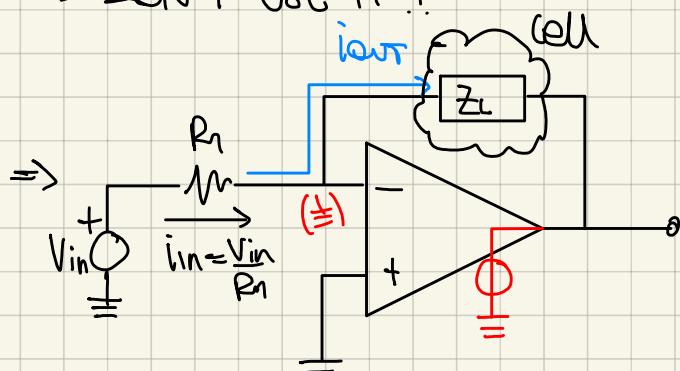ISSUE: if I_{in} is very high, then $I_{out,max} = I_{in}$, must be very high



\rightarrow If $I_{in} = 100\text{mA} \rightarrow I_{out,max} = 100\text{mA}$ and the op-amp must drink it, and it may not be able to do that


SOLUTION:

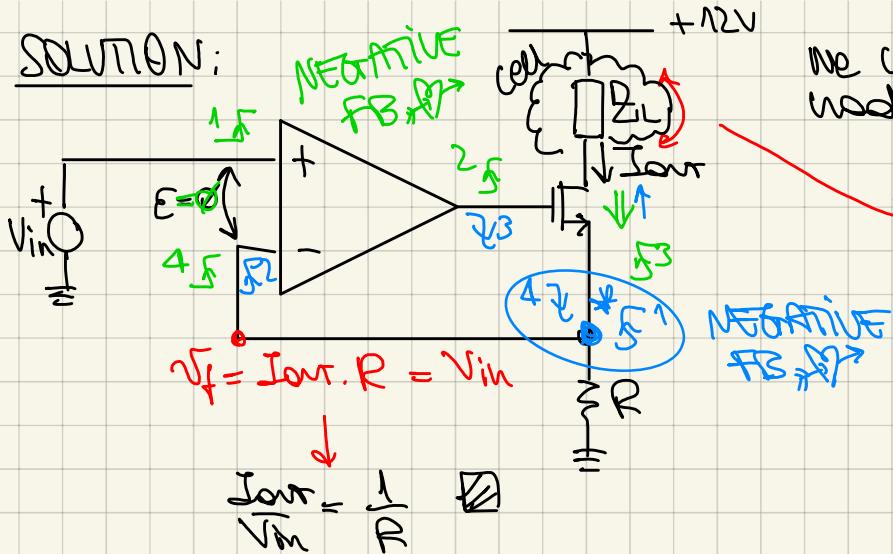


We can check The fb even @ another node inside The loop *

If The voltage across The load changes we don't care b/c The current flowing Through the loop is set by The fb and R

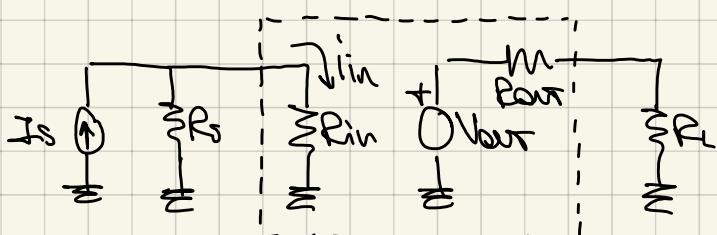• CURRENT-VOLTAGE CONVERTER (TRANSIMPEDANCE AMPLIFIER)




$$V_{out} = G_R I_{in}$$

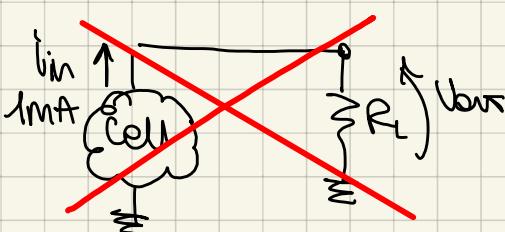

⇒ This is a stupid I-to-V converter, b/c if we used a huge load The voltage drop across the load and so also across the cell would be huge too and the cell could get destroyed

DON'T USE IT!!

SOLUTION:

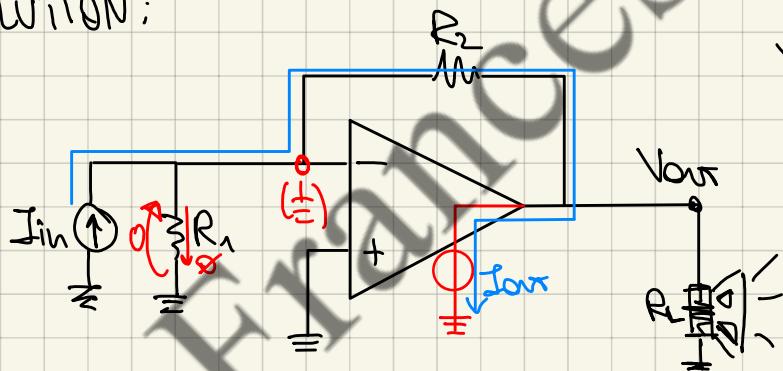


$$V_{out} = -I_{in} R_2$$

→ we can change R1 as we want b/c it has no effect on Vout

EXP AND LOG CONVERTER


• LOGARITHMIC AMPLIFIER

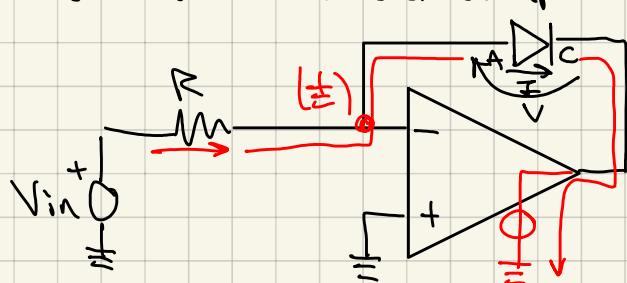Let's use a non-linear component (ex: a diode)



$$I_D = I_S (e^{\frac{V}{kT/q}} - 1)$$

I-V curve of a diode :

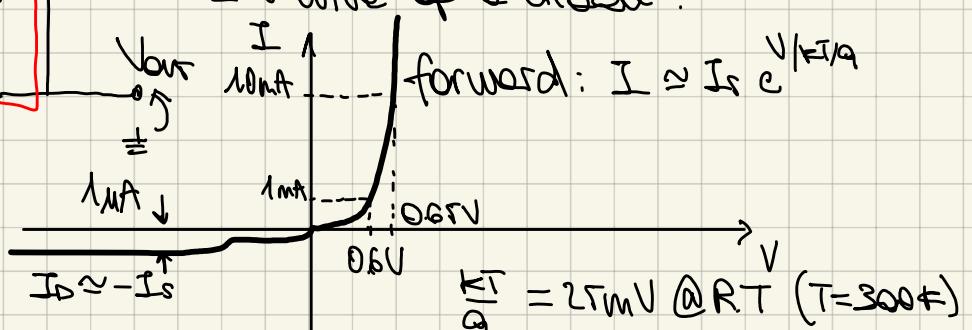


How does the circuit operate?

$$\text{if the diode is ON} \rightarrow V = 0.6V \rightarrow I_D = I_S (e^{\frac{V}{kTq}} - 1) \approx I_S e^{\frac{V}{kTq}}$$


$$\begin{cases} I_D = I_{in} \\ V = -V_{out} \end{cases} \Rightarrow \frac{V_{in}}{R} \approx I_S e^{-\frac{V_{out}}{kTq}} \Rightarrow V_{out} = -\frac{kT}{q} \ln \left(\frac{V_{in}}{R \cdot I_S} \right)$$

Notice: The output has a logarithmic dependence to what we apply @ the input (V_{in})

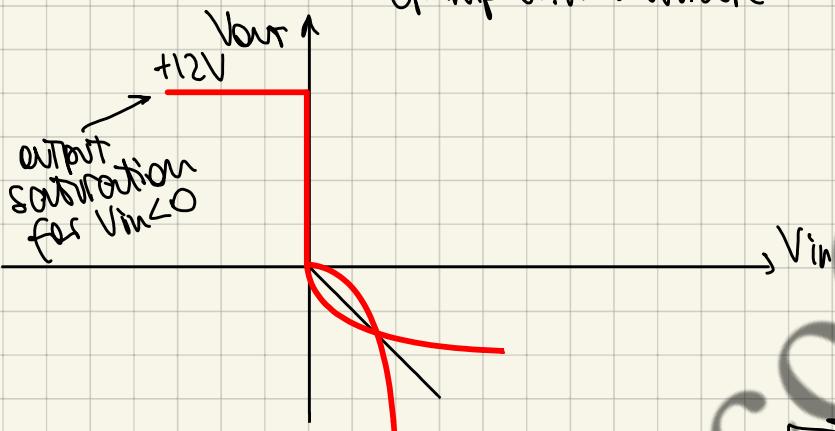
Beware: if $V_{in} < 0 \rightarrow$ The diode becomes reverse biased, The current should reverse but it cannot, bcz no current can flow in the opposite direction through the diode or better There is a current but it is almost constant, and The output of the OpAmp will saturate



Alternatives:

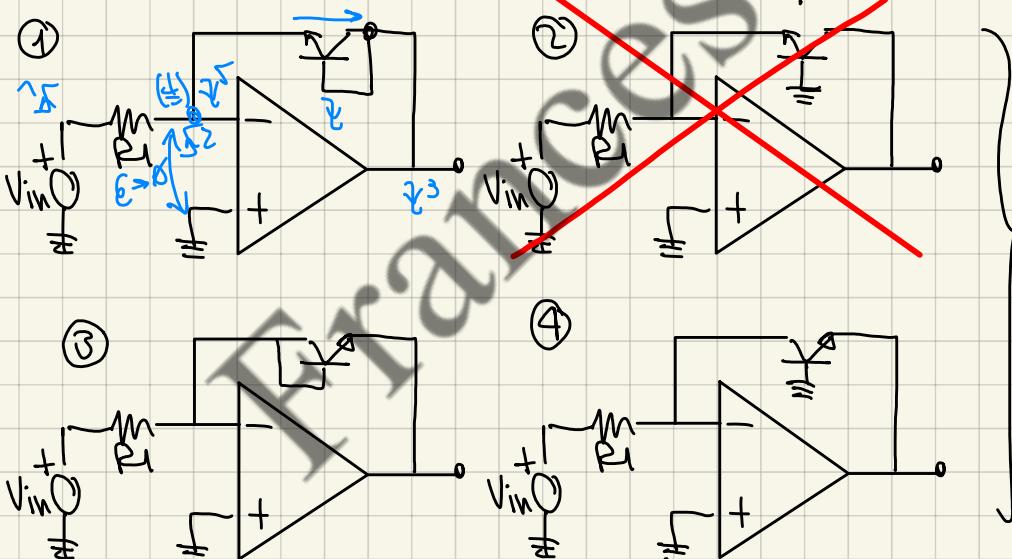

P-N-P

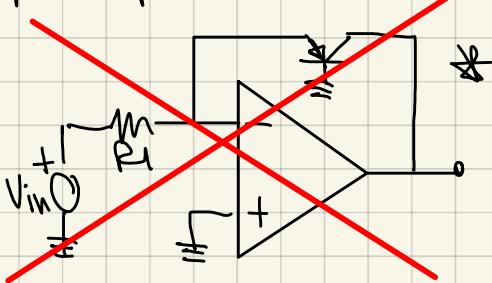


This circuit cannot work bcz whenever we apply something at the input, The output moves (and so the collector of the BJT), but the current cannot change. The current of the BJT changes only if we vary the V_{BE}


The best configuration is the 4th: it's preferred to keep the base at ground in such a way we can compensate the approximation on the current ($I_D = I_S (e^{V_{BE}/kT_A} - 1) \approx I_S e^{V_{BE}/kT_A}$)

In fact the collector current compared to the emitter one slightly differs, but there is also a base current: $I_E = I_C + I_S$ and $I_C = \beta I_S$

④

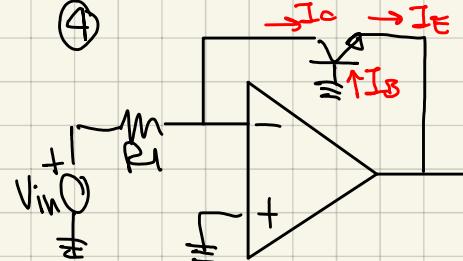

• EXPONENTIAL AMPLIFIER

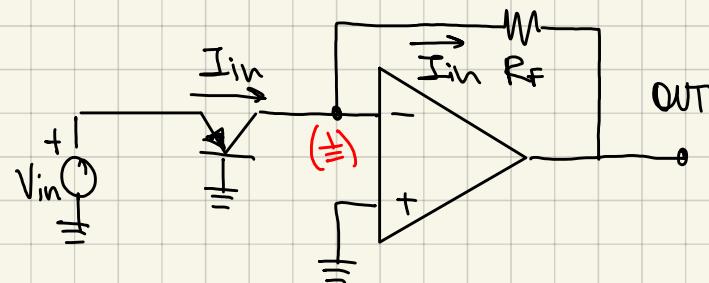


$$V_{out} = -I_{in} R_f = -R_f I_s e^{\frac{V_{in}}{kT_A}}$$



VOLTAGE MULTIPLIER = a. we convert the voltages into logarithms through LOGARITHMIC AMPLIFIERS



b. we sum up the logarithms through a simple ADDER

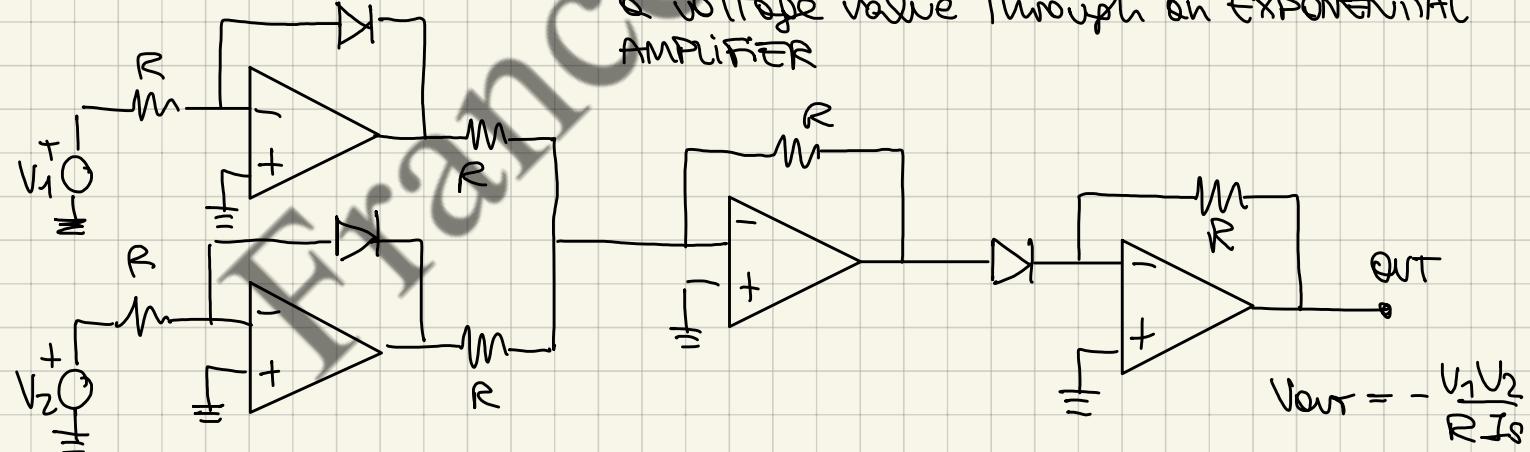
c. we convert again the resulting logarithmic into a voltage value through an EXPONENTIAL AMPLIFIER



Up to now we considered small signals, but we can also operate these stages w/ large signals (non-DC signals (AC)).


RECTIFIER

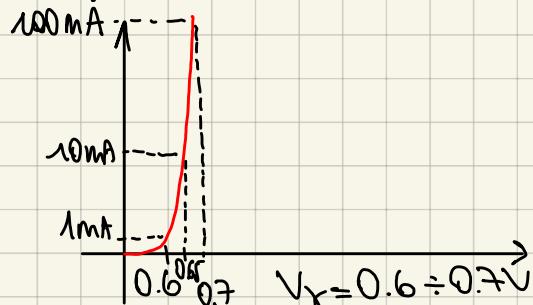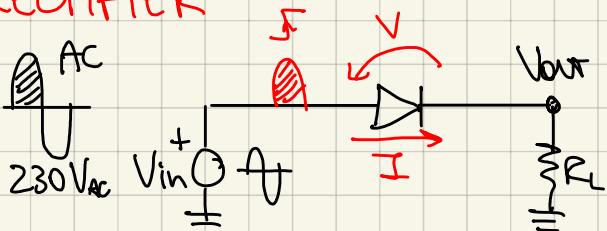

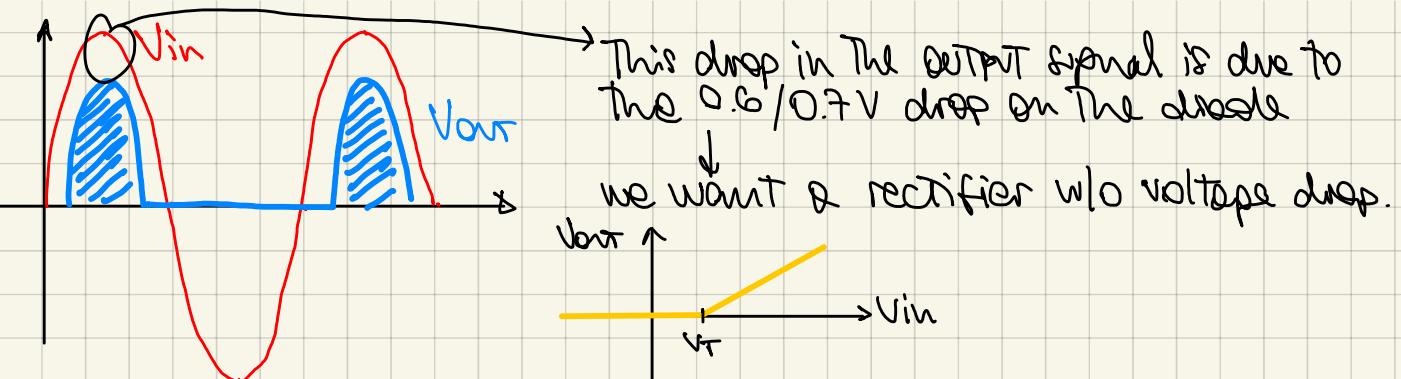

The solution to this issue is known as PRECISION RECTIFIER (or SUPER DIODE)

PRECISION RECTIFIER (SUPER DIODE)

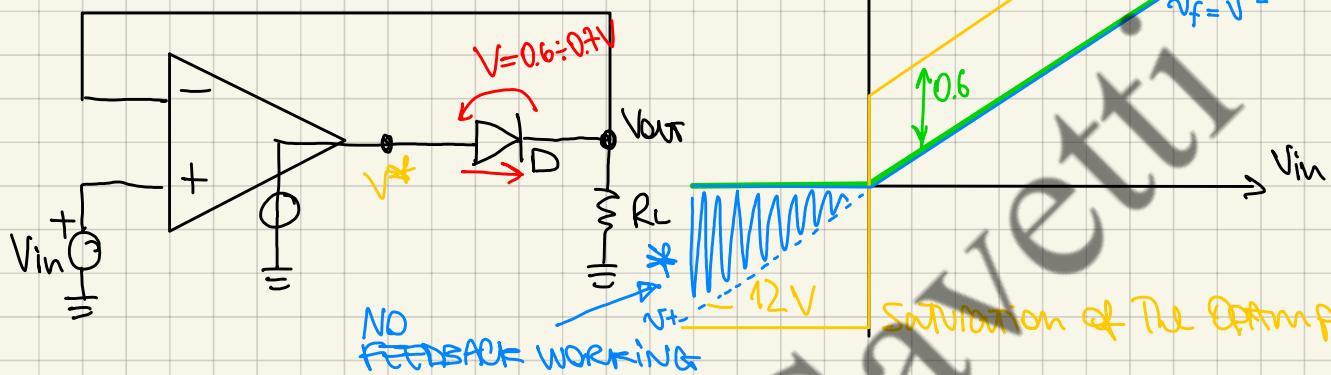

- when $V_{in} > 0 \rightarrow D: ON \rightarrow V_{out} = V_{in} - V_f \quad \& \quad V^* = V_{out} + 0.6V$

- when $V_{in} < 0 \rightarrow$ The diode stops the current flow $\rightarrow V_{out} = 0 = V_f$

$V^* \rightarrow$ goes to a very negative value but it tries to force the diode to reverse the current (ideally $V^* \rightarrow -\infty$), but the current cannot flow to the opposite direction so V^* saturates to the most negative power supply (-12 V)


$\rightarrow V^* = -12 \text{ V}$

* when $V_{in} < 0$ There is a voltage diff. b/w V^* and V^- which means that the feedback doesn't work

Notice: it's called super diode b/c the voltage drop b/w V_{in} and V_L is 0V


How can we avoid the saturation of the opamp?

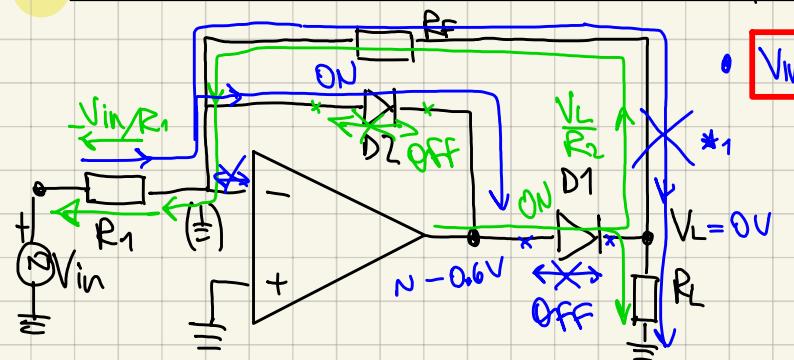① SUPER DIODE INVERTING RECTIFIER W/O SATURATION OF THE OPAMP





* $V_{in} > 0 \Rightarrow D_1: OFF \rightarrow R_F \text{ is in series w/ } R_L$
 $D_1: ON \rightarrow R_F \text{ is in parallel w/ } R_L$


* $V_L = 0V$

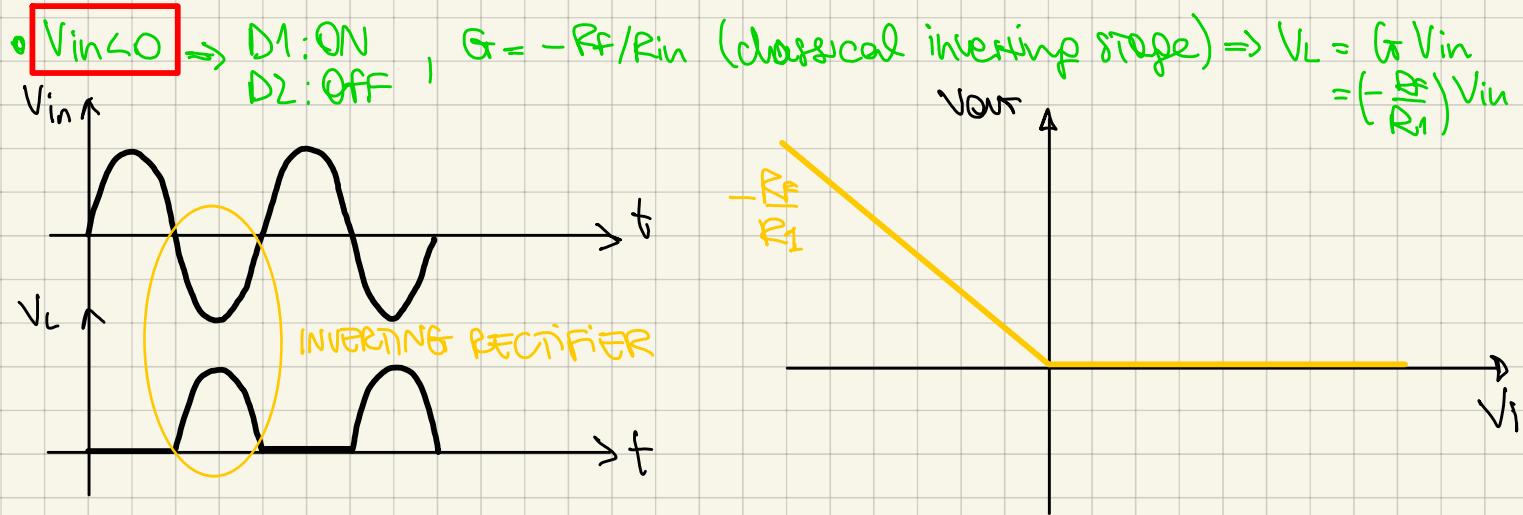

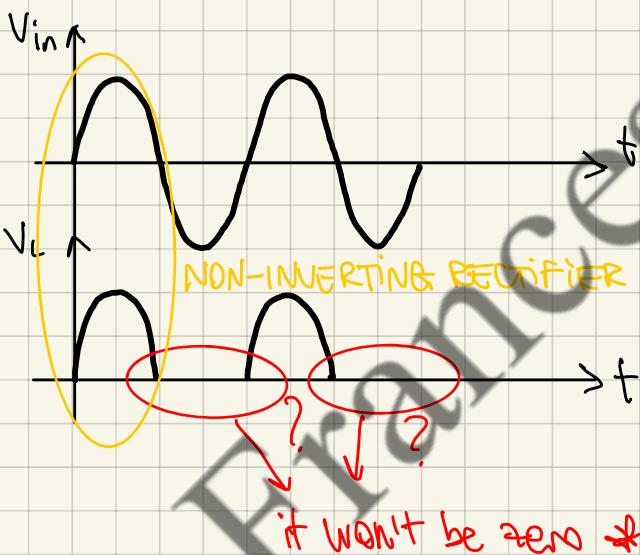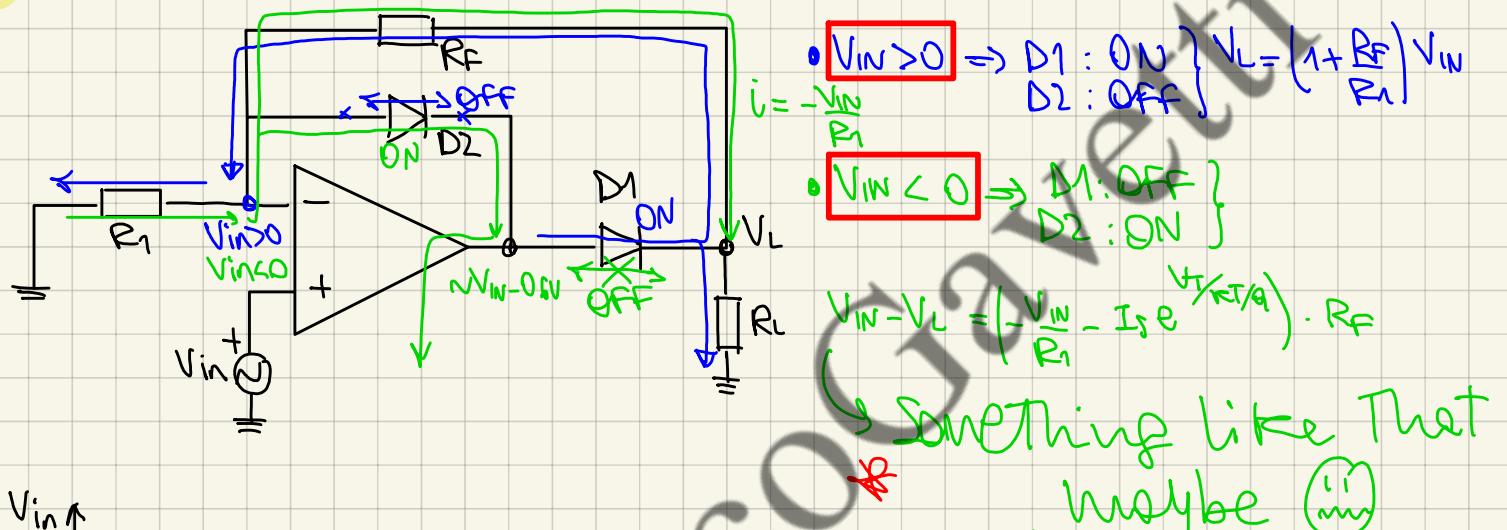② SUPER DIODE NON-INVERTING RECTIFIER w/o SATURATION OF THE OPAMP





③ SUPER DOUBLE-RECTIFIER

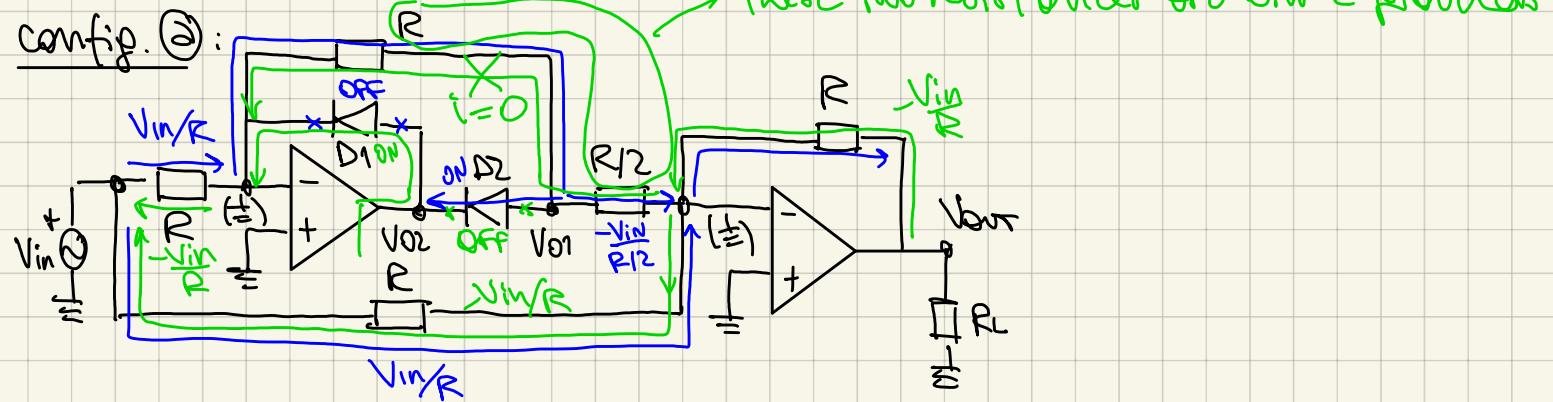

• $V_{in} > 0$: D1: OFF , D2: ON , $V_{O1} = \left(-\frac{R_2}{R}\right) V_{in} = -V_{in}$, $V_{out} = -\left(-\frac{V_{in}}{R/2} + \frac{V_{in}}{R}\right) R$
 $= V_{in} R \left(\frac{2}{R} - \frac{1}{R}\right) = V_{in}$

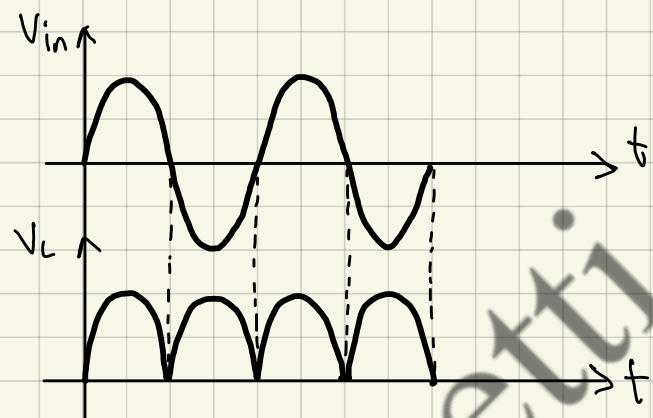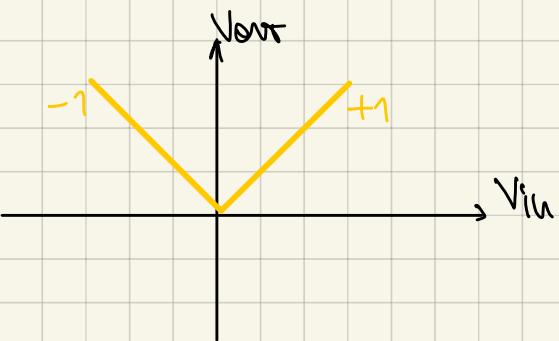• $V_{in} < 0$: D1: ON , D2: OFF , $V_{O2} \approx -0.6V$, $V_{out} = \left(-\frac{V_{in}}{R}\right) \cdot R = -V_{in}$



config. (b)

config. (c)


COMPARATORS (DISCRIMINATORS) (NO FEEDBACK)

① ONE-THRESHOLD DISCRIMINATOR (LEVEL DETECTOR)



When V_s is very close to V_r , if we move a little bit V_s compared to V_r we get a strong amplification.

Application:

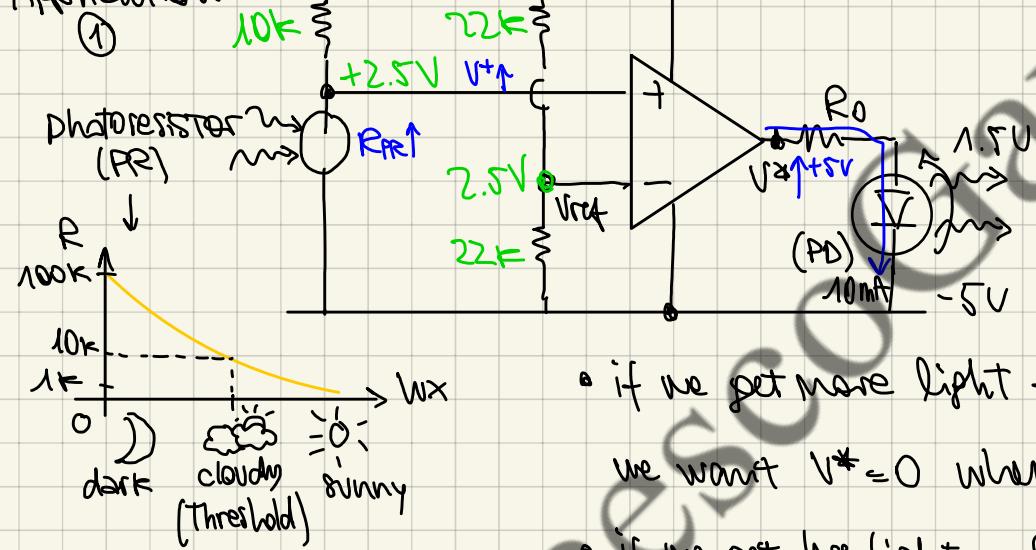

• if we get more light $\rightarrow R_{PR} \downarrow \rightarrow V^+ \downarrow$

we want $V^* = 0$ when $V^+ < V_{ref}$


• if we get less light $\rightarrow R_{PR} \uparrow \rightarrow V^+ \uparrow \rightarrow V^* \uparrow$

\rightarrow we can set R_o in order to have the proper current we wish:


$$R_o = \frac{5 - 1.5}{10\text{mA}} \approx 350\Omega$$

Now let's suppose we want to check the battery's charge level of our motor bike


②

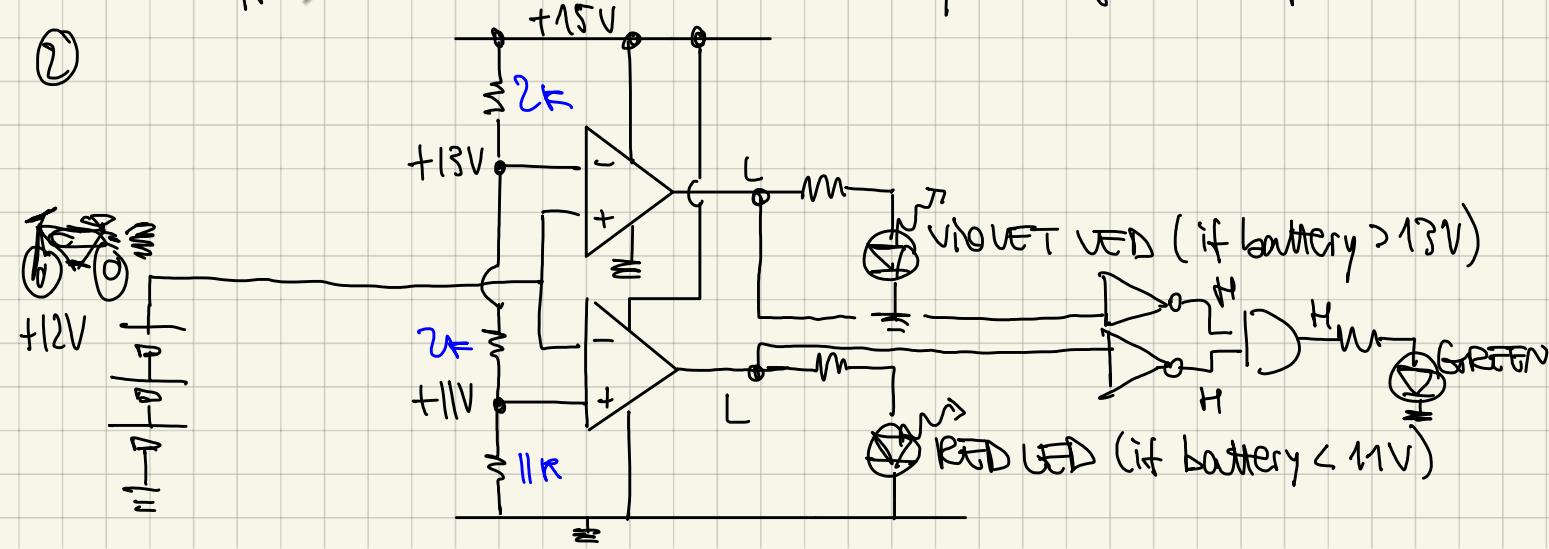

better solution :

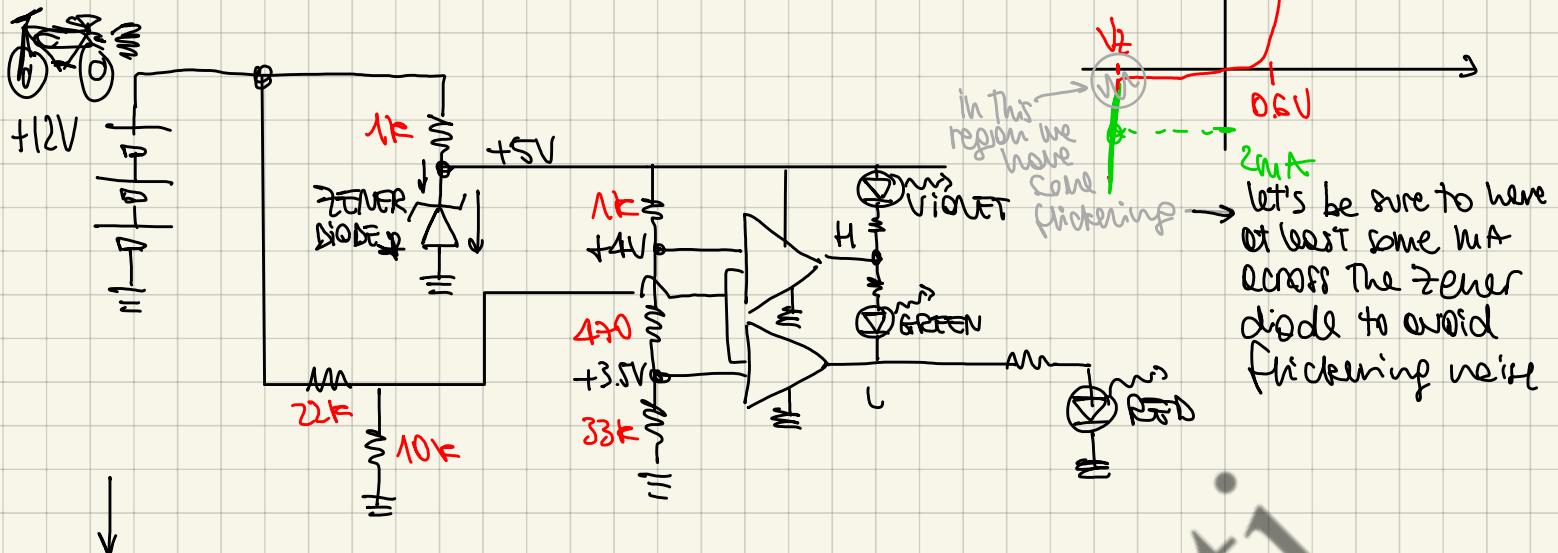

• TWO-THRESHOLDS DISCRIMINATOR ("WINDOW COMPARATOR")

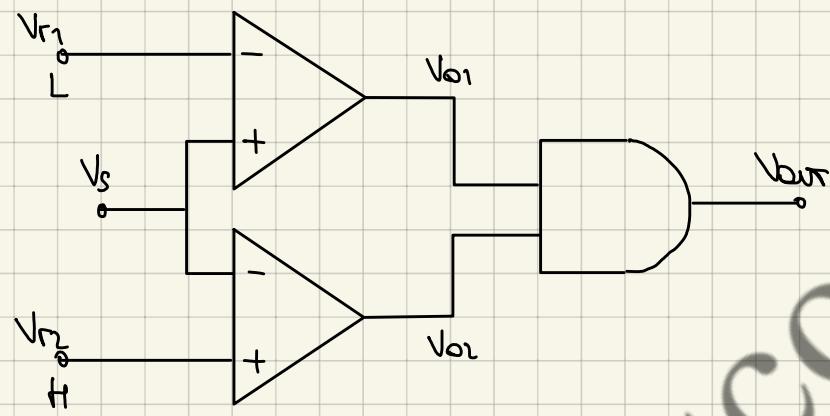


ES03 - OPAMP STAGES (3)

23/09/2021

SQRT AMPLIFIER

NEGATIVE FB

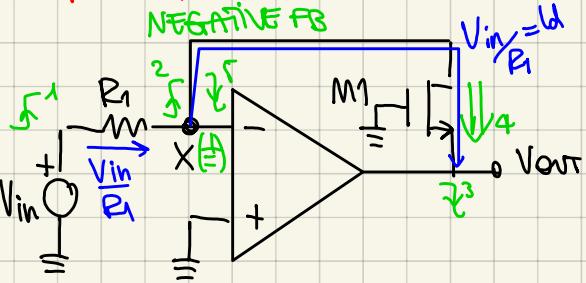

$$|id|_{sat} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{Th})^2$$

$$V_{GS} - V_T = V_{GS}$$

$$\frac{V_{in}}{R_1} = id$$

$$id = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{GS} - V_{in})^2 \Rightarrow \frac{V_{in}}{R_1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (-V_{out} - V_{Th})^2$$

$$V_{GS} = 0$$

$$V_S = V_{out}$$

$$V_{out}^2 + V_{Th}^2 - 2V_{Th}V_{out} - \frac{V_{in}}{\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 R_1} = 0$$


$$V_{out}^2 - 2V_{Th}V_{out} + V_{Th}^2 - \frac{V_{in}}{\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 R_1} = 0$$

$$V_{out,1/2} = \frac{V_{Th} \pm \sqrt{V_{Th}^2 - V_{in}^2 + \frac{V_{in}}{\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 R_1}}}{2}$$

DC term

POWER-2 AMPLIFIER


NEGATIVE FB

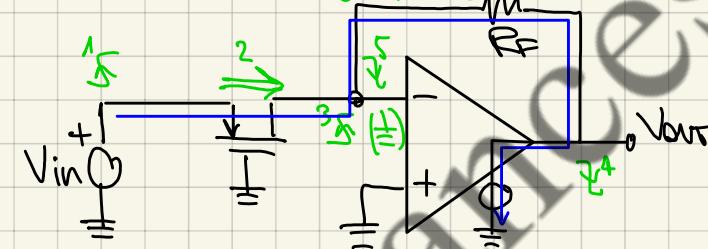

$$|id|_{sat} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_p (V_{SG} - |V_{Tp}|)^2$$

$$V_{out} = -id \cdot R_f$$


$$= -\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_p (V_{in} - |V_{Tp}|)^2$$

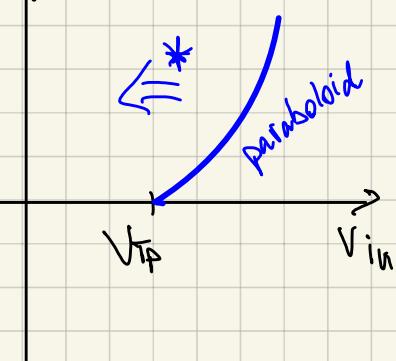


$$\text{if } |V_{Tp}| = |-0.4|V \rightarrow V_{SG} > |V_{Tp}| \Rightarrow V_{in} > 0.4V$$

\exists channel condition

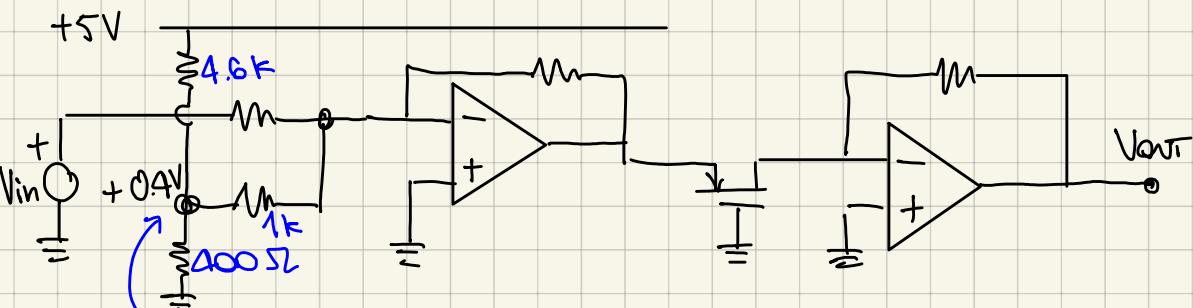* Notice : if we want to bring this paraboloid back to zero, so we have to play some trick in order to make Vin able to be @ 0V



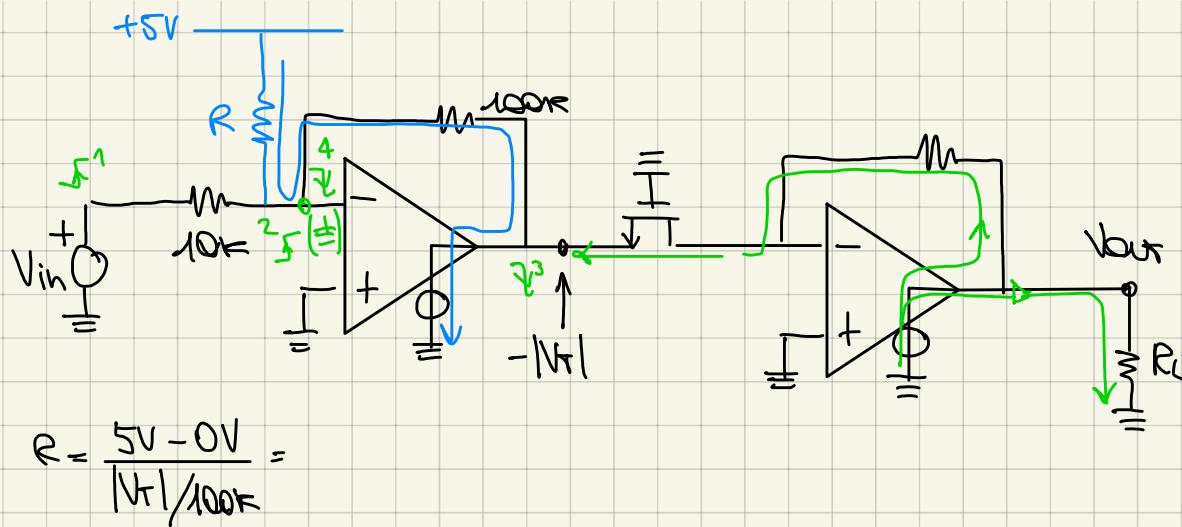
$$5V \cdot \frac{400\Omega / 1k}{400\Omega / 1k + 1k + 4.6k} \approx 0.3 \dots$$




NEED OF HISTERESIS COMPARATOR → SCHMITT TRIGGER

We have previously seen:

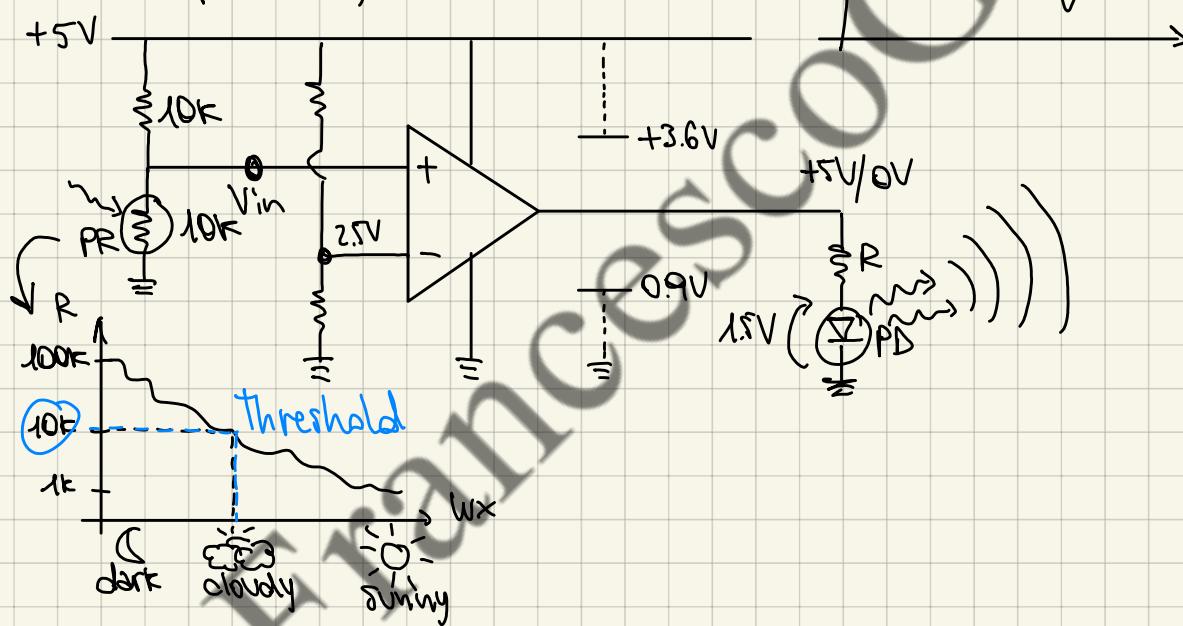

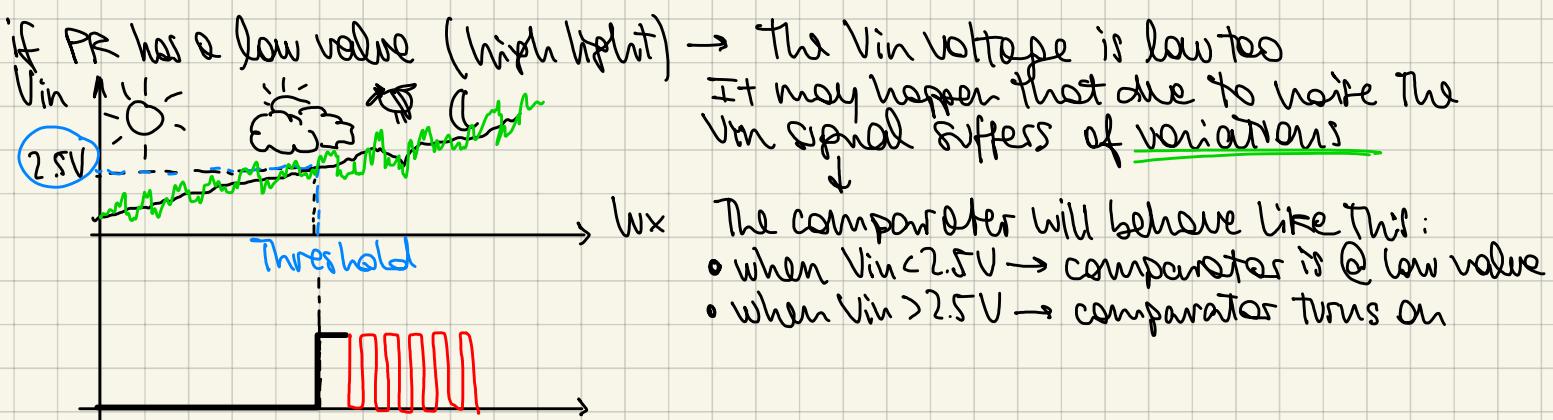All the comparators presented so far suffer of a big issue: They all have a single voltage reference for threshold switching and so they suffer noise and other stuff... let's see!!




But if the LED turns on, it produces light and this light could introduce a negative FB to the PR itself

if there is more light → PR decreases its value and so V_{in}
 → so the comparator turns off
 → the LED turns off
 → PR increases again and so V_{in}
 → the comparator turns on again

To avoid this undesired effect (undesired commutations) must be avoided and to do so, we should use two thresholds

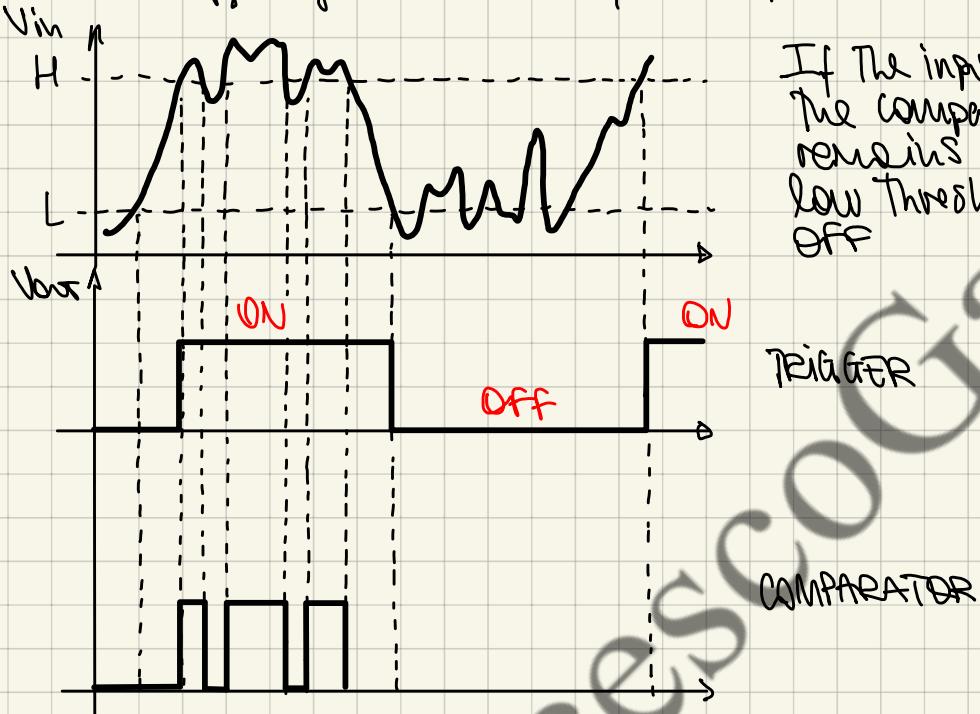To avoid triggering "undecisions", let's implement two switching thresholds:




If the input signal passes the high threshold, the comparator turns ON and it remains ON till it does not pass the low threshold, at that point it turns OFF

How can we design such a comparator?

Let's set the previous comparator → To add the second threshold we have just to add a positive FB

• INVERTING SCHMITT TRIGGER

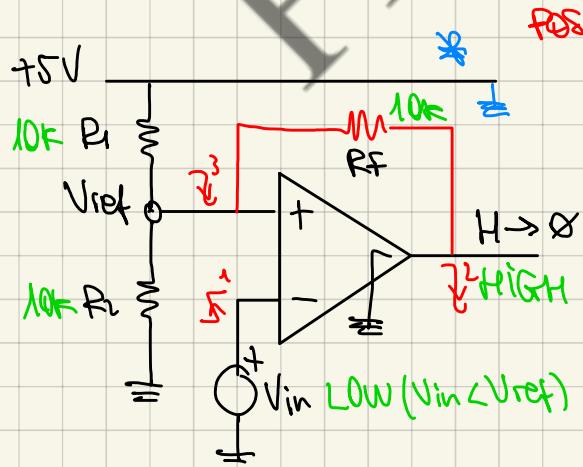

POSITIVE FB

$$V_{ref} = +5V \quad \frac{R_1}{R_1 + R_2} = 2.5V$$

$$\left\{ \begin{array}{l} V_L = +5V \quad \frac{R_2 || R_F}{R_2 || R_F + R_1} = 1.7V \\ R_2 || R_F + R_1 \end{array} \right. \quad (\text{when output is low } NO)$$

$$V_H = +5V \quad \frac{R_2}{R_2 + R_1 || R_F} = 3.4V \quad (\text{when output is high } SV)$$

HYSTÉRISE $H = \Delta = V_H - V_L$

The hysteresis is caused by the variation of V_{out} which varies from $0 \rightarrow 5V$

How can we compute it?


$$\rightarrow \text{let's turn off the PS} \Rightarrow H = 5V \frac{R_1||R_2}{R_1||R_2 + R_F}$$

$$\text{if we decide } \begin{cases} \Delta \ll V_H \text{ where } V_H = 2.6V, V_L = 2.4V \rightarrow \Delta = 0.2V \\ \Delta \ll V_L \end{cases}$$


$$\rightarrow \text{if } \Delta \text{ is small} \rightarrow R \ll R_1, R_2 \rightarrow H = \Delta \approx 5V \frac{R_1||R_2}{R}$$

Instead of applying Q system w/ 3 unknowns

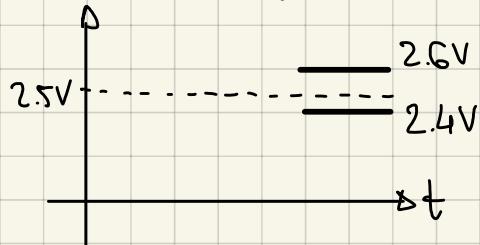Simplified setting of The Schmitt Trigger





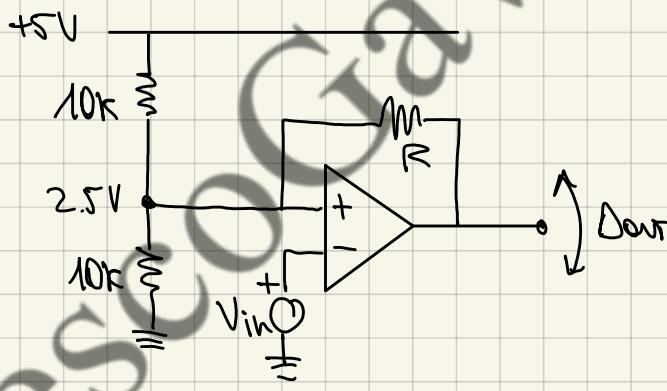1. Create The threshold
2. Apply The threshold To The positive input of The OpAmp
3. Apply The hysteresis adding R in positive loop
4. The hysteresis we want to apply is:





$$\Delta \approx \text{Dout} \cdot \frac{R_1||R_2}{R} \rightarrow 0.2 \approx 5 \cdot \frac{5k}{R} \rightarrow R = \frac{5V}{0.2V} \cdot 5k = 125k\Omega$$

Output swing

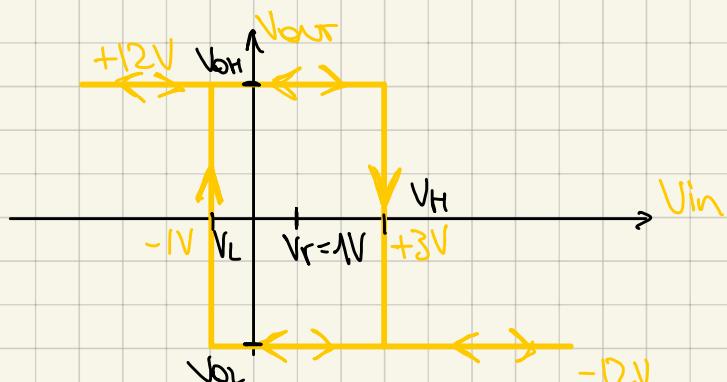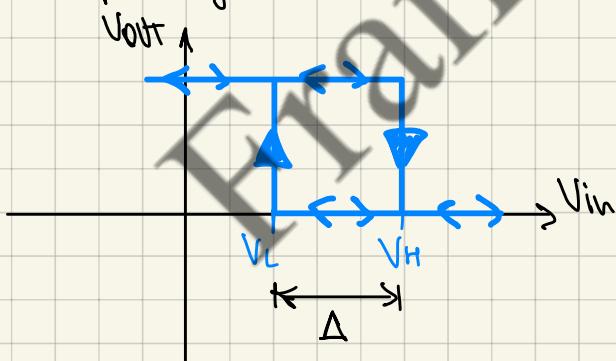

• NON-INVERTING SCHMITT TRIGGER

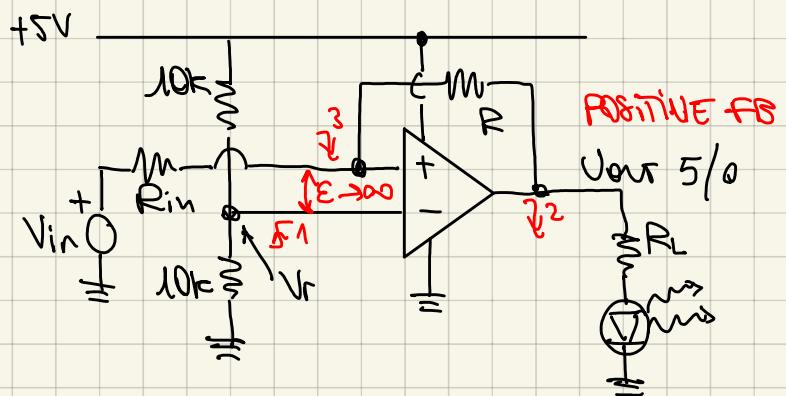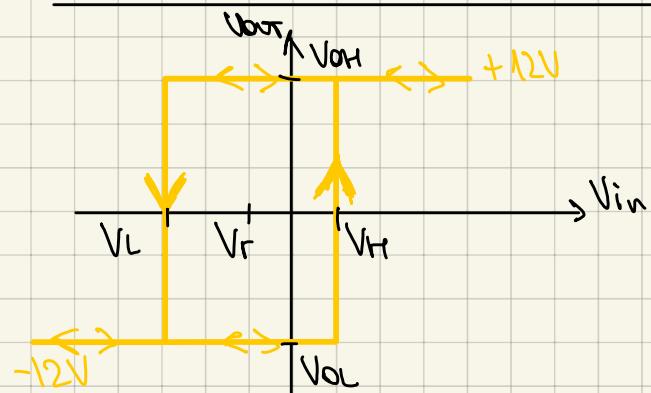


The feed back is positive, but if by chance $V_t = V_{ref}$:

$$I_{ref} = \frac{V_{in} - V_{ref}}{R_{in}} = I_F = \frac{V_{ref} - V_{out}}{R} \quad \text{where } V_{out} = \begin{cases} 5V & V_{out} > V_{ref} \\ 0V & V_{out} < V_{ref} \end{cases}$$

- if $V_{out} = 5V \rightarrow \frac{V_{in} - V_{ref}}{R_{in}} = \frac{V_{ref} - 5V}{R} \rightarrow V_H =$
- if $V_{out} = 0V \rightarrow \frac{V_{in} - V_{ref}}{R_{in}} = \frac{V_{ref} - 0V}{R} \rightarrow V_L =$

EXERCISE 1

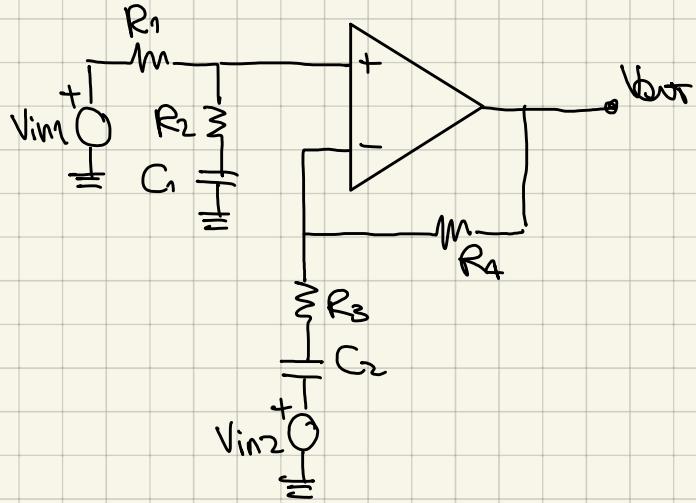


$$R_1 = 20\text{k}\Omega, R_2 = 30\text{k}\Omega, R_3 = 1\text{k}\Omega, R_4 = 10\text{k}\Omega$$

$$C_1 = 200\text{nF}, C_2 = 1\text{nF}$$

$$A_0 = 10^6 \quad I_S = 10\text{nA} \quad f_0 = 10\text{Hz}$$

① FEEDBACK CHECK

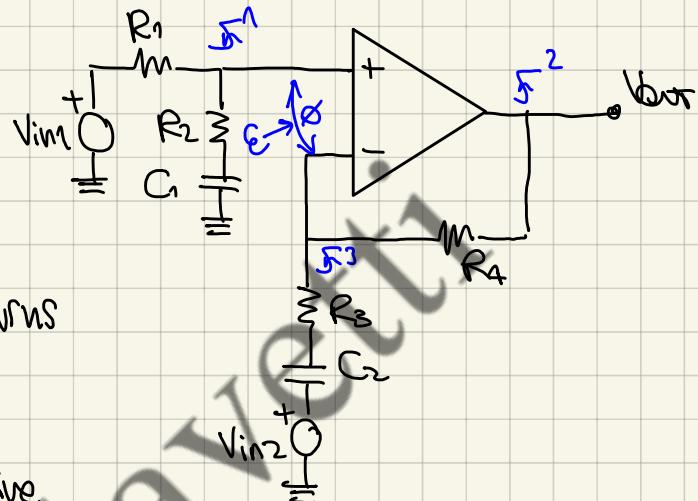

Notice: if in the FB path there are just passive components and it returns to the $(-)$ pin
→ The ~~FEEDBACK~~ is NEGATIVE

if in the FB path there are active components (transistors, optoisos, etc)
even if the FB path returns to the $(-)$ pin
→ we have to check it !!!


In this case it's evident that the FB is NEGATIVE but we can check it anyway

② ASYMPTOTIC ANALYSIS

Notice: we can notice that we have two inputs and that the circuit can be divided in two stages

Let's study the behavior of the circuit considering the two inputs separately

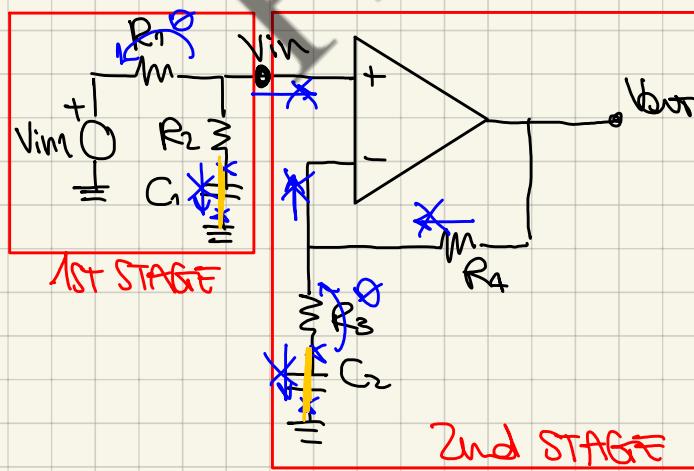(A) V_{in1} → let's short V_{in2} → Then let's study the two stages separately



• 1st STAGE

$$@DC \rightarrow C \text{ open} \rightarrow \frac{V_{in}(0)}{V_{in}} = 1$$


$$@HF \rightarrow C \text{ short} \rightarrow \frac{V_{in}(\infty)}{V_{in}} = \frac{R_2}{R_1 + R_2} = 0.6$$

• 2nd STAGE

$$@DC \rightarrow C \text{ open} \rightarrow \frac{V_{out}(0)}{V_{in}} = 1$$

$$@HF \rightarrow C \text{ short} \rightarrow \frac{V_{out}(\infty)}{V_{in}} = 1 + \frac{R_4}{R_3} = 11$$

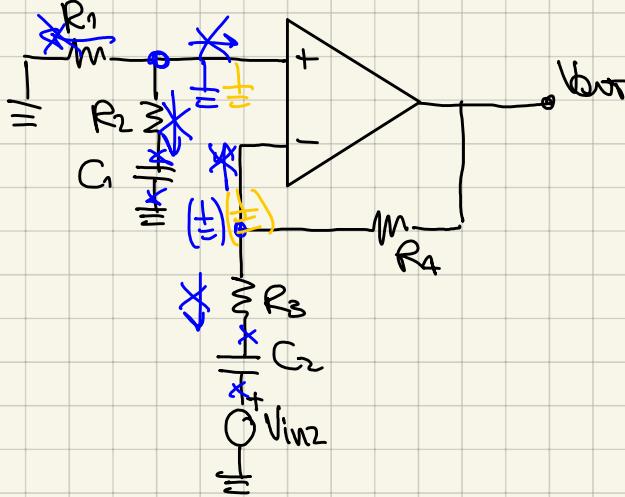(B) V_{in2} \rightarrow let's short V_{in1} \rightarrow Notice: how there's just one stage to consider




$$@DC \rightarrow C \text{ open} \rightarrow \frac{V_{out}(0)}{V_{in2}} = 0$$

@HF \rightarrow C short \rightarrow INVERTING STAGE

$$\rightarrow \frac{V_{out}(\infty)}{V_{in2}} = -\frac{R_4}{R_3} = -10$$

③ POLES & ZEROS

(A) V_{in1}

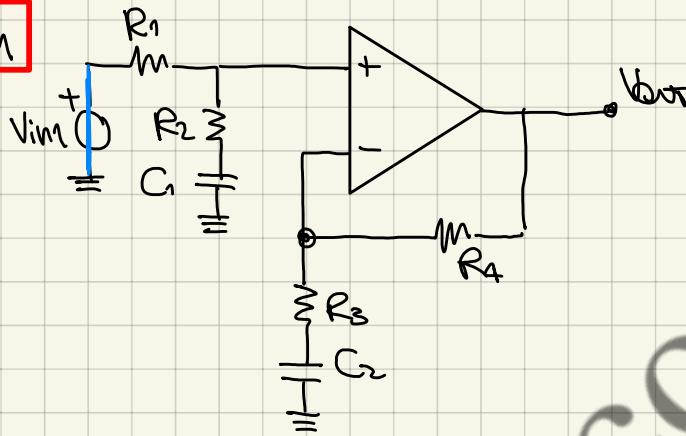

• POLES: \rightarrow x Short all the generators

- x compute the equivalent resistance seen by the capacitor
 - \hookrightarrow so we should replace the capacitor under investigation w/ a test generator ex: $\frac{i_{C1}}{V_{C1}}$


$$f_{p1} = \frac{1}{2\pi C_1 (R_1 + R_2)} = 16 \text{ Hz}$$

$$f_{p2} = \frac{1}{2\pi C_2 R_3} = 160 \text{ kHz}$$

• ZEROS:

x METHOD 1 = "BY CALCULUS"

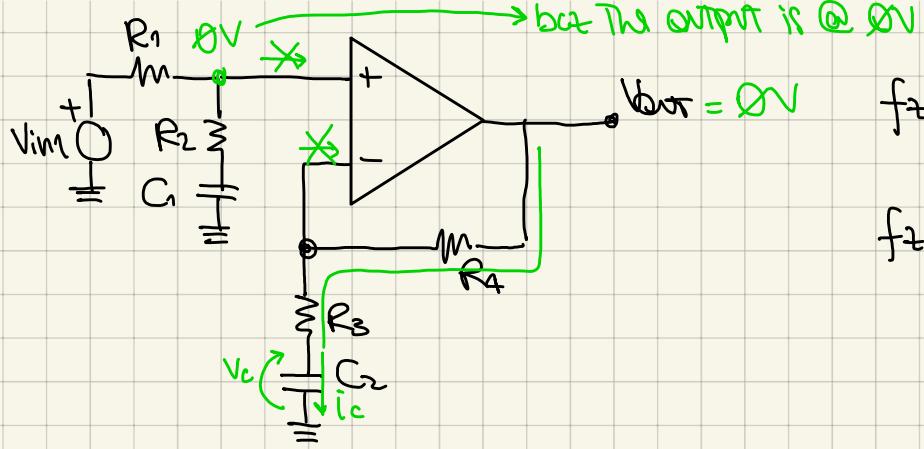- put the output @ 0V
- keep the signal generator
- replace the capacitor under investigation w/ a test generator and compute the resistance seen by the capacitor / the generator




$$f_{z1} = \frac{1}{2\pi C_1 R_2} \approx 27 \text{ Hz}$$

$$f_{z2} = \frac{1}{2\pi C_2 (R_3 + R_4)} \approx 14.5 \text{ kHz}$$


METHOD 2 = "GRAPHICALLY"

1st STAGE

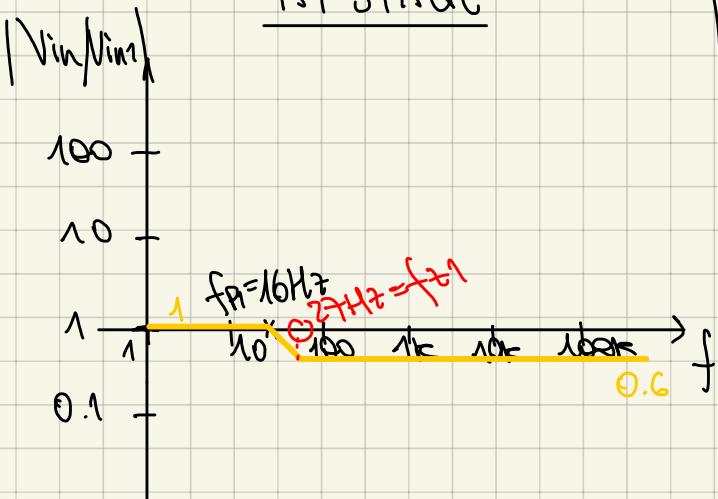


$$f_{z1} = f_P1 / 0.6 = 27 \text{ Hz}$$

2nd STAGE

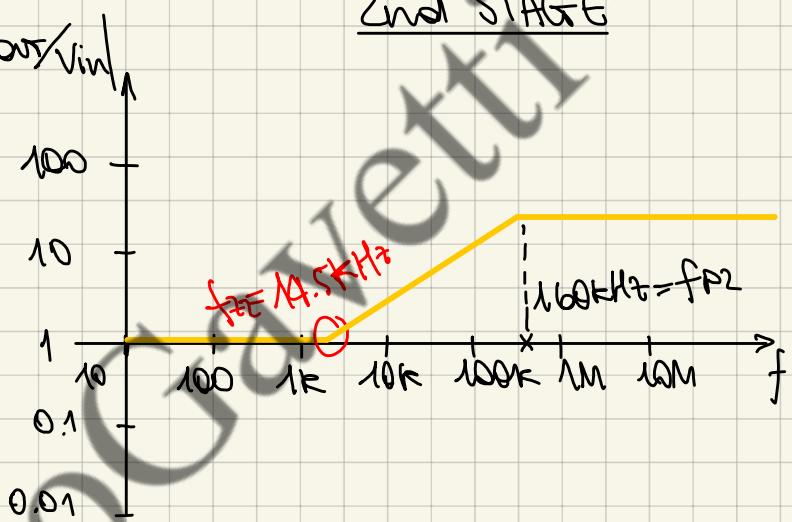


$$f_{z2} = f_P2 / 11 = 160 \text{ kHz} / 11 = 14.5 \text{ kHz}$$

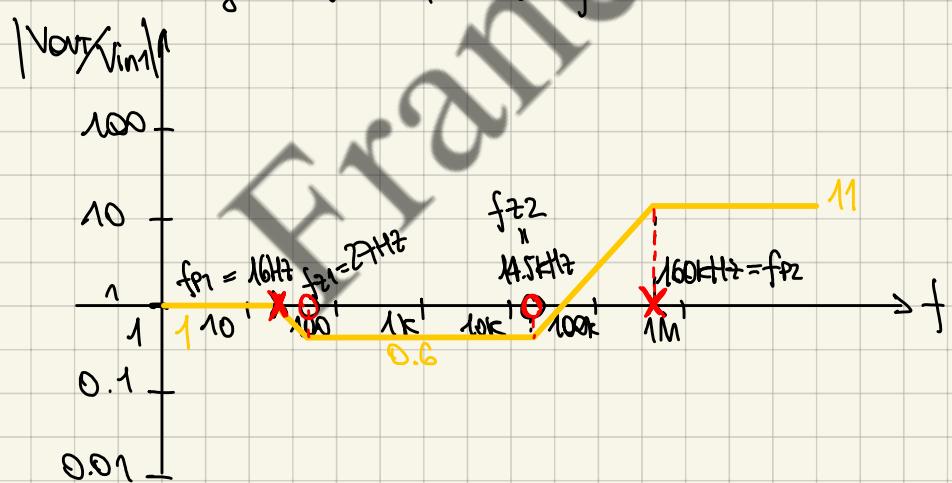In conclusion for The 1st Sallen generator we can plot The final Bode diagram in This way:



(B) V_{in2}

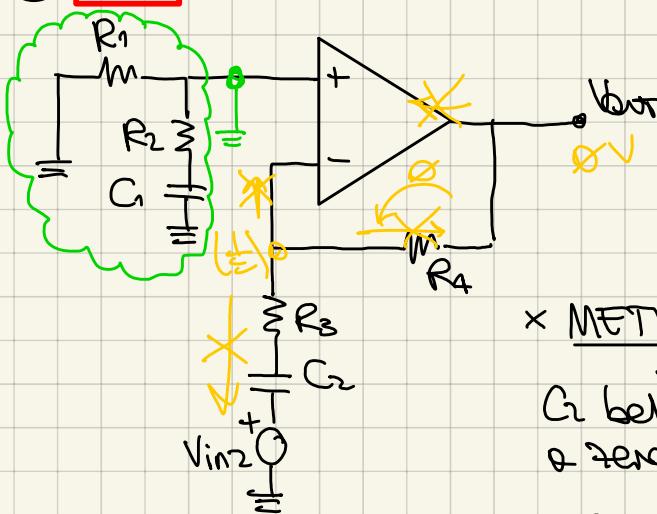

• POLVES:

$$f_{p2} = \frac{1}{2\pi C_2 R_3} = 160\text{Hz}$$

• ZEROS:


× METHOD 1 := "THEORETICALLY"

G belongs to the signal path so it introduces a zero @ $f=0$

$$\rightarrow f_{z2} = 0\text{Hz}$$

× METHOD 2 := "BY COMPUTATION"

× METHOD 3 := "GRAPHICALLY"

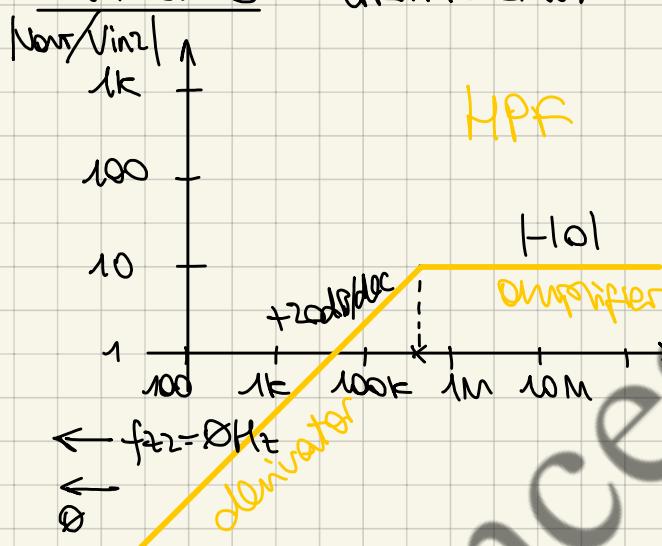

from the graph it's easy to see that there must be a zero @:
 $f_{z2} = 0\text{Hz}$.

$$+20\text{dB/dec} \rightarrow \text{BW} = f_{p2}/10 = 160\text{Hz}$$

EXAMPLE ②

Calvin measures his bike's speed s , by employing Hobbe's speedometers ($V_s = s \cdot 50\text{mV/m/s} + 200\text{mV}$) and 10V FJR voltmeters

(A) Design a circuit for displaying the speed, up to 40km/h, w/ 3s smoothing.

$$s_{FSR} = 40\text{km/h} \leftrightarrow V_{s,FSR} = 10\text{V}$$


$$V_s = 40\text{km/h} \cdot 50\frac{\text{mV}}{\text{m/s}} + 200\text{mV} \cdot G = 10\text{V}$$

Let's neglect this term → we'll design a circuit in order to cancel out this DC term

$$\rightarrow V_s = 40 \cdot \frac{1000\text{m}}{3600\text{s}} \cdot \frac{50\text{mV}}{\text{m/s}} = 555\text{mV} \cdot G = 10\text{V}$$

I need an amplification to reach 10V of FJR
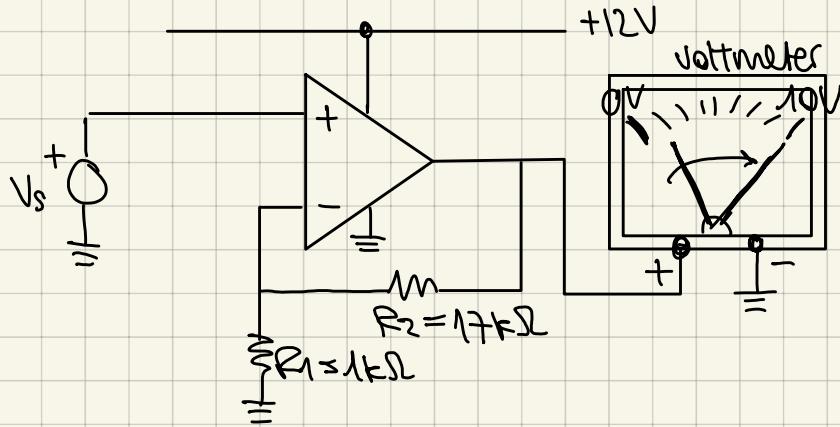
$$G = \frac{10V}{550mV} \approx 18 \rightarrow I need to design an amplifier w/ this gain$$



it's a non-inverting stage


$$A_O = 1 + \frac{R_2}{R_1} = 18$$

$$\rightarrow \frac{R_2}{R_1} = 17 \rightarrow \begin{cases} R_2 = 17k\Omega \\ R_1 = 1k\Omega \end{cases}$$


Beware: set the PS b/w +12V and 0V, b/c if we set the PS b/w [+12V, -12V] we run the risk to burn the Opamp b/c we apply a voltage which is outside the CMVR

Can we limit the input in order to not become negative?

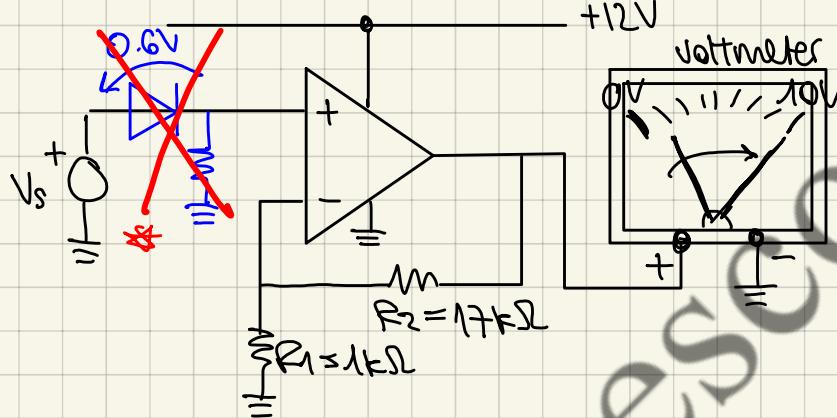↳ let's use a diode → only a positive signal will pass through it



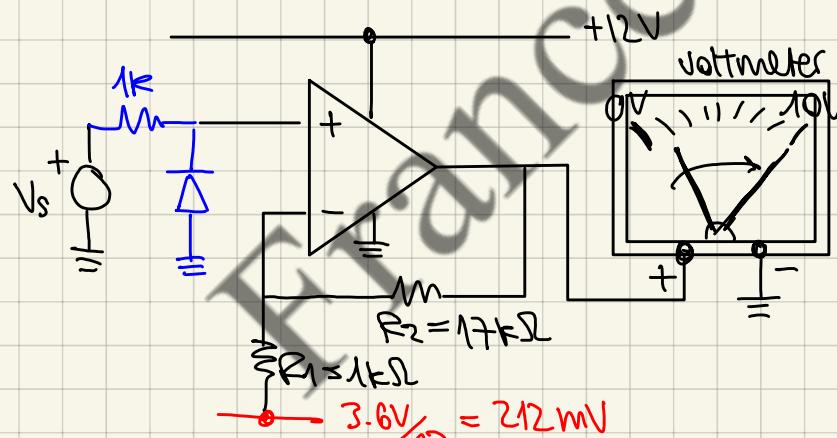* But we don't like this solution b/c in this way we lose 0.6V and we cannot afford it





Now we have to find a way to cancel the 200mV DC

$$200mV \cdot 18 = 3.6V$$


at the output we have to subtract 3.6V in order to remove the 200mV DC value in input

↳ Do we have to use a battery? NO!!

SOLUTION ①

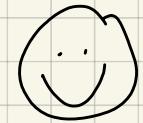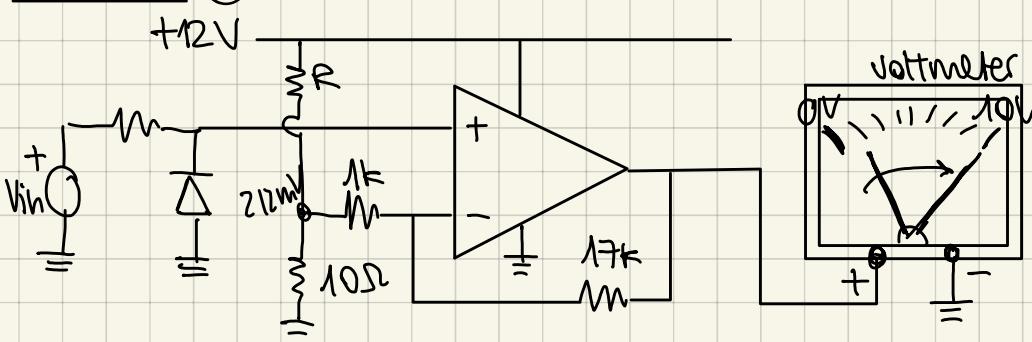


SOLUTION ②

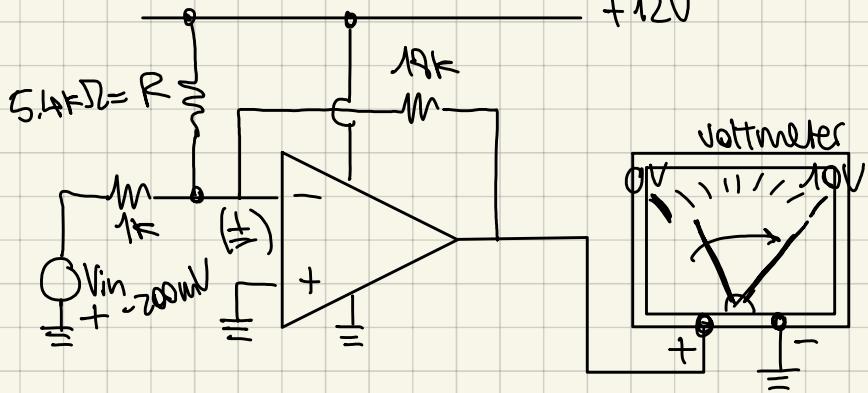


$$\frac{12V - 0V}{R} \cdot 18k = 3.6V$$
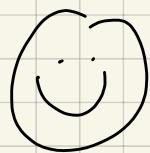
$$R = \frac{3.6}{12} \cdot 18k = 54k\Omega$$



Francesco Gavetti


EXAMPLE ③

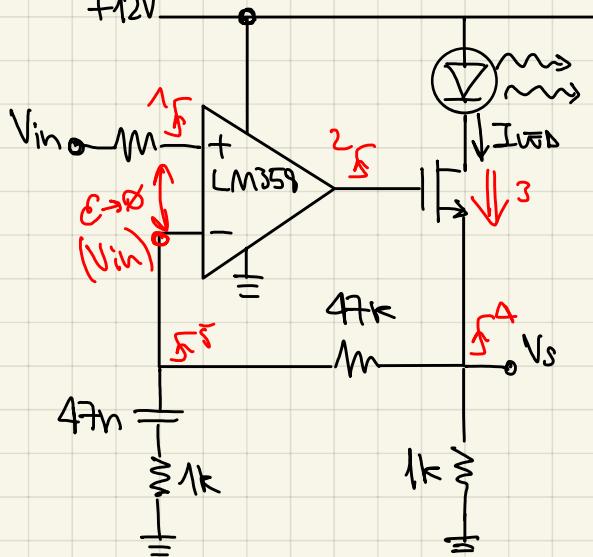

MOSFET: $V_T = 0.5V$

$$k = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_n = 12 \text{ mA/V}^2$$

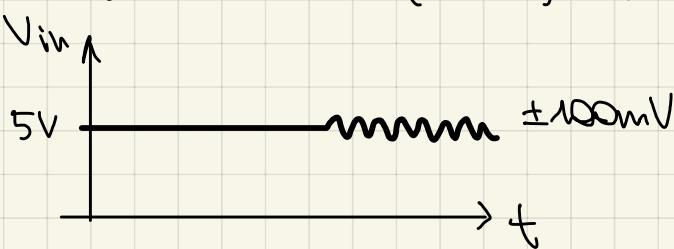
$V_{in}(t)$ has 5V DC + ($\pm 100\text{mV}$) sinusoid



A Compute I_{VFD}/V_{in} relationship @ DC and I_{VFD} for $V_{in}=5V$

NEGATIVE FB \rightarrow V-to-I converter

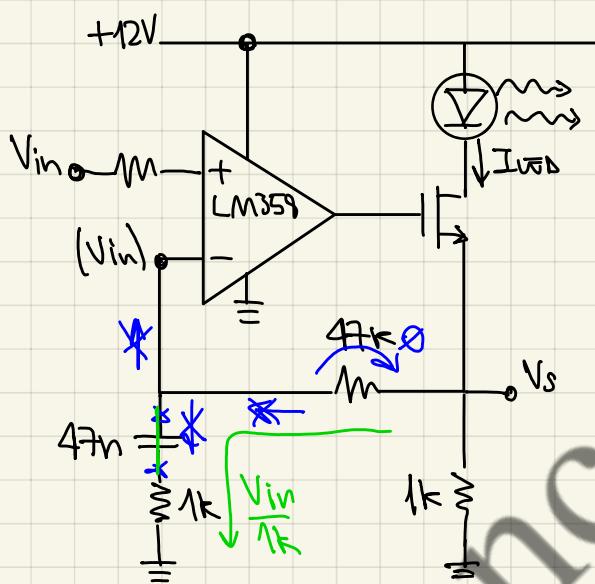(If we had a positive feedback it would have been a comparator)



$$I_{VFD}(0) = \frac{V_s}{1k} = \frac{V_{in}}{1k}$$

$$\rightarrow \frac{I_{VFD}(0)}{V_{in}} = 1 \text{ mA/V}$$

$$I_{VFD}(0) = \frac{V_s}{1k} + \frac{V_{in}}{1k} = \frac{1}{1k} (48V_{in} + V_{in}) = V_{in} \frac{49}{1k}$$

$$\frac{I_{VFD}(0)}{V_{in}} = \frac{49}{1k} = 49 \text{ mA/V}$$

$$V_{in} = 5V \text{ DC} \rightarrow I_{VFD}(0) = 1 \text{ mA/V} \cdot 5V = 5 \text{ mA}$$